

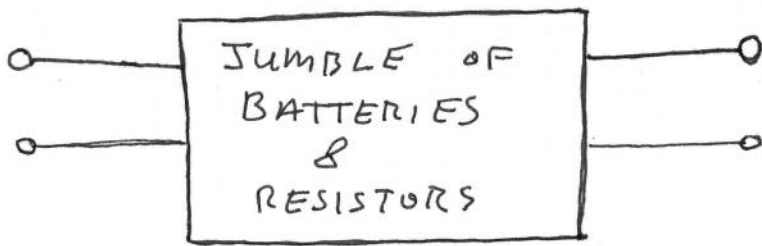


T.E. COAN

① THEVENIN & NORTON EQUIVALENTS

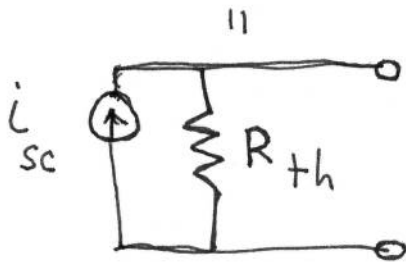

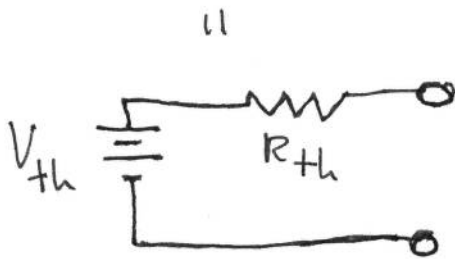ANY COLLECTION OF BATTERIES + RESISTORS THAT HAS 2 INPUTS AND 2 OUTPUTS CAN BE REPRESENTED AS A "THEVENIN EQUIVALENT."
SEE H. & H. p. 11.



$$I_{sc} = \frac{V_{th}}{R_{th}}$$

② GENERAL OHM'S LAW

FOR COMPLEX I, V, Z:

$$I = V/Z$$

$$V = IZ$$

$$Z = Z_1 + Z_2 + Z_3 + \dots \quad (\text{SERIES})$$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots \quad (\text{PARALLEL})$$


$$Z_R = R \quad (\text{RESISTOR})$$

$$Z_C = -j/\omega C \quad (\text{CAPACITOR})$$

$$Z_L = j\omega L \quad (\text{INDUCTOR})$$


$$j^2 = -1$$

③ SIMPLE RC FILTERS

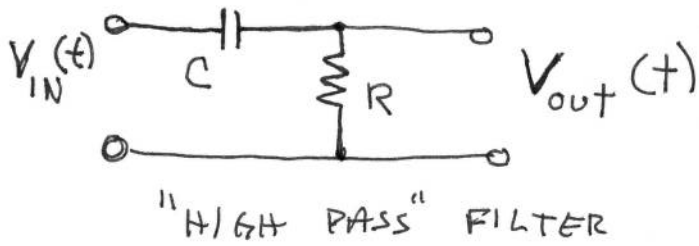

$$f_{3dB} = \frac{1}{2\pi RC} \quad [f] = \text{Hz}$$

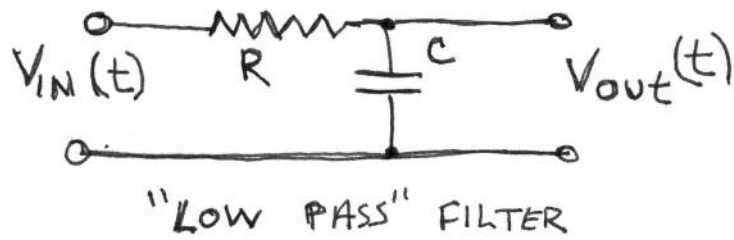FOR $f \gg f_{3dB}$, $V_{out} \approx V_{in}$




$$f_{3dB} = \frac{1}{2\pi RC}$$

FOR $f \ll f_{3dB}$, $V_{out} \approx V_{in}$



$$\text{dB} = 20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$

V_o/V_{in}	dB
$\frac{1}{\sqrt{2}}$	-3
$\frac{1}{2}$	-6
$\frac{1}{10}$	-20

④ FULL WAVE RECTIFIER

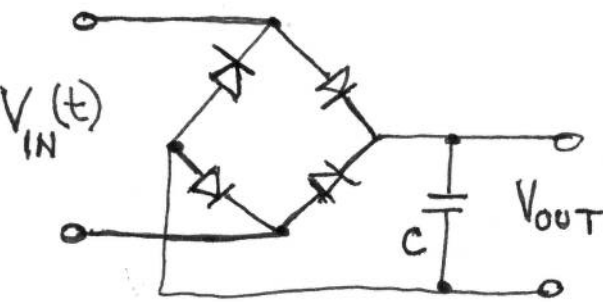

$$\Delta V = \frac{I_{LOAD}}{2fC}$$

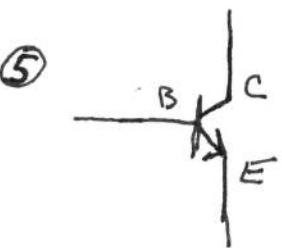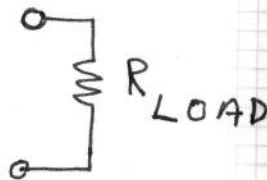

NPN TRANSISTOR

WHEN "ON",

$$V_B - V_E = 0.6 \text{ VOLTS}$$

$$i_C = h_{fe} i_B \quad (h_{fe} \approx 100)$$

$$i_E = (h_{fe} + 1) i_B$$

$$I_C = I_S \left\{ e^{V_{BE}/V_T} - 1 \right\}$$


$$V_T = 25 \text{ mV}$$

$$\Delta V_{BE} = -2.1 \text{ mV}/^\circ\text{C}$$

"EBERS-MOLL" EQN

$$I_C = I_{C0} \left\{ \exp(V_{BE}/25 \text{ mV}) \right\}$$

⑥ EMITTER FOLLOWER

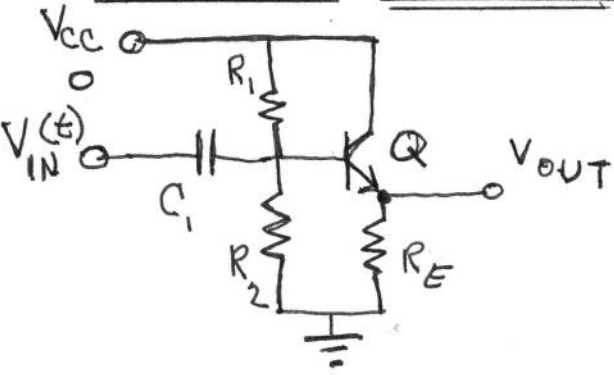

$$Z_{IN}^Q \approx (h_{fe} R_E)$$

$$Z_{IN}^{CIRCUIT} = R_{th_bias} \parallel Z_{IN}^Q$$

$$\approx R_{th_bias}$$

$$Z_{out} = R_E \parallel \frac{R_{th_bias}}{h_{fe}}$$

$$\approx \frac{R_{th_bias}}{h_{fe}}$$

$$V_{out}(t) \approx V_{IN}(t) - 0.6 \text{ VOLTS}$$


① CHOOSE $R_{th_bias} = R_1 \parallel R_2 \ll Z_{IN}^Q$

FOR STABLE BIASING.

② CHOOSE C_1 FROM f_{3dB}

$$C_1 = \frac{1}{2\pi f_{3dB} R_{th_bias}}$$


⑦ COMMON EMITTER AMP

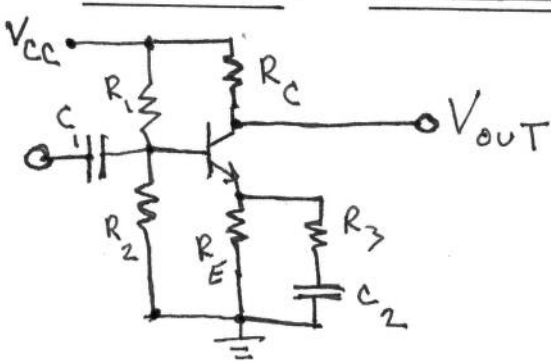

$$G = \frac{V_{out}(t)}{V_{in}(t)} = -\frac{R_C}{R'_E} ; R'_E = R_E \text{ EFFECTIVE}$$

SEE LAB MANUAL, P. 115

⑧ DIFFERENTIAL AMP

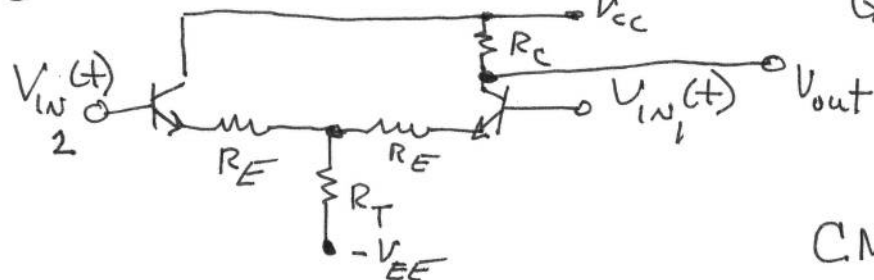

$$G_{DIFF} \equiv \frac{V_{out1}}{V_1(t) - V_2(t)} = \frac{R_C}{2(R_E + r_e)}$$

$$G_{CM} \equiv \frac{V_{out1}}{V_{com}} = \frac{-R_C}{2R_T + R_E + r_e}$$



$$CMRR = G_{DIFF} / G_{CM}$$

$$= R_T / R_C$$

$$V_1(t) \approx V_1(t) + V_{com}$$

$$V_2(t) \approx V_2(t) + V_{com}$$


9) CURRENT MIRRORS

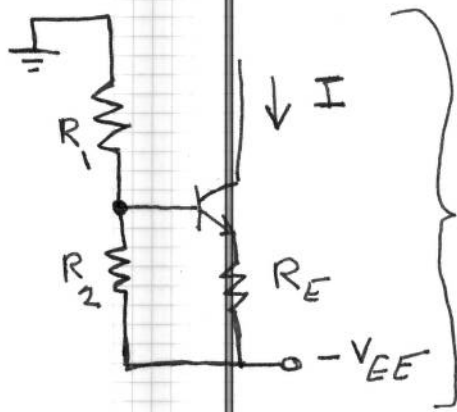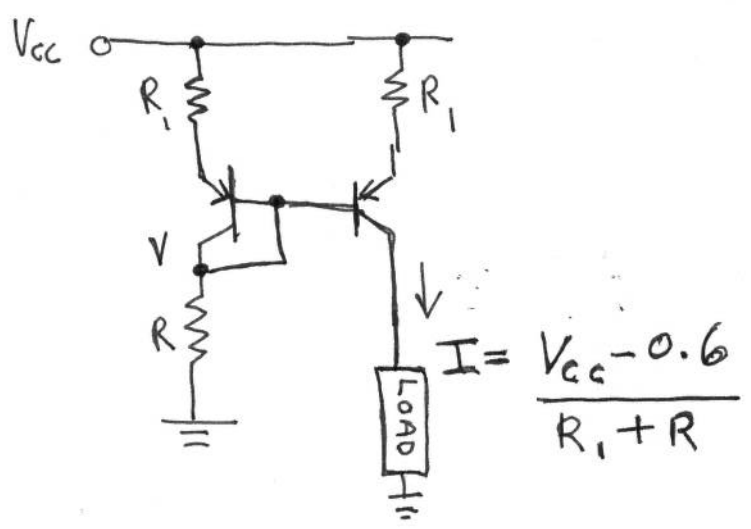

USEFUL FOR R_T IN DIFF. AMP

OP-AMPS

① VERY USEFUL + VERSATILE DEVICE.

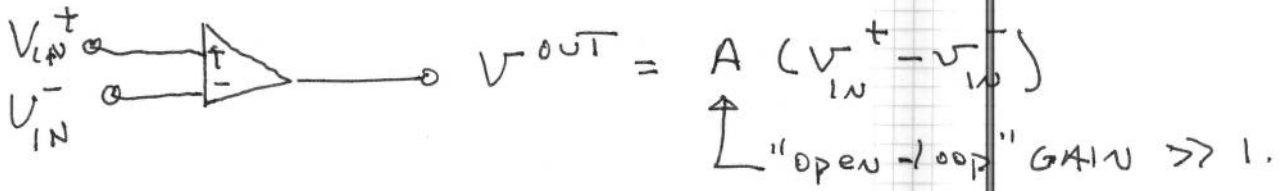


"GOLDEN RULES"

① OP-AMP INPUTS (INVERTING (-) & NON-INVERTING (+)) DRAW NO INPUT CURRENT.

② w/ "NEGATIVE FEEDBACK", V_{OUT} TRIES TO MAKE $\Delta V_{IN} = V^+ - V^-$ EQUAL ZERO.

CAVEAT: RULES ① & ② WORK ONLY IF OP-AMP NOT SATURATED.

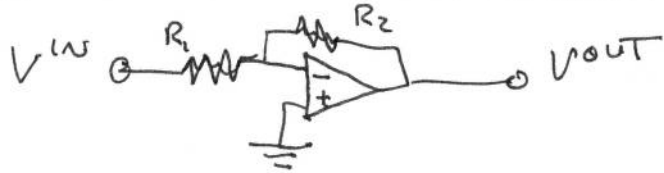
② STANDARD CONFIGURATIONS w/ NEGATIVE FEEDBACK.



INVERTING AMP

$$V_{OUT} = - \left(\frac{R_2}{R_1} \right) V_{IN}$$


GAIN

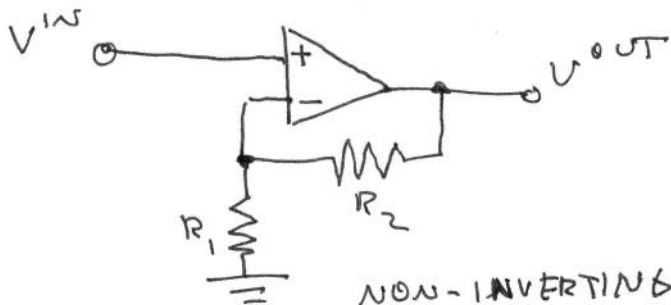

NON-INVERTING AMP

$$V_{OUT} = \left(1 + \frac{R_2}{R_1} \right) V_{IN}$$

GAIN

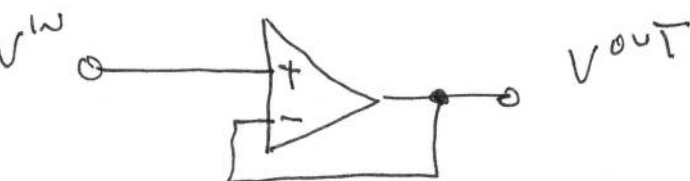

FOLLOWER

$$V_{OUT} = V_{IN}, \quad G = 1$$


$Z_{IN} \gg 1$

OP-AMPS

③ OP-AMP "REALITIES" & CAVEATS.


- GOLDEN RULES WORK ONLY IF OP-AMP NOT SATURATED;
THIS MEANS $V_{OUT} < V_{OUT_{max}} (\approx V_{CC})$
- FEEDBACK MUST BE NEGATIVE.
- THERE MUST BE FEEDBACK AT DC ($f=0$),
OTHERWISE OP-AMP WILL SATURATE.
- RESPECT $(V_{IN}^+ - V_{IN}^-)$ INPUT VOLTAGE LIMITS.

OP-AMP INTEGRATOR:

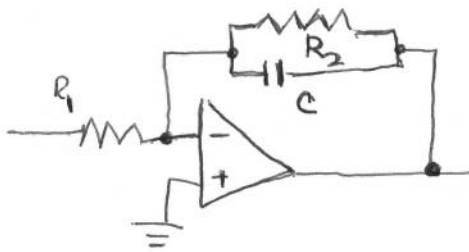

$$V_{OUT} = -\frac{1}{R_1 C} \int V_{IN} dt + \text{CONST}$$


DIFFERENTIATOR

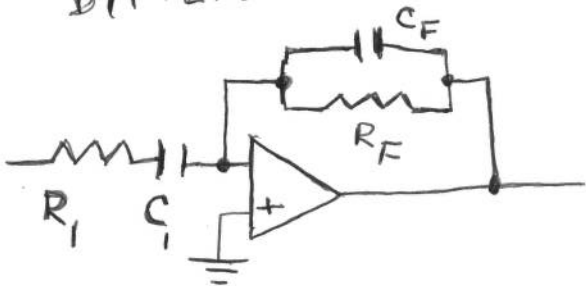

$$V_{OUT} = -R_f C_1 \frac{dV_{IN}}{dt}$$

PAY ATTENTION TO WHAT R'S AND WHAT C'S
APPEAR IN THE FORMULAE.


OSCILLATORS

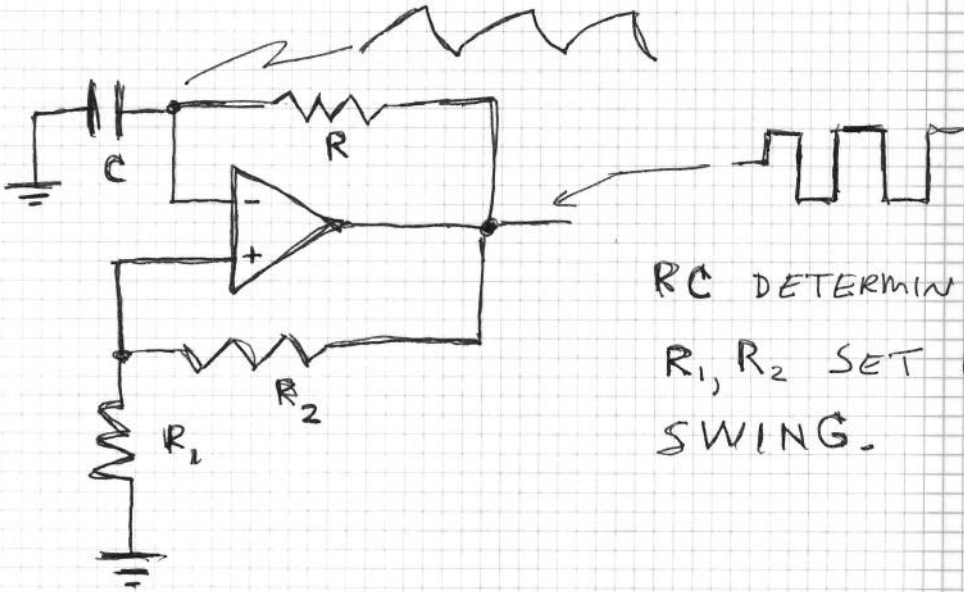

RC DETERMINE PERIOD

R_1, R_2 SET MIN/MAX OF OUTPUT SWING.

555 OSCILLATOR

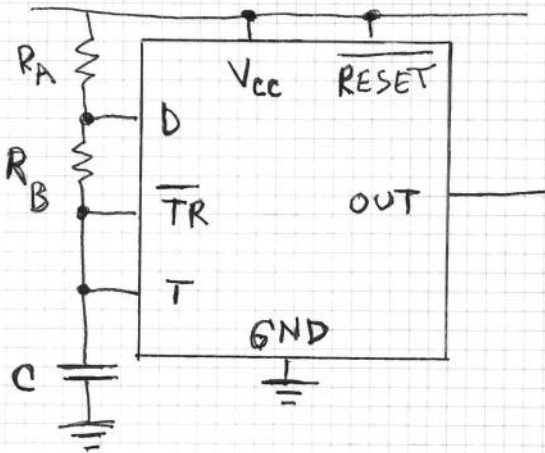

$$T = \ln 2 (R_A + 2R_B) C$$