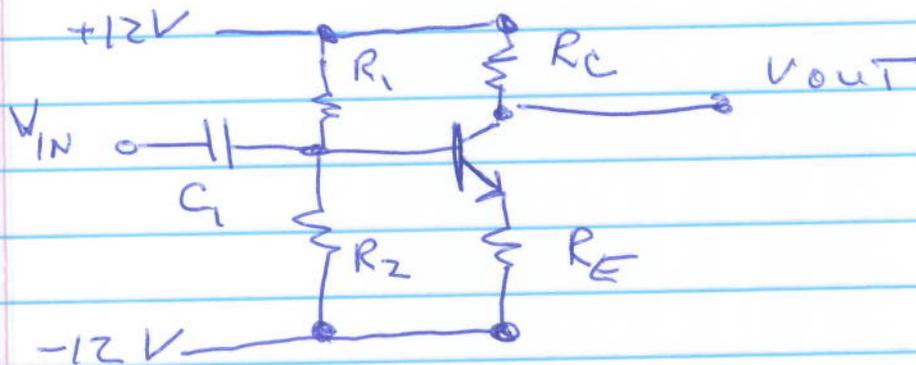


## COMMON EMITTER AMPLIFIER

$$G = -10, V_{\text{SUPPLY}} = +12 \text{ V}$$

$$f_{3\text{dB}} = 10 \text{ kHz (WORKING } f = 100 \text{ kHz)}$$

FOLLOW EXAMPLE ON P116, MANUAL  
FOR SIMPLICITY I G N O R E B Y P A S S C.



FOR  $I_Q = 1 \text{ mA}$ , CHOOSE  $R_C = 10 \text{ k}\Omega$

$G = -10$ , CHOOSE  $R_E = 1 \text{ k}\Omega$

NOTE, THIS PUTS  $V_E = -1 \text{ V}$

SO,  $V_B = -10.4 \text{ V}$

~~SELECT~~ SELECT  $R_1/R_2$  RATIO

$$\frac{R_2}{R_1} \approx \frac{1.6}{22.4} \quad (\text{USING ABSOLUTE VALUES OF VOLTAGE DROPS})$$

$$\approx \frac{1}{14}$$

SET  $R_2 = 10 \text{ k}\Omega$ ,  $R_1 = 120 \text{ k}\Omega$   
(STD RESISTOR VALUES)

## COMMON EMITTER AMPLIFIER

CALCULATE  $V_B$  MORE ACCURATELY

$$V_B = \frac{R_2}{R_2 + R_1} * 24V - 12V$$
$$= \frac{24V}{13} - 12V$$

$$V_B = -10.1V$$

$$\Rightarrow V_E \approx -10.7V$$

$$\Rightarrow I_Q = \frac{-10.7V - (-12V)}{1k\Omega} = 1.3 \text{ mA}$$

THIS IS CLOSE ENOUGH TO OUR DESIGN CURRENT OF  $I_Q = 1 \text{ mA}$ .

$$f_{3dB} = \frac{1}{2\pi R' C_1}, \quad w/R' = R_1 || (R_2 || \beta R_E) \approx R_2$$


$$\Rightarrow C_1 \approx \frac{1}{2\pi f_{3dB} R_2}$$

$$\text{SET } f_{3dB} = \frac{1}{10} f_{\text{work}}$$
$$= 10 \text{ kHz}$$


$$\text{So, } C_1 \approx \frac{1}{2\pi \times 10 \text{ kHz} \times 10k\Omega}$$

$$C_1 \approx 0.001 \mu\text{F}$$
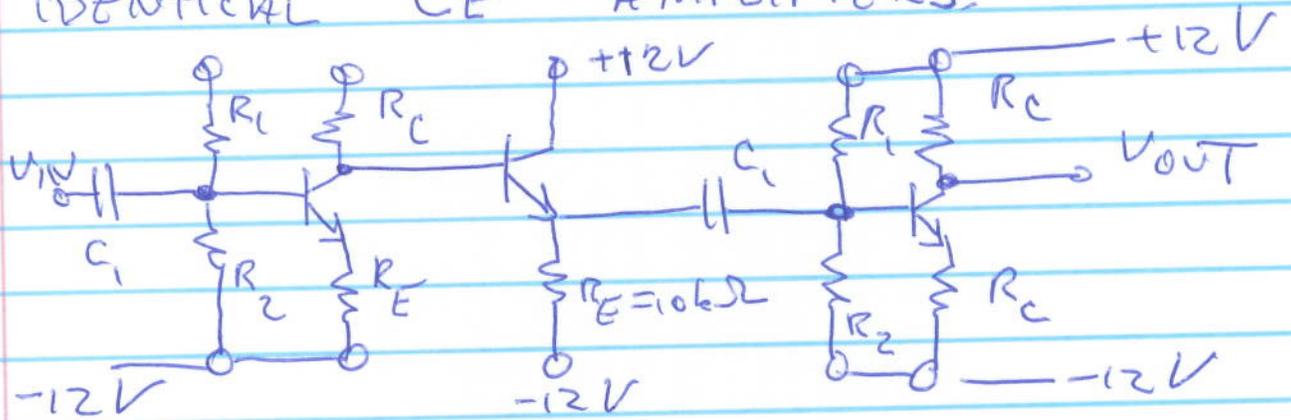
#2 MANY VARIATIONS POSSIBLE.  
BASIC IDEA IS TO INSERT  
EMITTER FOLLOWER BETWEEN  
IDENTICAL CE AMPLIFIERS.


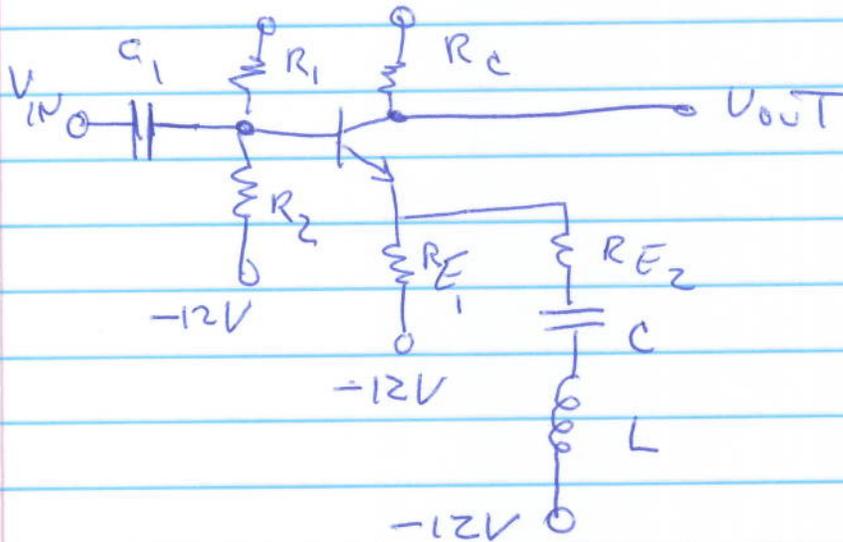
#3. MANY VARIATIONS POSSIBLE.  
HERE'S ONE.



CHOOSE  $R_1$  &  $R_2$ :

$$R_1 = 120 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$C_1 = 0.01 \mu\text{F}$$

$$R_C = 15 \text{ k}\Omega$$

$$R_{E2} = 150 \Omega$$

$$\left. \begin{array}{l} R_C = 15 \text{ k}\Omega \\ R_{E2} = 150 \Omega \end{array} \right\} G = -15 \text{ k}\Omega / 150 \Omega = -100$$

$$R_{E1} = 1 \text{ k}\Omega$$

$$Z_L = j\omega L$$

$$Z_C = -j/\omega C$$

$\left. \begin{array}{l} Z_L = j\omega L \\ Z_C = -j/\omega C \end{array} \right\} \omega f = 10 \text{ kHz}$  THESE IMPEDANCES CANCEL