

#1. LET  $V_L$  = VOLTAGE DROP ACROSS  $R_L$

IN FIG 1, IF  $R_L = \infty$ , THEN  $V_L = \frac{R_2}{R_1 + R_2} \times V_0$

MUST BE SAME IN FIG 2.

HENCE

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_0$$

SUPPOSE NOW  $R_L = 0$ .

IN FIG 2,  $i = V_{TH} / R_{TH}$

IN FIG 1,  $R_L = 0 \Rightarrow i = V_0 / R_1$ ,  
WHERE  $i$  = CURRENT THROUGH  $R_L$ .


HENCE,  $i = V_0 / R_1 = V_{TH} / R_{TH}$

$$= \frac{R_2}{R_1 + R_2} \cdot V_0 / R_{TH}$$

$$\Rightarrow \boxed{R_{TH} = \frac{R_1 R_2}{R_1 + R_2}}$$

PHYS 4211

# 2

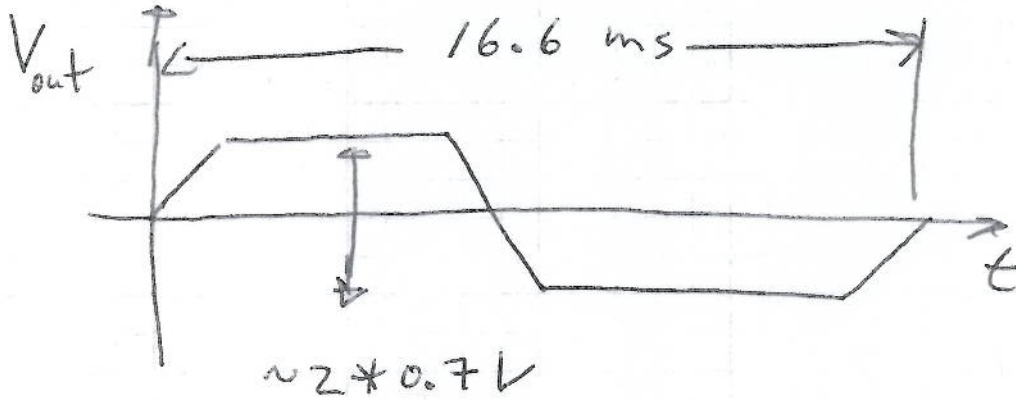

WAVEFORM IS SYMMETRIC  
DIODES CLAMP OUTPUT.  
USEFUL TRICK FOR LIMITING  
VOLTAGE INPUT INTO  
SENSITIVE AMPLIFIERS.

