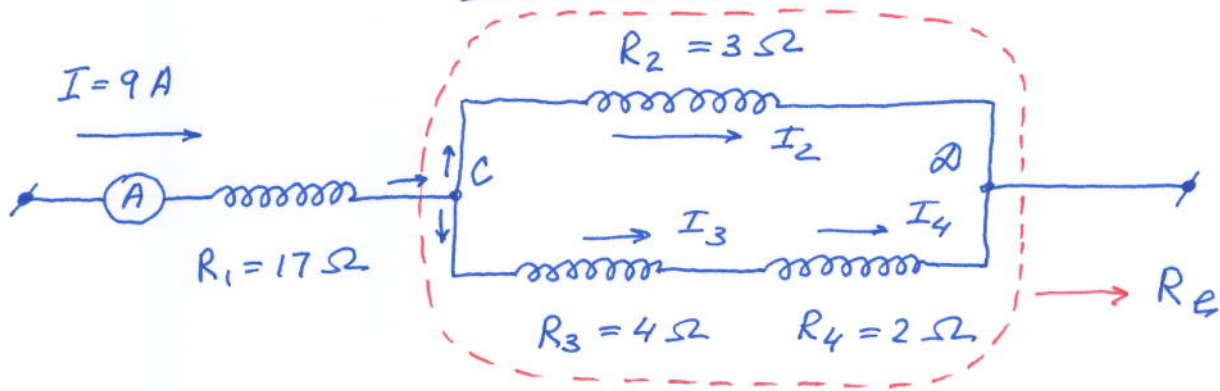


#18.33



1) find  $R_e$

$$\frac{1}{R_e} = \frac{1}{R_2} + \frac{1}{R_3 + R_4} \quad \Rightarrow \quad \underline{\underline{R_e = \frac{1}{2}}}$$

2) Ohm's Law to find  $V_{CD}$ :

$$V_{CD} = I R_e \quad \Rightarrow \quad \underline{\underline{V_{CD} = 18\text{ V}}}$$

3) Ohm's Law to find  $I_2$ :

$$V_{CD} = I_2 R_2 \quad \Rightarrow \quad \underline{\underline{I_2 = 6\text{ A}}}$$

4) Note that  $I_3 = I_4$  ( $R_3, R_4$  are in series)

$$I = I_2 + I_3 \quad \Rightarrow \quad \underline{\underline{I_3 = 3\text{ A}}}, \quad \underline{\underline{I_4 = 3\text{ A}}}$$