

#18.69

Solution to diff. eq. : $\frac{\Delta Q}{\Delta t} R + Q/C = \mathcal{E}$ (*)

$$\frac{\Delta Q}{\Delta t} \rightarrow \frac{dQ}{dt}$$

$$R \frac{dQ}{dt} + Q/C = \mathcal{E} \quad (**)$$

Solution to homogeneous eq. $R \frac{dQ}{dt} + Q/C = 0$

is $Q(t) = A e^{-t/RC}$ where A - const. (see 18.9)

(which can be found from initial condition)

For non-homogeneous eq. (***) assume that A is function, i.e. $A = A(t)$

Try $Q(t) = A(t) e^{-t/RC}$ (*) as solution

Let's find $\frac{dQ}{dt}$:

$$\frac{dQ(t)}{dt} = \frac{d}{dt} (A(t) \cdot e^{-t/RC}) = \frac{dA(t)}{dt} \cdot e^{-t/RC} + A(t) \frac{d}{dt} (e^{-t/RC})$$

$$\frac{dQ(t)}{dt} = A'(t) e^{-t/RC} - \frac{A(t)}{RC} e^{-t/RC}$$

plug in this into (**); replace $Q(t)$ accordingly (*)

$$\Rightarrow R A'(t) = \mathcal{E} e^{t/RC}$$

integrate: $A(t) = \mathcal{E} C e^{t/RC} + B$, B - const

$$\Rightarrow Q(t) = B e^{-t/RC} + \mathcal{E} C$$

$$I(t) = \frac{dQ(t)}{dt} = -\frac{B}{RC} e^{-t/RC}$$

Initial condition $I(0) = \frac{\mathcal{E}}{R}$ (read p 739)


\Rightarrow gives $B = -\mathcal{E} C$

therefore

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

#18.93

Can transform to more convenient look

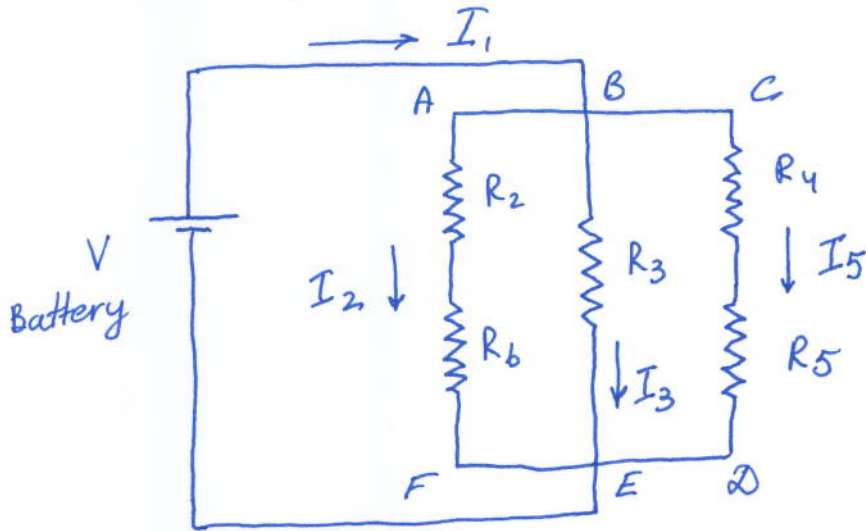

$$R_2 = 5\Omega; R_3 = 30\Omega; R_4 = 2\Omega; R_6 = 10\Omega;$$

$$I_3 = 1A; I_2 = 2A; I_4 = 5A;$$

What are V, R, I_2, I_5 -? (where $R \equiv R_5$)

1) Note

$$I_4 = I_5$$

$$I_6 = I_2$$

2) Consider closed branch B-C-D-E:

Apply Loop Rule:

$$-I_3 R_3 + I_5 R_4 + I_5 R_5 = 0$$

(direct. is counter-clockwise)

$$\Rightarrow 30 = I_5 (2 + R)$$

$$\Rightarrow \boxed{R = 4}$$

3) Consider node B:

Apply Node Rule

$$I_1 = I_2 + I_3 + I_5$$

$$\Rightarrow \boxed{I_1 = 8A}$$

4) Voltage V : ($AF \parallel BE \parallel CD$)

$$\Rightarrow \underline{V = I_3 R_3}$$

$$\boxed{V = 30 \text{ V}}$$