

In Series

L11 p1

In this configuration,

$$\Delta V = \Delta V_1 + \Delta V_2$$

while  $Q_1 = Q_2$  since charge in a conductor between  $C_1 + C_2$

Let's consider some "equivalent" capacitor to  $C_1 || C_2 ||$


$$\Delta V = Q / C_{equiv} = \Delta V_1 + \Delta V_2$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

When in series, sum the inverses of each capacitance to get the equivalent capacitance.

NOTE:  $C_{eq} < C_1, C_2$  always

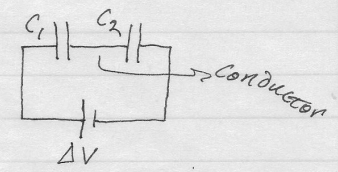

Example:

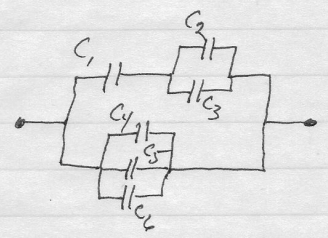

What is Equivalent Capacitance?

$$C_{23} = C_2 + C_3 ; C_{456} = C_4 + C_5 + C_6$$

$$\frac{1}{C_{123}} = \frac{1}{C_1} + \frac{1}{C_{23}}$$

$$C_{TOT} = C_{123} + C_{456}$$

$$= \left[ \frac{1}{C_1} + \frac{1}{C_2 + C_3} \right]^{-1} + C_4 + C_5 + C_6$$


1304/1404

L6, ~~10/11~~  
p11
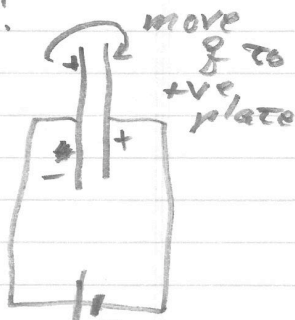
### Energy Stored in Charged Cap.

Consider 2 plates:

→ move <sup>+</sup> charge,  $dq$ ,  
to + plate




( $U=0$ )

→ initially, no work  
to move it

→ once some charge  
moved, work required

→ more + more as charge  
deposited

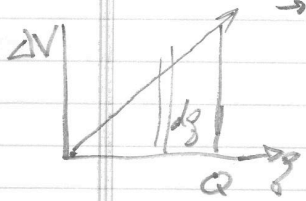→ work required to move  
 $dq$  to +ve plate (higher  
potential)



$$dW = \Delta V dq = \frac{Q}{C} dq$$

Total work, is

$$W = \int_0^Q \frac{Q}{C} dq = \frac{1}{C} \int_0^Q Q dq = \frac{Q^2}{2C}$$

→ appears electric  
potential energy  $U$

$$U = \frac{Q^2}{2C} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2$$

Energy  
stored in  
ch. cap.