

Capacitive Circuit

(1)

$$V_c = V_{c,m} \sin \omega t$$



What is relationship between voltage & current? Recall $i_c = C V_c$

$$i_c = C V_{c,m} \sin \omega t$$

Take derivative to get the current



$$i_c = \omega C V_{c,m} \cos \omega t$$

$\frac{1}{X_c} \rightarrow$ capacitive reactance

$$= \frac{V_{c,m}}{X_c} \sin(\omega t + \pi/2)$$

90° out-of-phase
with voltage

$$\therefore \underline{i_c}$$

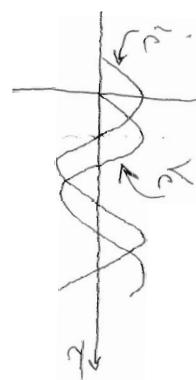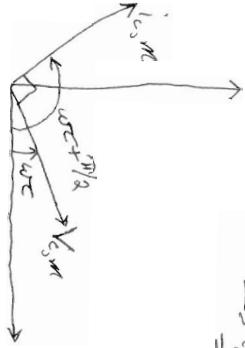

Inductive Circuit

(2)

$$V_L = V_{L,m} \sin \omega t$$



We know $V_L = L \frac{di}{dt}$, so we have



$$\begin{aligned} i_L &= \int \frac{di}{dt} dt = -\frac{V_{L,m}}{\omega L} \int \sin \omega t dt \\ &= -\frac{V_{L,m}}{\omega L} \cos \omega t \\ \therefore \underline{i_L} &= inductive reactance \end{aligned}$$

Noting that $-\cos \omega t = \sin(\omega t - \pi/2)$,

$$i_L = \frac{1}{\omega L} V_{L,m} \sin(\omega t - \pi/2)$$

90° out-of-phase
with voltage


Polar diagram:

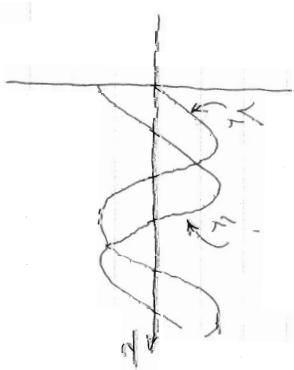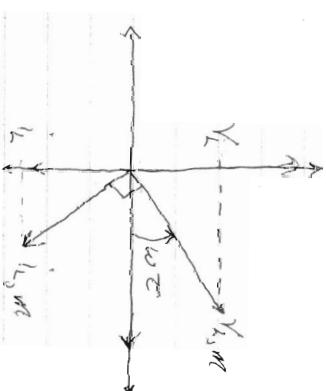

The RLC Circuit Revision:


(3)

$$V = V_m \sin \omega t$$

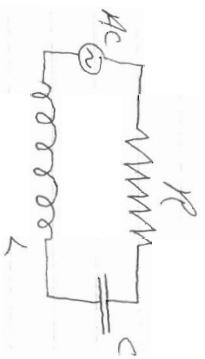

Again, we would like to understand the relationships between current, i , and V .

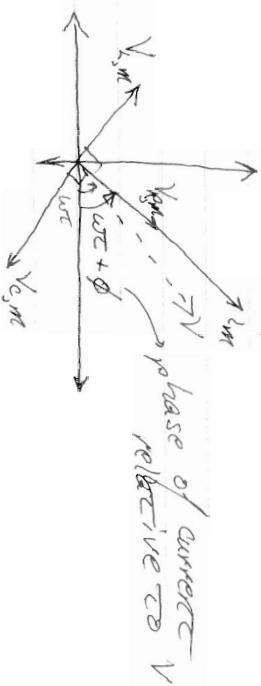Since each element has voltage drop, at any instant $V = V_R + V_L + V_C$. The current thru all three elements must be the same at any given time, so relative phases exhibited by voltages



$$\begin{aligned} V_m &\rightarrow V_m^2 = V_{R,m}^2 + (V_{L,m} - V_{C,m})^2 \\ &= (i_m R)^2 + (i_m X_L - i_m X_C)^2 \\ &= i_m^2 (R^2 + (X_L - X_C)^2) \end{aligned}$$

$$\begin{aligned} \text{Thus } i_m &= V_m / \sqrt{R^2 + (X_L - X_C)^2} = V_m / Z \\ \text{and we define denominator as impedance} \end{aligned}$$

$$\begin{aligned} Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{R^2 + (1/X_C - 1/X_L)^2} \quad (\text{a function of } \omega) \end{aligned}$$

Note, ω here is driving frequency of impressed voltage. This can be different than the natural frequency of the LC components ($\omega_{nat} = 1/\sqrt{LC}$).

$$\begin{aligned} \text{The final phase angle } \phi &\text{ is} \\ \tan \phi &= \frac{V_{L,m} - V_{C,m}}{V_{R,m}} = \frac{i_m X_L - i_m X_C}{i_m R} = \boxed{\frac{X_L - X_C}{R}} \end{aligned}$$

RLC Impedance

Consider components // & \perp to V_m

(4)