

# Quiz 3

1. equipotential have no work on line  
electric field represent gradient of energy.  
if ~~they~~ electric field have component on potential line  
⇒ contradict

+2

2. electric energy in  $\vec{E}$  field

+2

3.



$$V = \sum_{i=1}^4 \frac{k q_i}{r_i} = \frac{9 \cdot 10^9}{\cancel{3}} \times 4 \times 10^{-6} C$$


≈

$$\frac{9 \cdot 10^9 \cdot (4+8) \cdot 10^{-6}}{\sqrt{5} \cdot (10^{-2})^2} \approx 4.8 \cdot 10^6 V$$

2

4.

$$\sqrt{10^2 + 8^2} = 12.8 N$$

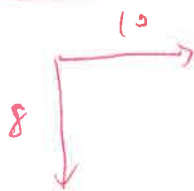

$$\tan \frac{-8}{10}$$

4

$$= -38.66^\circ$$


2

total =

24

# Quiz 4

15 points  
total

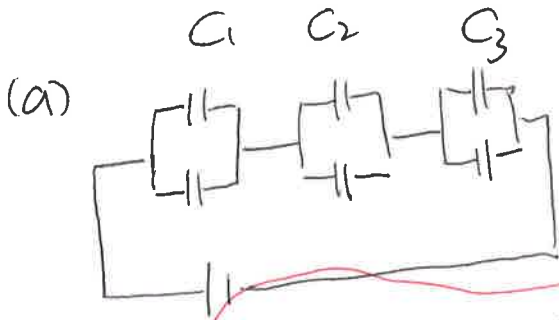

$$\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad (3)$$

$$C_1 = C_2 = C_3 = 10 + 5 \text{ pF} \quad (3)$$

$$\frac{1}{C_{tot}} = \frac{1}{15} + \frac{1}{15} + \frac{1}{15}$$

$$= \frac{3}{15} \Rightarrow C_{tot} = 5 \text{ pF} \quad (1)$$

(b)  $Q = CV = 5 \cdot 9 = 45 \text{ pC} \quad (1)$

(c)  $\frac{1}{2} CV^2 = \frac{1}{2} \cdot 5 \cdot 9^2 = 405 \text{ pJ} \quad (1)$   
 202.5

Q5

$$1. V = IR + \frac{Q}{C} = R \frac{dQ}{dt} + \frac{Q}{C}$$

inhomogeneous:  $Q = at + b \Rightarrow V = \frac{a}{R} + \frac{a + b}{C}$

③  $\Rightarrow a = 0, b = CV$

homogeneous:  $0 = R \frac{dQ}{dt} + \frac{Q}{C} \quad Q = A e^{\alpha t}$

③  $\Rightarrow (AR\alpha + \frac{A}{C}) e^{\alpha t} = 0$

$\Rightarrow \alpha = -\frac{1}{RC}$

$$\Rightarrow Q(t) = A e^{-\frac{t}{RC}} + CV$$

$$Q(0) = a, I(0) = \frac{V}{R} : A = -CV$$

②  $\Rightarrow Q(t) = CV(1 - e^{-\frac{t}{RC}})$

1. (a)  $Q(t) = CV \cdot 0.9 \Rightarrow 1 - e^{-\frac{t}{RC}} = 0.9, e^{-\frac{t}{RC}} = 0.1$

①  $t = 1.38 \cdot 10^{-7} s$  ①

(b)  $I(t) = \frac{V}{R} e^{-\frac{t}{RC}} = \frac{12}{10} \cdot 0.1 = 0.12 A$

④ ①

2.  $F = q \vec{v} \times \vec{B} = ?? \quad I = \frac{\Delta Q}{\Delta t} \Rightarrow F = IB \ell$

$F = 0.3 \cdot 0.5 \cdot 2 = 0.3 N$

①

~~$F = IB \ell$~~

Q7

$$1. (a) \omega = \frac{1}{\sqrt{LC}} = 1.414 \cdot 10^5$$

$$Q_{max} = CV$$

$$(b) U = \frac{Q^2}{2C} + \frac{1}{2} LI^2 = \frac{Q_{max}^2}{2C} (\cos \omega t)^2 + \dots = 3.6 \cdot 10^{-10} \text{ J}$$

$$\frac{1}{2} CV^2 = \frac{1}{2} \cdot 144 \cdot 5 \cdot 10^{-12} \text{ J}$$

$$(c) \frac{U \cos^2(\omega \cdot 5)}{U} = 4$$

$$\omega \cdot 5 = \frac{5}{\sqrt{5 \cdot 10^{-11}}} = \sqrt{\frac{1}{5} \cdot 10^{11}} = \sqrt{5 \cdot 10^1}$$

$$\Rightarrow \cos^2(\omega t) = 0.94$$

Extra Q1

$$\omega = \frac{1}{\sqrt{LC}} = 6 \cdot 10^4 \text{ Hz}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (4)$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C} \quad (4)$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

Q8

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \cancel{8.07} \Omega \quad 8 \Omega \quad (2)$$

$$\omega L \quad (4)$$

$$\frac{1}{\omega C}$$

$$\tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \cancel{-0.11 \text{ rad}}$$

$$= \cancel{-0.82 \text{ rad}} \quad 0.0014 \text{ rad}$$

$$= \cancel{-47^\circ} \quad \cancel{-63^\circ} \quad 0.08^\circ$$

$$(2)$$

Q8 b:

$$Z^2 = R^2 + (X_L - X_C)^2 \quad (+4)$$

$$\omega = 2\pi f$$

$$Z^2 - R^2 = \left( \omega L - \frac{1}{\omega C} \right)^2$$

$$\omega L = \sqrt{Z^2 - R^2} + \frac{1}{\omega C}$$

$$L = \frac{1}{\omega} \left( \sqrt{Z^2 - R^2} + \frac{1}{\omega C} \right) = 0.12 \text{ H}$$

$$(4)$$

Q10 extra:

$$\delta \theta \approx (n + \frac{1}{2}) \lambda$$

(a)

$$\delta \theta \approx \frac{1}{2} \lambda$$

$$325 \cdot 10^{-3}$$

$$= 0.186^\circ$$

(b)

$$\delta \theta \approx \frac{5}{2} \lambda$$

$$1625 \cdot 10^{-3}$$

$$= 0.93^\circ$$

Q10

1.

$$n_w \sin \theta_w = n_d \sin \theta_d$$

$$1.3 \sin 35^\circ = n_d \sin 12^\circ = 3.58$$

2.

$$c = \lambda f$$

$$\lambda = 500 \cdot 10^{-9}$$

$$f = \frac{3 \cdot 10^8}{500 \cdot 10^{-9}}$$

$$6 \cdot 10^{16} \text{ Hz}$$