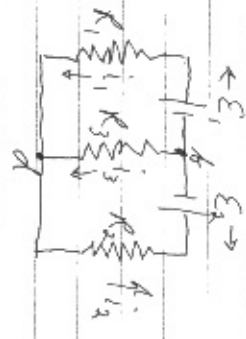


## Junction Theorem

①



In multiloop circuits

current in  $R_1$  may not be same as in  $R_2$  or  $R_3$   
 - have two junctions @  $b$  &  $d$

At each junction, charge flows in on some conductors, & flows out on others

@  $b$ :  $i_2$  flows in while  $i_1$  &  $i_3$  flow out

$\therefore i_1 + i_3 = i_2$  (from conservation of charge)

$$i_1 + i_3 - i_2 = \boxed{\sum i = 0}$$

At any junction, the algebraic sum of the currents must be zero.

②

Consider previous diagram

For left loop in counterclockwise direction:

$$E_1 - i_1 R_1 + i_3 R_3 = 0$$

The right loop has

$$-i_3 R_3 - i_2 R_2 - E_2 = 0$$

Plus unknown junction rule

$$i_3 + i_1 - i_2 = 0$$

You can solve these 3 equations for the 3 unknown currents:

$$i_1 = \frac{E_1 (R_2 + R_3) - E_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$i_2 = \frac{E_1 R_3 - E_2 (R_1 + R_3)}{R_1 R_3 + R_1 R_2 + R_1 R_3}$$

$$i_3 = \frac{E_1 R_2 + E_2 R_1}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

so we see  $i_3$  goes up  
 (i.e. opposite to our choice)  
 in figure.

Some notes about loop + junction rules:

# of times can use junction rule equals one less than the # of junction pts.  
(= 1 in example above)

# loops depends on finding new loops that have new unknown currents in each new equation  
(= 2 for previous example since one loop has 2 new currents, + next loop adds the third remaining current)

The # of independent Eqs will equal the # of unknown currents

(3)

Ex 28.8

1309/1404

29, p3  
18, p13

a) what is current?



so a-b)  $\sum \Delta V = 0$  (loop rule)  
E<sub>1</sub> - I R<sub>2</sub> - E<sub>2</sub> - I R<sub>2</sub> = 0

- I (R<sub>1</sub> + R<sub>2</sub>) = E<sub>2</sub> - E<sub>1</sub>

$$I = \frac{E_1 - E_2}{R_1 + R_2} = \frac{2V - 1.7V}{8\Omega + 10\Omega} = \underline{\underline{-0.33A}}$$

-ve sign means I flows opp. assumed, [a → b → c → d]


$1304/1409$

$L_{9,809}$   
 $L_{8,5019}$

$1304/1409$

$L_{9,809}$   
 $L_{8,5019}$

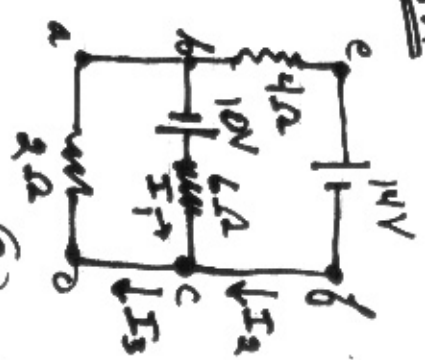Can't reduce  
to R's in series  
+ parallel



①  $I_1 + I_2 = I_3$

②  $10V - 6\Omega I_1 - 2\Omega I_3 = 0$   
(for abcd)

6 of c & d) ③  $14V + 6\Omega I_1 - 10V - 4\Omega I_2 = 0$

using ① in ②,

$10V - 6\Omega I_1 - 2\Omega(I_1 + I_2) = 0$

④  $10V = 8\Omega I_1 + 2\Omega I_2$

simplifying ③,

⑤  $-12V = -3\Omega I_1 + 2\Omega I_2$


④ - ⑤ gives  $22V = 11\Omega I_1$   
 $I_1 = 2A$

Use in ⑤ to get  $I_2 = -3A$

Use in ① to get  $I_3 = -1A$

Ex 28.10

Multi-loop circuit

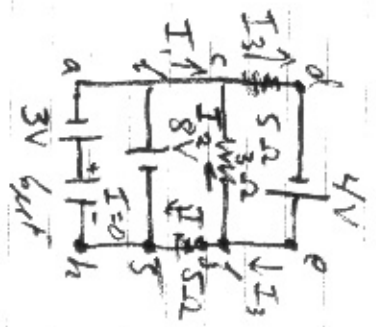

using  $\sum I_{in} = \sum I_{out}$

at f, gives

$I_3 = I_2 + I_1$

using  $\sum V = 0$ ,

8 of f & g:  $8V + 3\Omega I_2 - 5\Omega I_1 = 0$

cd of e:  $4V + 3\Omega I_2 - 5\Omega I_3 = 0$

use  $I_3 = I_2 + I_1$  in 20

$8V + 3\Omega I_2 = 5\Omega I_1$

$8V + 3\Omega I_2 - 5\Omega I_2 + 5\Omega I_2 = 0$

cd of e - 8 of f & g gives

$-4V - 11\Omega I_2 = 0 \Rightarrow I_2 = -\frac{4}{11}A$

using cd of e

$4V + \frac{12}{11}V - 5\Omega I_3 = 0$

$I_3 = I_1 + I_2$   
 $I = 1.05A + \frac{4}{11} = 1.38A$   
 $I_3 = +\frac{1}{5} \left( + \left( \frac{56}{11} \right) \right) = 1.08A$

28.10.8)

1304/1404

L9, p6

What is Q on bat capacitor?

→ find  $\Delta V$  across capacitor,

$$\sum \Delta V = 0$$

$$-8V + \Delta V_{cap} - 3V = 0$$

$$\Delta V_{cap} = 11V$$

$$Q = C \Delta V_{cap} \quad C = 6\mu F$$

$$Q = 66\mu C$$

1304/1404


L10, p1

### RC Circuits:

→ circuit containing resistors + cap in series

→ don't limit ourselves to steady state situation

→ consider time when cap is charging

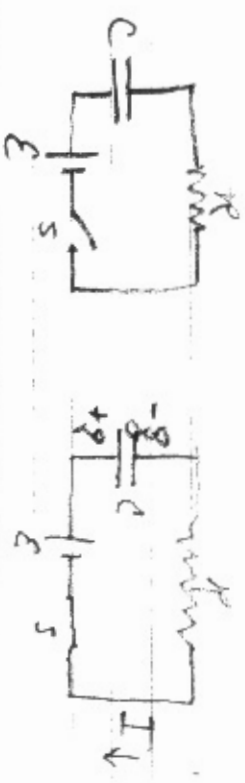

→  $\mathcal{E}$  sets up  $\vec{E}$  in wires

→ causes charge to be transferred

between plates + accumulating wires

→ until capacitor fully charged

→ max charge depends on voltage

→  $I = 0$  when max Q reached

1304/1404

10, p 2

Q20 When switch closed

$$\mathcal{E} \rightarrow \frac{q}{N} \rightarrow \text{instantaneous values}$$

↓ potential  
diff. across cap

at  $\tau = 0$

$$I_0 = \frac{\mathcal{E}}{R}$$

(I is maximum)

As  $V$  eventually falls across resistor as no  $\mathcal{E}$  in cap

when charges fully,  $I = 0$ , so

$$Q = C\mathcal{E} \text{ (max. charge)}$$

1304/1404

10, p 3

To get analytical expression

use  $I = \frac{dq}{dt}$

$$\frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

$$= \frac{q - C\mathcal{E}}{RC}$$

$$\frac{dq}{q - C\mathcal{E}} = \frac{-1}{RC} dt$$

Integrating + using  $q = 0$  at  $t = 0$

$$\int_0^q \frac{dq}{q - C\mathcal{E}} = -\frac{1}{RC} \int_0^t dt$$

$$\ln \left( \frac{q - C\mathcal{E}}{-C\mathcal{E}} \right) = -\frac{t}{RC}$$

$$\frac{q - C\mathcal{E}}{-C\mathcal{E}} = e^{-t/RC}$$

$$\frac{q}{C\mathcal{E}} = -1 + e^{-t/RC}$$


charge as  
AC for charging cap  $QC(1 - e^{-t/RC})$   
AC for cap  $Q(1 - e^{-t/RC})$

Differentiation:  $I = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$


130Y/110Y

410, p5

So,

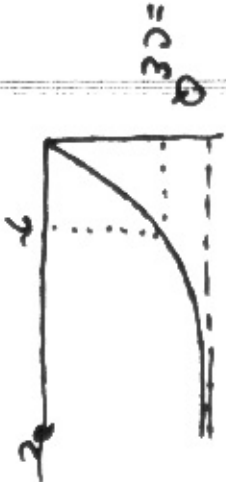

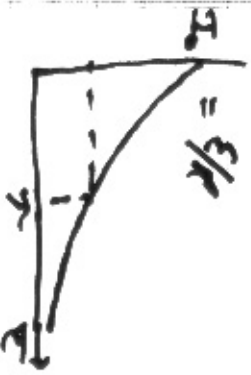Capacitor  
charge vs  
time  
no  $Q \rightarrow$  max.



Circuit current  
max  $I \rightarrow 0$


time constant,  $\tau = RC$   
time by which  $I$  goes  
to  $1/e$  of initial,  $I_0$   
 $\hookrightarrow = 0.37 I_0$   
in  $\tau$   $I = e^{-1} I_0 = 0.37 I_0$

130Y/110Y

410, p5

Ex 28.13 Discharging a Capacitor

How do  $Q, I$  vary

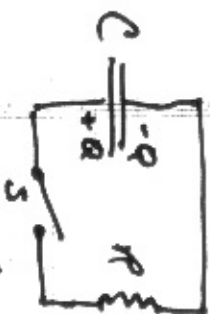

loop eq:

$$-\frac{Q}{C} - IR = 0$$

but  $I = dq/dt$ , so

$$-R \frac{dq}{dt} = \frac{Q}{C}$$

$$\frac{dq}{Q} = -\frac{1}{RC} dt$$

$$\int_0^Q \frac{dq}{Q} = -\frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$Q(t) = Q_0 e^{-t/RC}$$

$$I(t) = \frac{dq}{dt} = -\frac{Q}{RC} e^{-t/RC}$$

$$I_0 = Q_0/RC$$

1307/1409

2/10/22

→ after how long is  $Q$   $1/4$  of  $Q_0$

$$Q(t) = Q_0 e^{-\tau/\tau_c}$$

$$\frac{1}{4} Q_0 = Q_0 e^{-\tau/\tau_c}$$

$$\ln\left(\frac{1}{4}\right) = \ln\left(e^{-\tau/\tau_c}\right)$$

$$+\ln 4 = +\tau/\tau_c$$

$$\tau = (\ln 4)\tau_c = \boxed{1.39\tau_c}$$

→ how about half-life

$$\frac{Q}{2} = Q_0 e^{-\tau/\tau_c}$$

$$\tau_{1/2} = \boxed{0.693\tau_c}$$