

## Self Inductance

From Faraday's law

$$\mathcal{E} = -\frac{d\phi_B}{dt}$$

and  $\phi_B \propto B \propto I$  in a current loop.

$$\mathcal{E} \propto \frac{dI}{dt}$$

$$\mathcal{E} = -L \frac{dI}{dt}$$

a constant called "inductance"  
- depends on geometry of coil

In general with coil of  $N$  turns

$$\mathcal{E} = -N \frac{d\phi_B}{dt} = -L \frac{dI}{dt}$$

equations + integrating over time

$$N\phi_B = LI$$

$$L = \frac{N\phi_B}{I}$$

units: henrys  $1H = 1 \text{ V}\cdot\text{s}/\text{A}$

## RL Circuits

an 'inductor' (symbol) has large self-inductance  
- so it opposes changes in current in a circuit



when we close the switch,  
I increases ( $dI/dt > 0$ )  
 $\mathcal{E} = -L \frac{dI}{dt} < 0$   
 $\vec{E}$  back emf

the electric potential decreases when

so from a + b

From loop rule

$$\frac{\mathcal{E}}{R} - \frac{IR}{R} - \frac{L}{R} \frac{dI}{dt} = 0$$

if take  $x = IR - I$  then have

$$x + \frac{L}{R} \frac{dx}{dt} = 0$$

$$\int_{x_0}^x dx/x = -\left(\frac{R}{L}\right) \int_0^t dt$$

$$\ln(x/x_0) = -R/L t$$

$$x = x_0 e^{-Rt/L}$$

$$I = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$$


$$\tau = R/L \quad \text{time constant}$$

equilibrium value of the current

(1)

(2)

Ex 3.2.3:

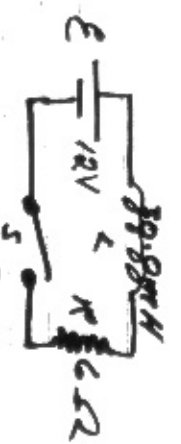


a) Time constant?

$$\tau = L/R = \frac{30 \times 10^{-3} \text{H}}{6 \Omega} = 5 \text{ms}$$

b) switch, 5 closed @  $t = 0$

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) = \frac{12 \text{V}}{6 \Omega} (1 - e^{-0.1}) = 0.6529 \text{A}$$

Ex 3.2.4

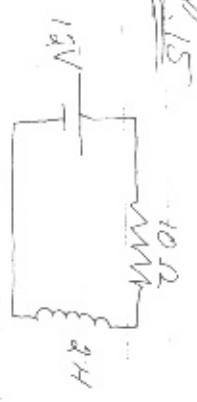

a) to reach 50% of final value

$$0.5 = \frac{I}{I_{\text{max}}} = 1 - e^{-Rt/L}$$

$$\ln 0.5 = -Rt/L \Rightarrow \ln 0.345 = -Rt/L \Rightarrow \boxed{0.345} = Rt/L = \tau/L$$

One can also use the log rule eg. to quantify the energy stored

$$I \mathcal{E} = I^2 R + L I \frac{dI}{dt}$$

$$\frac{dU}{dt} = LI \frac{dI}{dt} \quad (\text{rate energy stored})$$

$$\int dU = \int_0^I LI dI$$

$$\boxed{U = \frac{1}{2} LI^2}$$

total E. stored

c) DV across R + L

@  $t = 0, I = 0, \Delta V_R = 0$

@  $t = \tau, I = \frac{\mathcal{E}}{R} (1 - e^{-1})$   
 $\mathcal{E}_L \uparrow$  so  $\Delta V_R \downarrow$

$$3 = \Delta V_R + \mathcal{E}_L$$

130V/100V 415, p10

Ex 32.1

1304/11/09

L15, p12

Does all  $\epsilon$  stored at initially in inductor appear as internal  $\epsilon$  in R?

$$\frac{dU}{dt} = I^2 R = (I_0 e^{-Rt/L})^2 R$$

$$= I_0^2 R e^{-2Rt/L}$$

Solve for  $dU +$  inductor from  $t=0$  to  $t \rightarrow \infty$

$$U = \int_0^{\infty} I_0^2 R e^{-2Rt/L} dt$$

$$\frac{1}{2} I_0^2 (e^{-2Rt/L} - e^{-2Rt/L}) = I_0^2 R \int_0^{\infty} e^{-2Rt/L} dt$$

$$U = I_0^2 R \left( \frac{L}{2R} \right)$$

$$= \frac{1}{2} L I_0^2$$

(same as stored in inductor)


1304/11/09

L15, p1
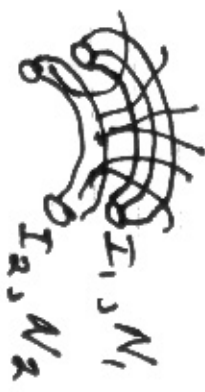
### Mutual Inductance

→ 2 adjacent coils

→ one has current,  $I$  which sets up magnetic field,  $\vec{B}$



If some field lines pass thru coil 2 which has  $N_2$  turns

→ call it  $\Phi_{12}$

define Mutual Inductance

$$M_{12} = \frac{N_2 \Phi_{12}}{I_1}$$

→ from Faraday's Law

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{12}}{dt} = -N_2 \frac{d}{dt} \left( \frac{M_{12} I_1}{N_2} \right)$$

like induced self  $\frac{dI}{dt}$

$= -L \frac{dI}{dt}$

proportional to rate of change of current

1309/1109

L16, P2

### LC Circuit

Total initial energy



$$U = \frac{Q^2}{2C} + \frac{1}{2}LI^2$$

Cap. Ind.

→ must remain constant in time  $\frac{dU}{dt} = 0$

$$\begin{aligned} \frac{dU}{dt} &= \frac{d}{dt} \left( \frac{Q^2}{2C} + \frac{1}{2}LI^2 \right) \\ &= \frac{Q}{C} \frac{dQ}{dt} + LI \frac{dI}{dt} = 0 \end{aligned}$$

but  $I = \frac{dQ}{dt}$ , so

$$\frac{Q}{C} \dot{Q} + LI \dot{Q} = 0$$

$$\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q$$

time-deriv of charge

similar to oscillations springs

$$\begin{aligned} \frac{d^2x}{dt^2} &= -\frac{k}{m} x = -\omega^2 x \\ x &= A \cos(\omega t + \phi) \end{aligned}$$

1309/1109

L16, P3

by analogy

$$Q = Q_{max} \cos(\omega t + \phi)$$

where  $\omega = \frac{1}{\sqrt{LC}}$  (natural frequency)

Since charge,  $Q$ , varies sinusoidally, so does  $I = \frac{dQ}{dt}$

$$I = -\omega Q_{max} \sin(\omega t + \phi)$$

→ dependent on initial conditions

→ current out of phase by  $90^\circ$  with charge

Total energy:

$$U = \frac{Q_{max}^2}{2C} \cos^2 \omega t + \frac{LI_{max}^2}{2} \sin^2 \omega t$$

→ constant sum

1302/1904

L16, p4

### RLC Circuit

- in LC + current oscillator  
as infinitesimal & constant
- add R to circuit  
-> deceleration of  
internal energy of  
resistor

$$\frac{dU}{dt} = -I^2 R$$

- so

$$L \frac{dI}{dt} + \frac{Q}{C} \frac{dQ}{dt} = -I^2 R$$

$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} + I^2 R = 0$$

like damped harmonic oscillator.  
when R small, damped

$$Q = Q_{max} e^{-\gamma t} \cos \omega_d t$$



$$\text{where } \omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$