


Alternating Currents (AC)

(1)

Consider circuit where voltage supplied varies sinusoidally w/ time

$$V = V_m \sin \omega t$$

→ voltage amplitude

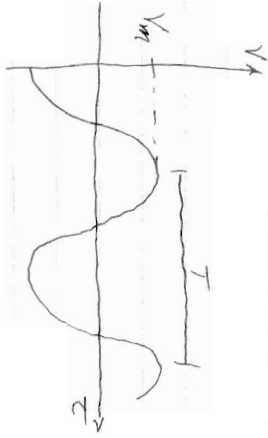

$$\omega = 2\pi f = \frac{2\pi}{T}$$

frequency in cycles/sec. (Hz.)

period

Each electrical outlet in US has AC voltage @ $f = 60\text{Hz}$

Resistive Circuit

(2)

AC voltage (emf)

$$V = V_m \sin \omega t$$

Use Kirchoff's loop rule:



$$V - V_R = 0$$

(@ any time, t)


$$\Rightarrow V_R = V_m \sin \omega t \quad (V = V_m \sin \omega t \text{ here})$$

↳ instantaneous voltage across resistor

Since $R = V/I$

$$i_R = \frac{V}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t$$

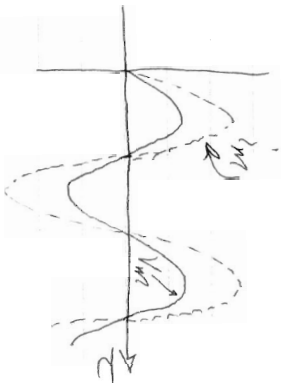
↳ " in phase with voltage (maximum current)



Phasor Diagrams

Amplitude (i_m, V_m) \Rightarrow length
 phase ($\omega t, \phi$) \Rightarrow angle

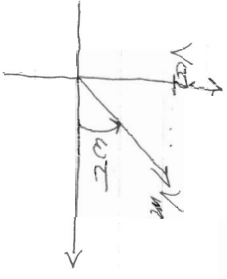So a 'phasor' is a vector in a coordinate system whose vertical axis is the instantaneous value of the quantity




Project onto
 Y-axis to get
 $V(t), V(t), \dots$

We can use phasors to consider phase relationships between i + V 's

- reduced to vector arithmetic

For a single R in a circuit


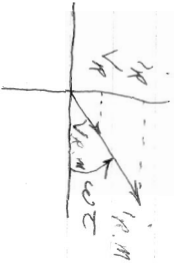


3

Power Delivered to a Resistor

I doesn't matter if have positive or negative current since $P = I^2 R$ (instantaneous current)

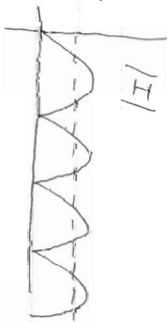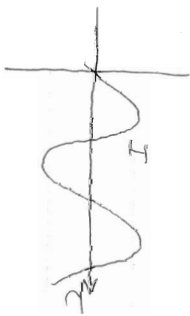- but average I is different than DC case



Average $\neq I_{max}$

We want the 'root-mean-square' of the current

$$I_{rms} = \sqrt{\langle I^2 \rangle} = \sqrt{\frac{\sum I^2}{N}}$$

- Since I^2 of sine wave, the average of sine wave is $\frac{1}{2}$

$$\langle I^2 \rangle = \frac{1}{2} I_m^2 \Rightarrow I_{rms} = \frac{I_m}{\sqrt{2}} = 0.7 I_m$$

(false $V_{rms} = \frac{V_m}{\sqrt{2}}$)

Average Power

$$P_{avg} = I_{rms}^2 R$$

4