

P26.1 (a) $Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 4.80 \times 10^{-5} \text{ C} = \boxed{48.0 \mu\text{C}}$

(b) $Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(1.50 \text{ V}) = 6.00 \times 10^{-6} \text{ C} = \boxed{6.00 \mu\text{C}}$

P26.2 (a) $C = \frac{Q}{\Delta V} = \frac{10.0 \times 10^{-6} \text{ C}}{10.0 \text{ V}} = 1.00 \times 10^{-6} \text{ F} = \boxed{1.00 \mu\text{F}}$

(b) $\Delta V = \frac{Q}{C} = \frac{100 \times 10^{-6} \text{ C}}{1.00 \times 10^{-6} \text{ F}} = \boxed{100 \text{ V}}$

P26.7 (a) $\Delta V = Ed$

$$E = \frac{20.0 \text{ V}}{1.80 \times 10^{-3} \text{ m}} = \boxed{11.1 \text{ kV/m}}$$

(b) $E = \frac{\sigma}{\epsilon_0}$

$$\sigma = (1.11 \times 10^4 \text{ N/C})(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2) = \boxed{98.3 \text{ nC/m}^2}$$

(c) $C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(7.60 \text{ cm}^2)(1.00 \text{ m}/100 \text{ cm})^2}{1.80 \times 10^{-3} \text{ m}} = \boxed{3.74 \text{ pF}}$

(d) $\Delta V = \frac{Q}{C}$

$$Q = (20.0 \text{ V})(3.74 \times 10^{-12} \text{ F}) = \boxed{74.7 \text{ pC}}$$

P26.16 (a) Capacitors in parallel add. Thus, the equivalent capacitor has a value of

$$C_{\text{eq}} = C_1 + C_2 = 5.00 \mu\text{F} + 12.0 \mu\text{F} = \boxed{17.0 \mu\text{F}}$$

(b) The potential difference across each branch is the same and equal to the voltage of the battery.

$$\Delta V = \boxed{9.00 \text{ V}}$$

(c) $Q_5 = C\Delta V = (5.00 \mu\text{F})(9.00 \text{ V}) = \boxed{45.0 \mu\text{C}}$

and $Q_{12} = C\Delta V = (12.0 \mu\text{F})(9.00 \text{ V}) = \boxed{108 \mu\text{C}}$

P26.17 (a) In series capacitors add as

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{5.00 \mu\text{F}} + \frac{1}{12.0 \mu\text{F}}$$

and

$$C_{eq} = \boxed{3.53 \mu\text{F}}$$

(c) The charge on the equivalent capacitor is $Q_{eq} = C_{eq} \Delta V = (3.53 \mu\text{F})(9.00 \text{ V}) = 31.8 \mu\text{C}$.

Each of the series capacitors has this same charge on it.

So

$$Q_1 = Q_2 = \boxed{31.8 \mu\text{C}}$$

(b) The potential difference across each is

$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{31.8 \mu\text{C}}{5.00 \mu\text{F}} = \boxed{6.35 \text{ V}}$$

and

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{31.8 \mu\text{C}}{12.0 \mu\text{F}} = \boxed{2.65 \text{ V}}$$

P26.21 (a) $\frac{1}{C_s} = \frac{1}{15.0} + \frac{1}{3.00}$

$$C_s = 2.50 \mu\text{F}$$

$$C_p = 2.50 + 6.00 = 8.50 \mu\text{F}$$

$$C_{eq} = \left(\frac{1}{8.50 \mu\text{F}} + \frac{1}{20.0 \mu\text{F}} \right)^{-1} = \boxed{5.96 \mu\text{F}}$$

(b) $Q = C \Delta V = (5.96 \mu\text{F})(15.0 \text{ V}) = \boxed{89.5 \mu\text{C}}$ on $20.0 \mu\text{F}$

$$\Delta V = \frac{Q}{C} = \frac{89.5 \mu\text{C}}{20.0 \mu\text{F}} = 4.47 \text{ V}$$

$$15.0 - 4.47 = 10.53 \text{ V}$$

$Q = C \Delta V = (6.00 \mu\text{F})(10.53 \text{ V}) = \boxed{63.2 \mu\text{C}}$ on $6.00 \mu\text{F}$

$89.5 - 63.2 = \boxed{26.3 \mu\text{C}}$ on $15.0 \mu\text{F}$ and $3.00 \mu\text{F}$

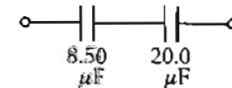
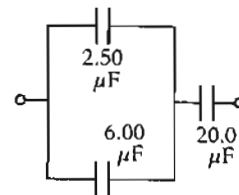
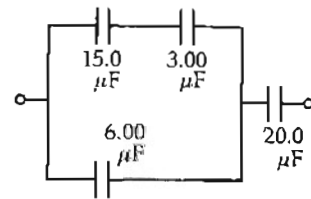


FIG. P26.21

P26.23 $C = \frac{Q}{\Delta V}$ so

and

$$Q = \boxed{120 \mu\text{C}}$$

$$Q_1 = 120 \mu\text{C} - Q_2$$

and

$$\Delta V = \frac{Q}{C}$$

$$\frac{120 - Q_2}{C_1} = \frac{Q_2}{C_2}$$

or

$$\frac{120 - Q_2}{6.00} = \frac{Q_2}{3.00}$$

$$(3.00)(120 - Q_2) = (6.00)Q_2$$

$$Q_2 = \frac{360}{9.00} = \boxed{40.0 \mu\text{C}}$$

$$Q_1 = 120 \mu\text{C} - 40.0 \mu\text{C} = \boxed{80.0 \mu\text{C}}$$

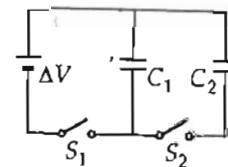


FIG. P26.23

P26.34 Use $U = \frac{1}{2} \frac{Q^2}{C}$ and $C = \frac{\epsilon_0 A}{d}$.

If $d_2 = 2d_1$, $C_2 = \frac{1}{2} C_1$. Therefore, the **stored energy doubles**.