

P28.1 (a)  $\mathcal{P} = \frac{(\Delta V)^2}{R}$

becomes  $20.0 \text{ W} = \frac{(11.6 \text{ V})^2}{R}$

so  $R = \boxed{6.73 \Omega}$ .

(b)  $\Delta V = IR$

so  $11.6 \text{ V} = I(6.73 \Omega)$

and  $I = 1.72 \text{ A}$

$\mathcal{E} = IR + Ir$

so  $15.0 \text{ V} = 11.6 \text{ V} + (1.72 \text{ A})r$

$r = \boxed{1.97 \Omega}$ .

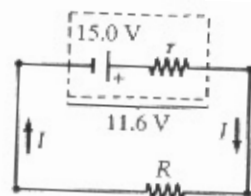


FIG. P28.1

P28.6 (a)  $R_p = \frac{1}{(1/7.00 \Omega) + (1/10.0 \Omega)} = 4.12 \Omega$

$R_s = R_1 + R_2 + R_3 = 4.00 + 4.12 + 9.00 = \boxed{17.1 \Omega}$

(b)  $\Delta V = IR$

$34.0 \text{ V} = I(17.1 \Omega)$

$I = \boxed{1.99 \text{ A}}$  for  $4.00 \Omega$ ,  $9.00 \Omega$  resistors.

Applying  $\Delta V = IR$ ,  $(1.99 \text{ A})(4.12 \Omega) = 8.18 \text{ V}$

$8.18 \text{ V} = I(7.00 \Omega)$

so  $I = \boxed{1.17 \text{ A}}$  for  $7.00 \Omega$  resistor

$8.18 \text{ V} = I(10.0 \Omega)$

so  $I = \boxed{0.818 \text{ A}}$  for  $10.0 \Omega$  resistor.

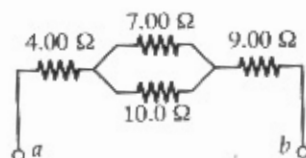


FIG. P28.6

P28.15  $R_p = \left( \frac{1}{3.00} + \frac{1}{1.00} \right)^{-1} = 0.750 \Omega$

$R_s = (2.00 + 0.750 + 4.00) \Omega = 6.75 \Omega$

$I_{\text{battery}} = \frac{\Delta V}{R_s} = \frac{18.0 \text{ V}}{6.75 \Omega} = 2.67 \text{ A}$

$\mathcal{P} = I^2 R$ :  $\mathcal{P}_2 = (2.67 \text{ A})^2 (2.00 \Omega)$

$\mathcal{P}_2 = \boxed{14.2 \text{ W}}$  in  $2.00 \Omega$

$\mathcal{P}_4 = (2.67 \text{ A})^2 (4.00 \Omega) = \boxed{28.4 \text{ W}}$  in  $4.00 \Omega$

$\Delta V_2 = (2.67 \text{ A})(2.00 \Omega) = 5.33 \text{ V}$ ,

$\Delta V_4 = (2.67 \text{ A})(4.00 \Omega) = 10.67 \text{ V}$

$\Delta V_p = 18.0 \text{ V} - \Delta V_2 - \Delta V_4 = 2.00 \text{ V} (= \Delta V_3 = \Delta V_1)$

$\mathcal{P}_3 = \frac{(\Delta V_3)^2}{R_3} = \frac{(2.00 \text{ V})^2}{3.00 \Omega} = \boxed{1.33 \text{ W}}$  in  $3.00 \Omega$

$\mathcal{P}_1 = \frac{(\Delta V_1)^2}{R_1} = \frac{(2.00 \text{ V})^2}{1.00 \Omega} = \boxed{4.00 \text{ W}}$  in  $1.00 \Omega$

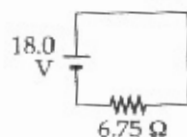
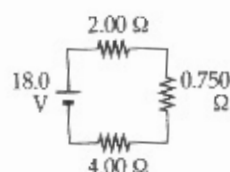
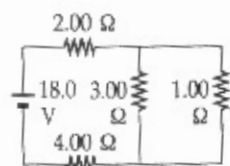


FIG. P28.15

**P28.21** We name currents  $I_1$ ,  $I_2$ , and  $I_3$  as shown.

From Kirchhoff's current rule,  $I_3 = I_1 + I_2$ .

Applying Kirchhoff's voltage rule to the loop containing  $I_2$  and  $I_3$ ,

$$12.0 \text{ V} - (4.00)I_3 - (6.00)I_2 - 4.00 \text{ V} = 0$$

$$8.00 = (4.00)I_3 + (6.00)I_2$$

Applying Kirchhoff's voltage rule to the loop containing  $I_1$  and  $I_2$ ,

$$-(6.00)I_2 - 4.00 \text{ V} + (8.00)I_1 = 0 \quad (8.00)I_1 = 4.00 + (6.00)I_2.$$

Solving the above linear system, we proceed to the pair of simultaneous equations:


$$\begin{cases} 8 = 4I_1 + 4I_2 + 6I_2 \\ 8I_1 = 4 + 6I_2 \end{cases} \quad \text{or} \quad \begin{cases} 8 = 4I_1 + 10I_2 \\ I_2 = 1.33I_1 - 0.667 \end{cases}$$

and to the single equation  $8 = 4I_1 + 13.3I_1 - 6.67$

$$I_1 = \frac{14.7 \text{ V}}{17.3 \Omega} = 0.846 \text{ A}. \quad \text{Then} \quad I_2 = 1.33(0.846 \text{ A}) - 0.667$$

and  $I_3 = I_1 + I_2$  give  $I_1 = 846 \text{ mA}$ ,  $I_2 = 462 \text{ mA}$ ,  $I_3 = 1.31 \text{ A}$ .

All currents are in the directions indicated by the arrows in the circuit diagram.

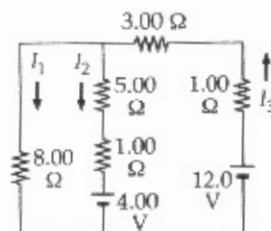

**FIG. P28.21**

**P28.25** Label the currents in the branches as shown in the first figure. Reduce the circuit by combining the two parallel resistors as shown in the second figure.

Apply Kirchhoff's loop rule to both loops in Figure (b) to obtain:

$$(2.71R)I_1 + (1.71R)I_2 = 250$$

and  $(1.71R)I_1 + (3.71R)I_2 = 500$ .

With  $R = 1000 \Omega$ , simultaneous solution of these equations yields:

$$I_1 = 10.0 \text{ mA}$$

and  $I_2 = 130.0 \text{ mA}$ .


From Figure (b),  $V_c - V_a = (I_1 + I_2)(1.71R) = 240 \text{ V}$ .

Thus, from Figure (a),  $I_4 = \frac{V_c - V_a}{4R} = \frac{240 \text{ V}}{4000 \Omega} = 60.0 \text{ mA}$ .


Finally, applying Kirchhoff's point rule at point  $a$  in Figure (a) gives:

$$I = I_4 - I_1 = 60.0 \text{ mA} - 10.0 \text{ mA} = +50.0 \text{ mA},$$

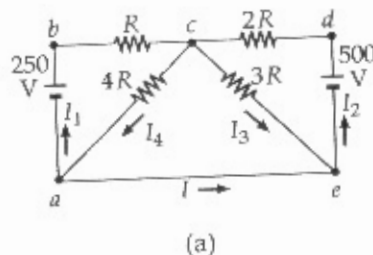or  $I = 50.0 \text{ mA}$  from point  $a$  to point  $e$ .



(a)

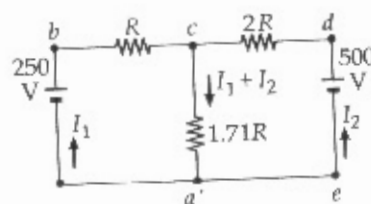

(b)

**FIG. P28.25**

**P28.29** We name the currents  $I_1$ ,  $I_2$ , and  $I_3$  as shown.

(a)  $I_1 = I_2 + I_3$

Counterclockwise around the top loop,  
 $12.0 \text{ V} - (2.00 \Omega)I_3 - (4.00 \Omega)I_1 = 0$ .


Traversing the bottom loop,

$$8.00 \text{ V} - (6.00 \Omega)I_2 + (2.00 \Omega)I_3 = 0$$

$$I_1 = 3.00 - \frac{1}{2}I_3, I_2 = \frac{4}{3} + \frac{1}{3}I_3, \text{ and } \boxed{I_3 = 909 \text{ mA}}$$

(b)  $V_a - (0.909 \text{ A})(2.00 \Omega) = V_b$

$$V_b - V_a = \boxed{-1.82 \text{ V}}$$

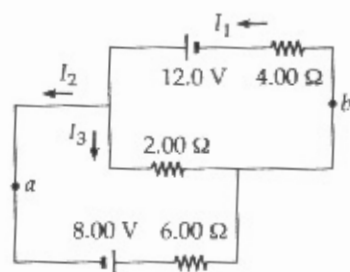


**FIG. P28.29**

**P28.31** (a)  $RC = (1.00 \times 10^6 \Omega)(5.00 \times 10^{-6} \text{ F}) = \boxed{5.00 \text{ s}}$

(b)  $Q = C\varepsilon = (5.00 \times 10^{-6} \text{ C})(30.0 \text{ V}) = \boxed{150 \mu\text{C}}$

(c)  $I(t) = \frac{\varepsilon}{R} e^{-t/RC} = \left( \frac{30.0}{1.00 \times 10^6} \right) \exp \left[ \frac{-10.0}{(1.00 \times 10^6)(5.00 \times 10^{-6})} \right] = \boxed{4.06 \mu\text{A}}$

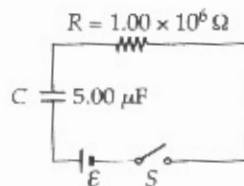

**FIG. P28.31**

**P28.33**  $U = \frac{1}{2}C(\Delta V)^2$  and  $\Delta V = \frac{Q}{C}$ .

Therefore,  $U = \frac{Q^2}{2C}$  and when the charge decreases to half its original value, the stored energy is one-

quarter its original value:  $\boxed{U_f = \frac{1}{4}U_0}$ .

**P28.36** (a)  $\tau = RC = (1.50 \times 10^5 \Omega)(10.0 \times 10^{-6} \text{ F}) = \boxed{1.50 \text{ s}}$

(b)  $\tau = (1.00 \times 10^5 \Omega)(10.0 \times 10^{-6} \text{ F}) = \boxed{1.00 \text{ s}}$

(c) The battery carries current

$$\frac{10.0 \text{ V}}{50.0 \times 10^3 \Omega} = 200 \mu\text{A}.$$

The 100 kΩ carries current of magnitude

$$I = I_0 e^{-t/RC} = \left( \frac{10.0 \text{ V}}{100 \times 10^3 \Omega} \right) e^{-t/1.00 \text{ s}}.$$

So the switch carries downward current

$$\boxed{200 \mu\text{A} + (100 \mu\text{A})e^{-t/1.00 \text{ s}}}$$