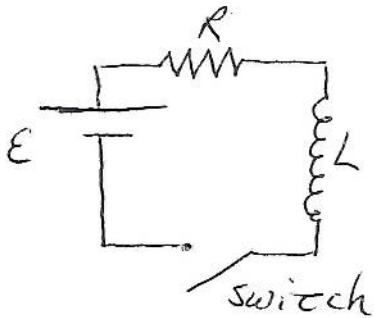


- 1) A circuit has a 12 V emf, a 10 ohm resistor and a 0.1 H inductor, as shown. When the switch is closed, how long will it take for the current thru the resistor to reach 99% of its peak value? [10 pts]



$$I = I_{\max} (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R} = \frac{0.1}{10} = 0.01$$

$$0.99 I_{\max} = I_{\max} (1 - e^{-t/\tau})$$

$$0.99 = 1 - e^{-t/0.01}$$

$$t = -0.01 \times \ln(0.01)$$

$$t = 0.046 \text{ s}$$

- 2) What is the natural frequency of a circuit containing only a 5 mF charged capacitor and a 10 mH inductor? [6 pts]

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(10 \times 10^{-3}) \cdot (5 \times 10^{-3})}}$$

$$\omega = 141.42 \text{ rad/s}$$