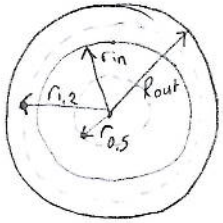


[Note: Please choose one of the two 12 pt problems, and three of the four 10 pt problems.]

1) A thick conducting cylinder has a uniform total current of 10 A, an inner radius of 1 cm and an outer radius of 1.5 cm. What is the magnetic field at a radius of 1.2 cm? What is it at 0.5 cm? Draw each Ampere's path and explain your answers. [12 pts]



$$\oint \mathbf{B} \cdot d\mathbf{s} = \mu_0 I_{in}$$

$$a) \quad B \cdot 2\pi r_{1,2} = \mu_0 \cdot \frac{I}{\pi (R_{out}^2 - R_{in}^2)} \cdot \pi (r_{1,2}^2 - R_{in}^2) \Rightarrow B = \frac{\mu_0 I}{2\pi r_{1,2}} \cdot \left(\frac{r_{1,2}^2 - R_{in}^2}{R_{out}^2 - R_{in}^2} \right)$$

$$B = \frac{(4\pi \times 10^{-7}) \cdot 10}{2\pi (0.012)} \cdot \left(\frac{0.012^2 - 0.01^2}{0.015^2 - 0.01^2} \right) \Rightarrow B = 5.87 \times 10^{-5} T$$

$$b) \quad I_{in} = 0 \Rightarrow B = 0$$

2) An emf of 12 V is placed across a 5 ohm resistor. What is the power consumption of the resistor? What current flows thru the circuit? [10 pts]

$$P = \frac{V^2}{R} = \frac{12^2}{5} \Rightarrow P = 28.8 W$$

$$I = \frac{V}{R} = \frac{12}{5} \Rightarrow I = 2.4 A$$

3) A capacitor is fully charged to a capacitance of 5×10^{-6} F. This is placed in a series circuit with a 5 ohm resistor and a switch, as shown. The switch is closed at $t=0$ s. At what time will the current in the circuit be 1% of its initial value? [10 pts]



$$I(t) = I_0 e^{-t/RC}$$

$$0.01 I_0 = I_0 e^{-t/RC}$$

$$0.01 = e^{-t/RC}$$

$$t = -RC \ln(0.01)$$

$$t = -5 \cdot (5 \times 10^{-6}) \cdot \ln(0.01)$$

$$t = 1.15 \times 10^{-4} s$$

4) A pair of conducting square plates are spaced 10 microns (10^{-6} m) apart to form a capacitor. If the plates are 200 microns long on a side, what is the resulting capacitor's capacitance? [10 pts]

$$C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12}) (200 \times 10^{-6})^2}{10 \times 10^{-6}}$$

$$C = 3.54 \times 10^{-14} \text{ F}$$



5) A solenoid has a current of 1 A. There are 10^4 turns over the solenoid's 1m length. What is the magnetic field inside the solenoid? A semicircular segment of wire is placed in the magnetic field so that it is aligned along the axis of the solenoid as shown. If there is a current of 5 mA in the wire and the semicircle's radius is 5 cm, what force is exerted on the wire? If a wire joins the ends of the semicircle, then what is the net force? [12 pts]

$$B = \mu_0 \frac{N}{L} I = (4\pi \times 10^{-7}) \cdot \frac{10^4}{1} \cdot 1$$

$$B = 1.26 \times 10^{-2} \text{ T}$$

$$F_B = I L \times B = I L_{\perp} B = I \cdot 2R \cdot B$$

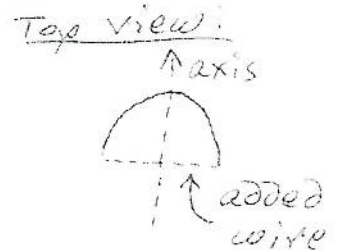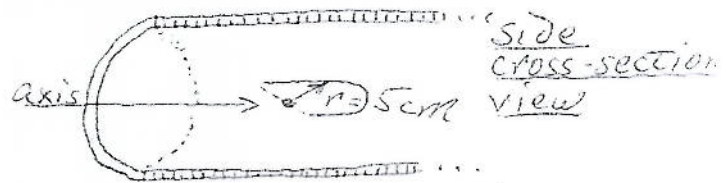
$$= (5 \times 10^{-3}) \cdot (2 \times 0.05) \cdot (1.26 \times 10^{-2}) \Rightarrow F_B = 6.3 \times 10^{-6} \text{ N}$$



If a wire joins the ends of semicircle:

$F_{\text{net}} = 0$ since the wire becomes a closed loop.

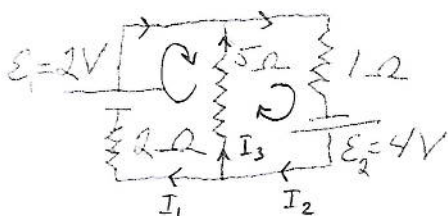6) The circuit below has two sources of emf and three resistors. What are the currents thru the 1 ohm, 2 ohm and 5 ohm resistors? [10 pts]



$$\left. \begin{aligned} I_1 + I_3 &= I_2 \\ \mathcal{E}_1 + 5I_3 - 2I_1 &= 0 \\ \mathcal{E}_2 - 5I_3 - 1I_2 &= 0 \end{aligned} \right\} \begin{array}{l} 3 \text{ equations} \\ 3 \text{ unknowns} \end{array}$$

When these three eqns are solved:

$$I_1 (\text{on } 2\Omega) = 1.88 \text{ A} , \quad I_2 (\text{on } 1\Omega) = 2.24 \text{ A} , \quad I_3 (\text{on } 5\Omega) = 0.35 \text{ A}$$