

P32.3 $\epsilon_{\text{back}} = -\mathcal{E} = L \frac{di}{dt} = L \frac{d}{dt}(I_{\text{max}} \sin \omega t) = L \omega I_{\text{max}} \cos \omega t = (10.0 \times 10^{-3})(120\pi)(5.00) \cos \omega t$
 $\epsilon_{\text{back}} = (6.00\pi) \cos(120\pi t) = \boxed{(18.8 \text{ V}) \cos(377t)}$

P32.12 $L = \frac{N\Phi_B}{I} = \frac{NBA}{I} = \frac{NA}{I} \frac{\mu_0 NI}{2\pi R} = \boxed{\frac{\mu_0 N^2 A}{2\pi R}}$



FIG. P32.12

P32.14 (a) At time t ,

$$i(t) = \frac{\mathcal{E}(1 - e^{-t/\tau})}{R}$$

where

$$\tau = \frac{L}{R} = 0.200 \text{ s}$$

After a long time,

$$i_{\text{max}} = \frac{\mathcal{E}(1 - e^{-\infty})}{R} = \frac{\mathcal{E}}{R}$$

At $i(t) = 0.500 i_{\text{max}}$

$$(0.500) \frac{\mathcal{E}}{R} = \frac{\mathcal{E}(1 - e^{-t/(0.200 \text{ s})})}{R}$$

so

$$0.500 = 1 - e^{-t/(0.200 \text{ s})}$$

Isolating the constants on the right,

$$\ln(e^{-t/(0.200 \text{ s})}) = \ln(0.500)$$

and solving for t ,

$$-\frac{t}{0.200 \text{ s}} = -0.693$$

or

$$t = \boxed{0.139 \text{ s}}$$

(b) Similarly, to reach 90% of i_{max} ,

$$0.900 = 1 - e^{-t/\tau}$$

and

$$t = -\tau \ln(1 - 0.900)$$

Thus,

$$t = -(0.200 \text{ s}) \ln(0.100) = \boxed{0.461 \text{ s}}$$

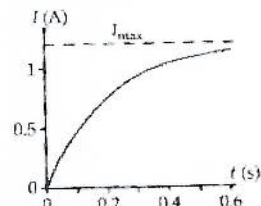


FIG. P32.15

P32.25 $L = \mu_0 \frac{N^2 A}{\ell} = \mu_0 \frac{(68.0)^2 [\pi(0.600 \times 10^{-2})^2]}{0.0800} = 8.21 \mu\text{H}$

$$U = \frac{1}{2} L i^2 = \frac{1}{2} (8.21 \times 10^{-6} \text{ H})(0.770 \text{ A})^2 = \boxed{2.44 \mu\text{J}}$$

P32.39

When the switch has been closed for a long time, battery, resistor, and coil carry constant current $i_{\text{max}} = \frac{\mathcal{E}}{R}$. When the switch is opened,

current in battery and resistor drops to zero, but the coil carries this same current for a moment as oscillations begin in the LC loop.

We interpret the problem to mean that the voltage amplitude of these oscillations is ΔV , in $\frac{1}{2} C(\Delta V)^2 = \frac{1}{2} L i_{\text{max}}^2$.

$$\text{Then, } L = \frac{C(\Delta V)^2}{i_{\text{max}}^2} = \frac{C(\Delta V)^2 R^2}{\mathcal{E}^2} = \frac{(0.500 \times 10^{-6} \text{ F})(150 \text{ V})^2 (250 \Omega)^2}{(50.0 \text{ V})^2} = \boxed{0.281 \text{ H}}$$

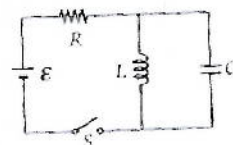


FIG. P32.50

*P32.48 (a)

Let Q represent the magnitude of the opposite charges on the plates of a parallel plate capacitor, the two plates having area A and separation d . The negative plate creates electric field $E = \frac{Q}{2\epsilon_0 A}$ toward itself. It exerts on the positive plate force $F = \frac{Q^2}{2\epsilon_0 A}$ toward the negative plate. The total field between the plates is $\frac{Q}{\epsilon_0 A}$. The energy density is $u_E = \frac{1}{2}\epsilon_0 E^2 = \frac{1}{2}\epsilon_0 \frac{Q^2}{\epsilon_0^2 A^2} = \frac{Q^2}{2\epsilon_0 A^2}$. Modeling this as a negative or inward pressure, we have for the force on one plate $F = PA = \frac{Q^2}{2\epsilon_0 A^2}$, in agreement with our first analysis.

(b) The lower of the two current sheets shown creates above it magnetic field $\mathbf{B} = \frac{\mu_0 J_s}{2}(-\hat{k})$. Let ℓ and w represent the length and width of each sheet. The upper sheet carries current $J_s w$ and feels force

$$\mathbf{F} = I\ell \times \mathbf{B} = J_s w \ell \frac{\mu_0 J_s}{2} \hat{i} \times (-\hat{k}) = \frac{\mu_0 w \ell J_s^2}{2} \hat{j}.$$

The force per area is $P = \frac{F}{\ell w} = \frac{\mu_0 J_s^2}{2}$.

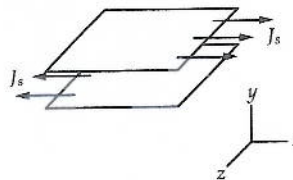


FIG. P32.59(b)

(c) Between the two sheets the total magnetic field is $\frac{\mu_0 J_s}{2}(-\hat{k}) + \frac{\mu_0 J_s}{2}(-\hat{k}) = \mu_0 J_s \hat{k}$, with magnitude $B = \mu_0 J_s$. Outside the space they enclose, the fields of the separate sheets are in opposite directions and add to zero.

(d) $u_B = \frac{1}{2\mu_0} B^2 = \frac{\mu_0^2 J_s^2}{2\mu_0} = \frac{\mu_0 J_s^2}{2}$

(e) This energy density agrees with the magnetic pressure found in part (b).

P32.51

$$\frac{1}{2} \frac{Q^2}{C} = \frac{1}{2C} \left(\frac{Q}{2}\right)^2 + \frac{1}{2} LI^2$$

so $I = \sqrt{\frac{3Q^2}{4CL}}$.

The flux through each turn of the coil is

$$\Phi_B = \frac{LI}{N} = \frac{Q}{2N} \sqrt{\frac{3L}{C}}$$

where N is the number of turns.

P32.76

$$\mathcal{P} = I\Delta V \quad I = \frac{\mathcal{P}}{\Delta V} = \frac{1.00 \times 10^9 \text{ W}}{200 \times 10^3 \text{ V}} = 5.00 \times 10^3 \text{ A}$$

From Ampere's law, $B(2\pi r) = \mu_0 I_{\text{enclosed}}$ or $B = \frac{\mu_0 I_{\text{enclosed}}}{2\pi r}$.

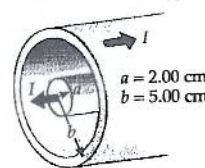


FIG. P32.73

(a) At $r = a = 0.0200 \text{ m}$, $I_{\text{enclosed}} = 5.00 \times 10^3 \text{ A}$

and $B = \frac{(4\pi \times 10^{-7} \text{ T}\cdot\text{m/A})(5.00 \times 10^3 \text{ A})}{2\pi(0.0200 \text{ m})} = 0.0500 \text{ T} = \boxed{50.0 \text{ mT}}$.

(b) At $r = b = 0.0500 \text{ m}$, $I_{\text{enclosed}} = I = 5.00 \times 10^3 \text{ A}$

and $B = \frac{(4\pi \times 10^{-7} \text{ T}\cdot\text{m/A})(5.00 \times 10^3 \text{ A})}{2\pi(0.0500 \text{ m})} = 0.0200 \text{ T} = \boxed{20.0 \text{ mT}}$.

(c) $U = \int u dV = \int_a^b \frac{[B(r)]^2 (2\pi r \ell dr)}{2\mu_0} = \frac{\mu_0 I^2 \ell}{4\pi} \int_a^b \frac{dr}{r} = \frac{\mu_0 I^2 \ell}{4\pi} \ln\left(\frac{b}{a}\right)$

$$U = \frac{(4\pi \times 10^{-7} \text{ T}\cdot\text{m/A})(5.00 \times 10^3 \text{ A})^2 (1000 \times 10^3 \text{ m})}{4\pi} \ln\left(\frac{5.00 \text{ cm}}{2.00 \text{ cm}}\right) = 2.29 \times 10^6 \text{ J} = \boxed{2.29 \text{ MJ}}$$

(d) The magnetic field created by the inner conductor exerts a force of repulsion on the current in the outer sheath. The strength of this field, from part (b), is 20.0 mT. Consider a small rectangular section of the outer cylinder of length ℓ and width w .

It carries a current of $(5.00 \times 10^3 \text{ A}) \left(\frac{w}{2\pi(0.0500 \text{ m})}\right)$

and experiences an outward force

$$F = I\ell B \sin\theta = \frac{(5.00 \times 10^3 \text{ A})w}{2\pi(0.0500 \text{ m})} \ell (20.0 \times 10^{-3} \text{ T}) \sin 90.0^\circ.$$

The pressure on it is $P = \frac{F}{A} = \frac{F}{w\ell} = \frac{(5.00 \times 10^3 \text{ A})(20.0 \times 10^{-3} \text{ T})}{2\pi(0.0500 \text{ m})} = \boxed{318 \text{ Pa}}$.