

P26.1 (a) $Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 4.80 \times 10^{-5} \text{ C} = \boxed{48.0 \mu\text{C}}$

(b) $Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(1.50 \text{ V}) = 6.00 \times 10^{-6} \text{ C} = \boxed{6.00 \mu\text{C}}$

P26.2 (a) $C = \frac{Q}{\Delta V} = \frac{10.0 \times 10^{-6} \text{ C}}{10.0 \text{ V}} = 1.00 \times 10^{-6} \text{ F} = \boxed{1.00 \mu\text{F}}$

(b) $\Delta V = \frac{Q}{C} = \frac{100 \times 10^{-6} \text{ C}}{1.00 \times 10^{-6} \text{ F}} = \boxed{100 \text{ V}}$

P26.5 (a) $\Delta V = Ed$

$$E = \frac{20.0 \text{ V}}{1.80 \times 10^{-3} \text{ m}} = \boxed{11.1 \text{ kV/m}}$$

(b) $E = \frac{\sigma}{\epsilon_0}$

$$\sigma = (1.11 \times 10^4 \text{ N/C})(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2) = \boxed{98.3 \text{ nC/m}^2}$$

(c) $C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(7.60 \text{ cm}^2)(1.00 \text{ m}/100 \text{ cm})^2}{1.80 \times 10^{-3} \text{ m}} = \boxed{3.74 \text{ pF}}$

(d) $\Delta V = \frac{Q}{C}$

$$Q = (20.0 \text{ V})(3.74 \times 10^{-12} \text{ F}) = \boxed{74.7 \text{ pC}}$$

P26.10 (a) Capacitors in parallel add. Thus, the equivalent capacitor has a value of

$$C_{\text{eq}} = C_1 + C_2 = 5.00 \mu\text{F} + 12.0 \mu\text{F} = \boxed{17.0 \mu\text{F}}$$

(b) The potential difference across each branch is the same and equal to the voltage of the battery.

$$\Delta V = \boxed{9.00 \text{ V}}$$

(c) $Q_5 = C\Delta V = (5.00 \mu\text{F})(9.00 \text{ V}) = \boxed{45.0 \mu\text{C}}$

and $Q_{12} = C\Delta V = (12.0 \mu\text{F})(9.00 \text{ V}) = \boxed{108 \mu\text{C}}$

P26.13

(a) In series capacitors add as

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{5.00 \mu F} + \frac{1}{12.0 \mu F}$$

and

$$C_{eq} = \boxed{3.53 \mu F}$$

(c) The charge on the equivalent capacitor is

$$Q_{eq} = C_{eq} \Delta V = (3.53 \mu F)(9.00 \text{ V}) = 31.8 \mu C$$

Each of the series capacitors has this same charge on it.

So

$$Q_1 = Q_2 = \boxed{31.8 \mu C}$$

(b) The potential difference across each is

$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{31.8 \mu C}{5.00 \mu F} = \boxed{6.35 \text{ V}}$$

and

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{31.8 \mu C}{12.0 \mu F} = \boxed{2.65 \text{ V}}$$

P26.17

(a) $\frac{1}{C_s} = \frac{1}{15.0} + \frac{1}{3.00}$

$$C_s = 2.50 \mu F$$

$$C_p = 2.50 + 6.00 = 8.50 \mu F$$

$$C_{eq} = \left(\frac{1}{8.50 \mu F} + \frac{1}{20.0 \mu F} \right)^{-1} = \boxed{5.96 \mu F}$$

(b) $Q = C \Delta V = (5.96 \mu F)(15.0 \text{ V}) = \boxed{89.5 \mu C}$ on $20.0 \mu F$

$$\Delta V = \frac{Q}{C} = \frac{89.5 \mu C}{20.0 \mu F} = 4.47 \text{ V}$$

$$15.0 - 4.47 = 10.53 \text{ V}$$

$Q = C \Delta V = (6.00 \mu F)(10.53 \text{ V}) = \boxed{63.2 \mu C}$ on $6.00 \mu F$

$89.5 - 63.2 = \boxed{26.3 \mu C}$ on $15.0 \mu F$ and $3.00 \mu F$

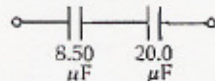
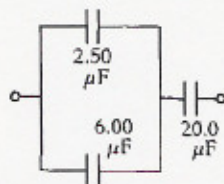
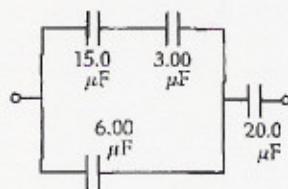


FIG. P26.21

P26.19

$C = \frac{Q}{\Delta V}$ so

$$6.00 \times 10^{-6} = \frac{Q}{20.0}$$

and

$$Q = \boxed{120 \mu C}$$

$$Q_1 = 120 \mu C - Q_2$$

and

$$\Delta V = \frac{Q}{C}$$

$$\frac{120 - Q_2}{C_1} = \frac{Q_2}{C_2}$$

or

$$\frac{120 - Q_2}{6.00} = \frac{Q_2}{3.00}$$

$$(3.00)(120 - Q_2) = (6.00)Q_2$$

$$Q_2 = \frac{360}{9.00} = \boxed{40.0 \mu C}$$

$$Q_1 = 120 \mu C - 40.0 \mu C = \boxed{80.0 \mu C}$$


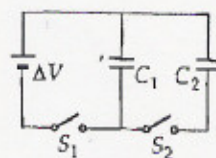


FIG. P26.23


P26.18

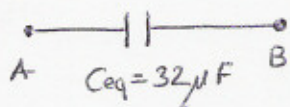

$$C_{eq} = 32 \mu F$$

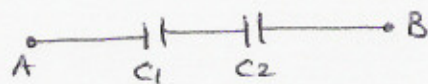a) $C_1 = 34.8 \mu F$

$C_1 > C_{eq} \Rightarrow$ The circuit should be series




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{32} = \frac{1}{34.8} + \frac{1}{C_2}$$

$$\Rightarrow \boxed{C_2 = 397.7 \mu F}$$

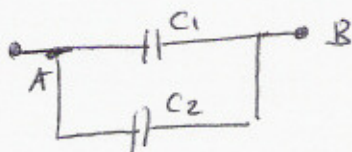b) $C_1 = 29.8 \mu F$

$C_1 < C_{eq} \Rightarrow$ The circuit should be parallel



$$C_{eq} = C_1 + C_2$$

$$32 = 29.8 + C_2$$

$$\Rightarrow \boxed{C_2 = 2.2 \mu F}$$