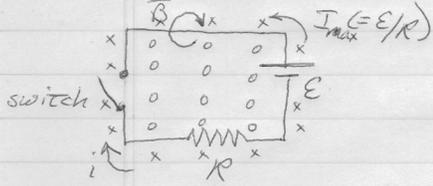


Self Inductance:

Consider circuit with current and emf



when throw switch

$$I = 0 \Rightarrow I_{max} = E/R$$

$$\therefore B = 0 \Rightarrow B = B_{max}$$

(Biot-Savart Law)

$$\therefore \Delta \Phi_B > 0$$

So, we will have induced emf + current

$$\mathcal{E}_L = - \frac{d\Phi_B}{dt}$$

• Lenz's Law means \mathcal{E}_L will oppose $\Delta \Phi_B$ and induce "back emf" + current, i


Since $\Phi_B \propto B \propto I$: $\mathcal{E}_L = -L \frac{dI}{dt}$
proportionality constant termed "inductance"

inductance: a measure of how much emf induced by loop (or coil - see later)

units: 'henrys' $1H = 1V \cdot s/A$

Get a slowdown in change in current: $I = I_{max} + i$

Inductors

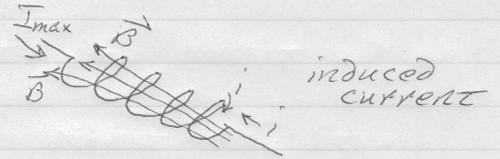

We can increase inductance by multiplying # loops, as shown for coil above.

$$\mathcal{E}_L = -N \frac{d\Phi}{dt} = -L \frac{dI}{dt}$$

Equating both sides + integrating over time:

$$N\Phi_B = LI$$


$$\therefore L = \frac{N\Phi_B}{I}$$

An 'inductor' has large self-inductance symbol: $\text{---} \text{---}$

-opposes changes in current in a circuit

③

RL Circuits

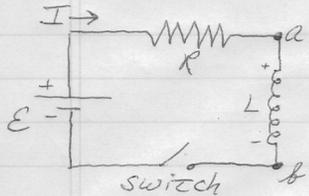

When close switch, I increases ($dI/dt > 0$)

$$\therefore \mathcal{E}_L = -L \frac{dI}{dt} < 0$$

Electric potential decreases when go from $a \rightarrow b$

From Kirchhoff's loop rule:
(+ divide by R)

$$\frac{\mathcal{E}}{R} - \frac{IR}{R} - \frac{L}{R} \frac{dI}{dt} = 0$$

if take $x = \mathcal{E}/R - I$, then

$$x + \frac{L}{R} \frac{dx}{dt} = 0$$

$$\int_{x_0}^x \frac{dx}{x} = -\left(\frac{R}{L}\right) \int_0^{\tau} d\tau$$

$$\Rightarrow \ln(x/x_0) = -R/L \tau$$

exponentiate:

$$x = x_0 e^{-R\tau/L}$$

$$\tau = \frac{L}{R}$$

time constant


$$I = \left(\frac{\mathcal{E}}{R}\right) (1 - e^{-R\tau/L})$$

↳ equilibrium value of the current

④

Prob. 15

RL circuit

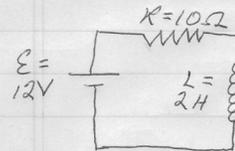

How long until current reaches 50% of its maximum value?

$$\frac{I}{I_{max}} = 0.5 = 1 - e^{-R\tau/L}$$

$$0.5 = e^{-R\tau/L}$$

$$\ln(0.5) = -R\tau/L$$

$$+0.69 = +R\tau/L \Rightarrow \tau = 0.69 \frac{L}{R}$$

$$\text{In seconds: } \tau = 0.69 \left(\frac{2H}{10\Omega}\right) = 0.14s$$

(5)

Energy Stored:

Use the Loop rule to quantify energy stored in an inductor in an RL circuit

$$\mathcal{E} + IR - L \frac{dI}{dt} = 0$$

$$I\mathcal{E} = I^2R + IL \frac{dI}{dt}$$

$$P_L = P_{\text{Tot}} - P_R = \frac{du}{dt}$$

$$\begin{matrix} \parallel & \parallel \\ I\mathcal{E} & I^2R \end{matrix}$$

$$\frac{du}{dt} = LI \frac{dI}{dt} \quad \text{rate energy stored}$$

Integrating gives

$$\int du = \int_0^{I_{\text{max}}} LI dI$$

$$U = \frac{1}{2} LI^2$$


Total energy stored

(6)

Mutual Inductance:

Take two adjacent coils

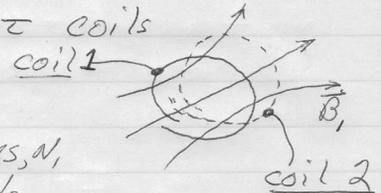- coil 1 has current I_1 and number of turns, N_1
- coil 2 has I_2, N_2



Coil 1 has current which sets up magnetic field, B_1

- some of these field lines pass thru coil 2 $\Rightarrow \Phi_{12}$ is flux thru 2 from 1

From Faraday's Law ($\Phi_{12} \propto I_1$)

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{12}}{dt} = -M_{12} \frac{dI_1}{dt}$$


"mutual inductance"
 $= N_2 \Phi_{12} / I_1$

So \mathcal{E}_2 is proportional to the rate other coil's current is changing.

7

LC Circuit

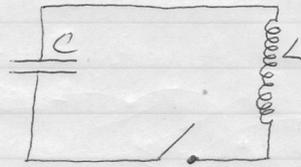Charge up a capacitor with charge Q , and place in circuit with inductor, L



switch

(note: no losses due to resistors)

Consider total energy

$$u = \frac{Q^2}{2C} + \frac{1}{2}LI^2$$

capac. induct.

- must remain constant in time ($du/dt = 0$)

$$\begin{aligned} \frac{du}{dt} &= \frac{d}{dt} \left(\frac{Q^2}{2C} + \frac{1}{2}LI^2 \right) \\ &= \frac{Q}{C} \frac{dQ}{dt} + LI \frac{dI}{dt} = 0 \end{aligned}$$

Since $I = dQ/dt$,

$$\frac{Q}{C} + L \frac{d^2Q}{dt^2} = 0$$

time-rate of change of current \rightarrow $\therefore \frac{d^2Q}{dt^2} = -\frac{1}{LC} Q$ $Q =$

NOTE: similarity to oscillating

springs $\frac{d^2x}{dt^2} = -\frac{k}{m}x = -\omega^2x$

Solution $\Rightarrow x = A \cos(\omega t + \phi)$

8

So solution would be

$$Q = Q_{\max} \cos(\omega t + \phi)$$

where $\omega = 1/\sqrt{LC}$ is the natural frequency.

We can calculate the current

$$I = dQ/dt = -\omega Q_{\max} \sin(\omega t + \phi)$$

so I is 90° out of phase with charge.

Total Energy

$$u = \frac{Q_{\max}^2}{2C} \cos^2 \omega t + \frac{LI_{\max}^2}{2} \sin^2 \omega t$$

E-field B-field

= constant