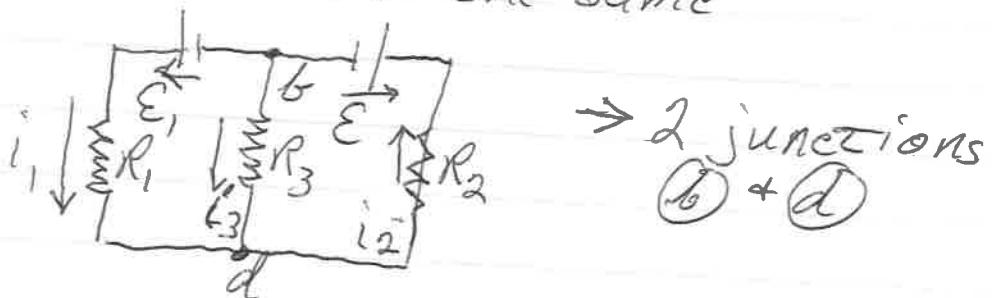


Multiloop Circuits

19.1

In a multiloop circuit, current thru resistors may not be the same



At each junction

- charge flows 'out' on some wires, and 'in' on others

@ b: i_2 "in" while i_3 "out"

$$+ i_1$$

$\therefore i_1 + i_3 = i_2$ {conservation of charge}

$$- \text{ or } \\ i_1 - i_2 + i_3 = \boxed{\sum i_i = 0}$$

Junction theorem:

"At any junction, the algebraic sum of currents must be zero."

14.2

How is this useful?

- we want to solve for relationships of currents, ϵ_i and R_i ,

left loop, counterclockwise:

$$\epsilon_1 - i_1 R_1 + i_3 R_3 = 0$$

right loop, clockwise:

$$-i_3 R_3 - i R_2 - \epsilon_2 = 0$$

need to have
consistent direction
thru R_3

using the junction rule,

$$i_3 + i_1 - i_2 = 0$$

We can solve for i_1 , i_2 and i_3 .

14. 3

$$i_1 = \frac{\mathcal{E}_1(R_2 + R_3) - \mathcal{E}_2 R}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$i_2 = \frac{\mathcal{E}_1 R_3 - \mathcal{E}_2 (R_1 + R_3)}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

$$i_3 = \frac{-\mathcal{E}_1 (R_2 + \mathcal{E}_2 R_1)}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

means i_3 goes 'up';
opposite our choice


Loop & Junction Rules 14.1

of times can use junction rule = one less than # of junctions
(=1 in prior example)

loops depends on finding new loops that have new unknown currents in each new equation
(=2 for prior example since 1 loop has 2 new currents + 2nd loop adds 3rd current)

The # of independent equations = # of unknown currents

14.5

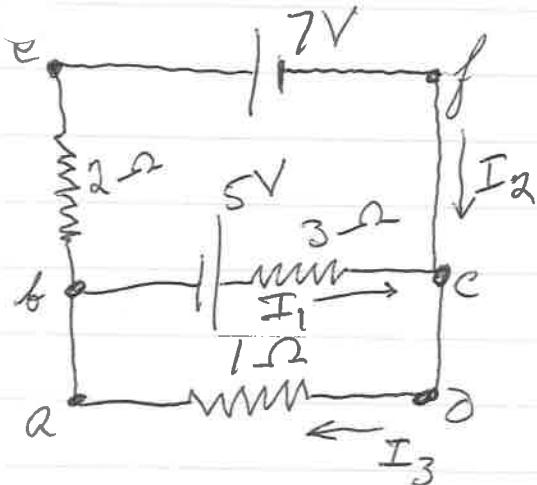Example

Consider

Cannot reduce
to R's in series
or parallel.

Write down
constraint eq's

$$\textcircled{1} @ c) \quad I_1 + I_2 = I_3$$

$$\textcircled{2} \text{ for abcda) } 5V - 3\Omega I_1 - 1\Omega I_2 = 0$$

$$\textcircled{3} \text{ for befcb) } -7V + 3\Omega I_1 - 5V - 2\Omega I_2 = 0 \\ -12V = 3\Omega I_1 + 2\Omega I_2 =$$

Using $\textcircled{1}$ in $\textcircled{2}$

$$\textcircled{4) } \quad 5V = 4\Omega I_1 + 1\Omega I_2$$

Taking $2 \times \textcircled{4} - \textcircled{3}$ yields $I_1 = 2A$

$$\text{in } \textcircled{3} \text{ get: } I_2 = -3.0A$$


$$\text{in } \textcircled{1} \text{ get: } I_3 = -1A$$

RC Circuits

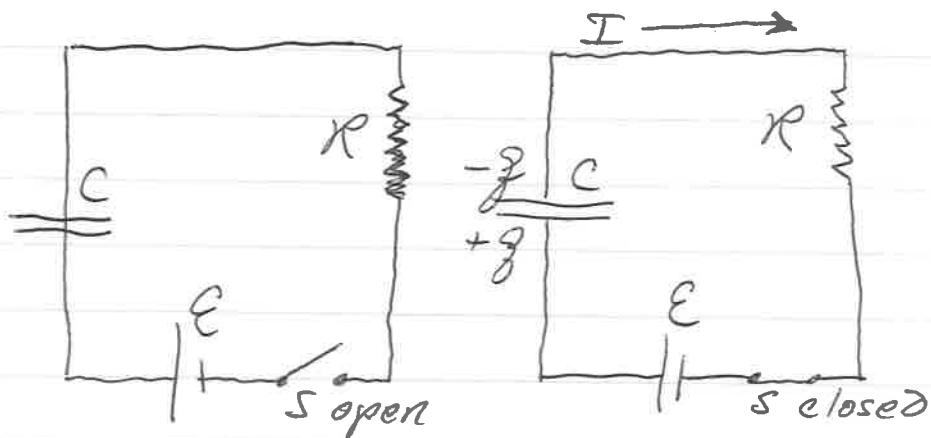14.6

Consider circuits containing R and C in series

- consider dynamic time when capacitor charges



- ϵ sets up E in wires
 - charge exchanged between plates and connecting wires
 - when capacitor fully charged \rightarrow max. charge depends on voltage
- $\rightarrow I=0$
- \rightarrow no more current

14.7

Consider case when switch 'S' is closed,

$$\mathcal{E} - \frac{Q}{C} - IR = 0$$

$\rightarrow Q(t)$ is instantaneous value of charge on capacitor

$$@ t=0 \quad I_0 = \frac{\mathcal{E}}{R}$$

- I is a maximum
- no \vec{E} in capacitor yet
- ΔV entirely felt across resistor

When charged fully

$$\rightarrow I_0 = 0$$

- $Q = CE$ (maximum charge)
- $\Delta V_{\text{across capacitor}}$

Time-Dependent Charge 14.3

We want analytic expression

$$\text{use } I = \frac{dq}{dt}$$

$$\frac{dq}{dt} = \frac{\epsilon}{R} - \frac{q}{RC} = -\frac{(q - C\epsilon)}{RC}$$

$$\frac{dq}{q - C\epsilon} = -\frac{1}{RC} dt$$

Integrating + using $q=0 @ t=0$

$$\int_0^q \frac{dq}{(q - C\epsilon)} = -\frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q - C\epsilon}{C\epsilon}\right) = -\frac{t}{RC}$$

$$-(q - C\epsilon)/C\epsilon = e^{-t/RC}$$

$$-q/C\epsilon = -1 + e^{-t/RC}$$


charge for

charging

capacitor

$$q(t) = C\epsilon(1 - e^{-t/RC})$$


$\rightarrow Q_0$

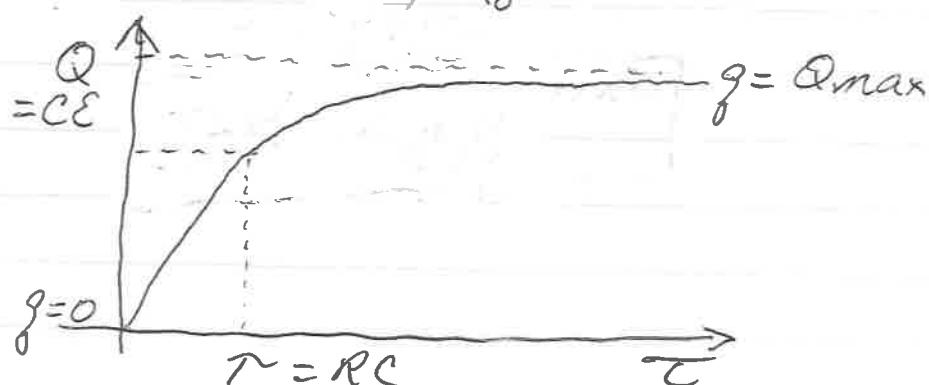

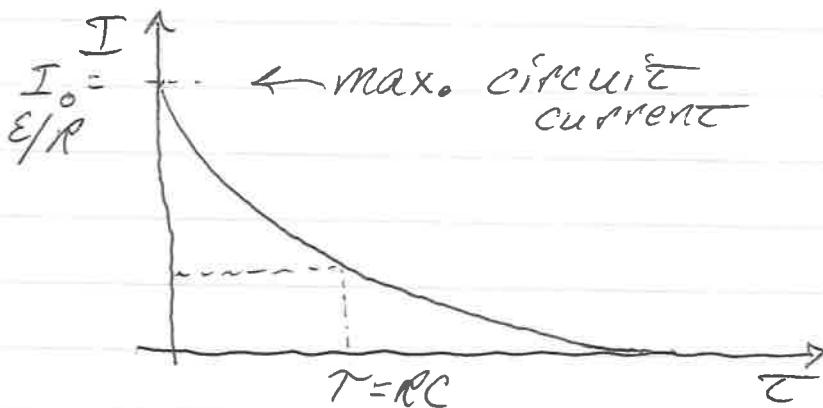14.9

$$\text{Current } I = \frac{dq}{dt}$$

$$I = \frac{dq}{dt} = \frac{E}{R} (e^{-t/\tau})$$
$$= [I_0 e^{-t/\tau}]$$




Time constant, $\tau = RC$

- time by which I goes to $1/e$ of initial I_0
 $\hookrightarrow = 0.368 I_0$

- in 2τ time
 $I = e^{-2} I_0 = \underline{\underline{0.135 I_0}}$

Discharging a Capacitor

14.10

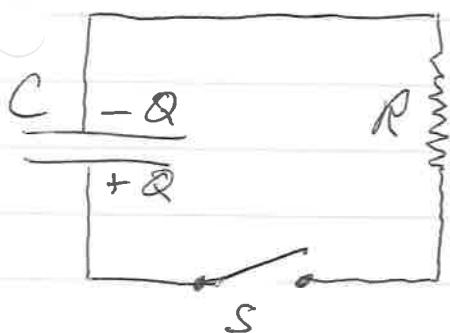

How do Q, I vary?

$$-\frac{Q}{C} - IR = 0 \quad (\text{loop eq.})$$

Using $I = \frac{dq}{dt}$

$$-R \frac{dq}{dt} = \frac{Q}{C}$$


$$\frac{dq}{q_0} = -\frac{1}{RC} dt$$

$$\int_a^q \frac{dq}{q_0} = -\frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q}{q_0}\right) = -t/RC$$

Therefore $q(t) = Q_0 e^{-t/RC}$
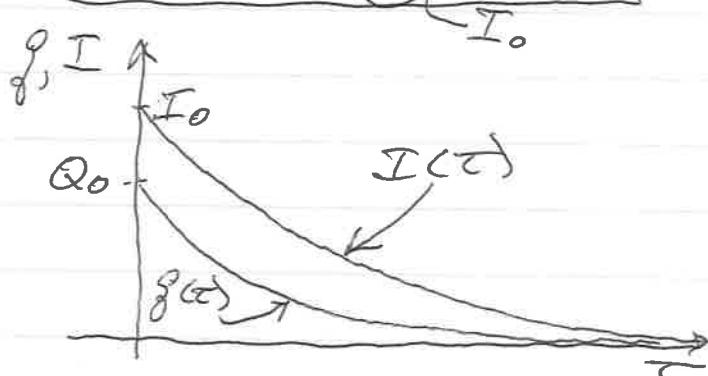
$$I = \frac{dq}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$



14.11

Example:

A circuit with a charged capacitor and a resistor in series is open.

If $R = 3\Omega$ and $C = 10\text{nF}$, how long will it take for the charge to reach $\frac{1}{4}$ of its initial value?

$$q(t) = Q_0 e^{-t/RC}$$

$$\frac{Q_0}{4} = Q_0 e^{-t/RC}$$

$$\ln\left(\frac{1}{4}\right) = \ln(e^{-t/RC})$$

$$+\ln 4 = +t/RC$$

$$t = RC \ln 4 = 1.39\pi$$

$$= 1.39(3.1)(10 \times 10^{-12} \text{F})$$

$$= 4.2 \times 10^{-8} \text{ sec}$$

$$\boxed{t = 4.2 \text{nsec}} !!$$