

# Electromotive Force

13.1

We saw that a battery delivers power to a resistive circuit in the work it does to move charge.


→ total potential difference in battery, "emf"




- not available to outside circuit

- battery has some internal resistance,  $r$

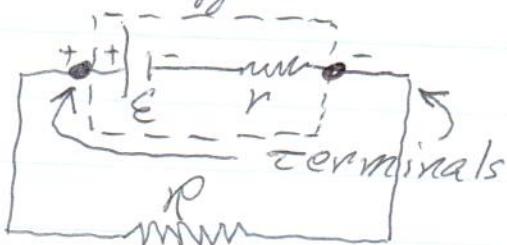- we need to adjust to determine potential difference across terminals



Consider voltage changes thru circuit

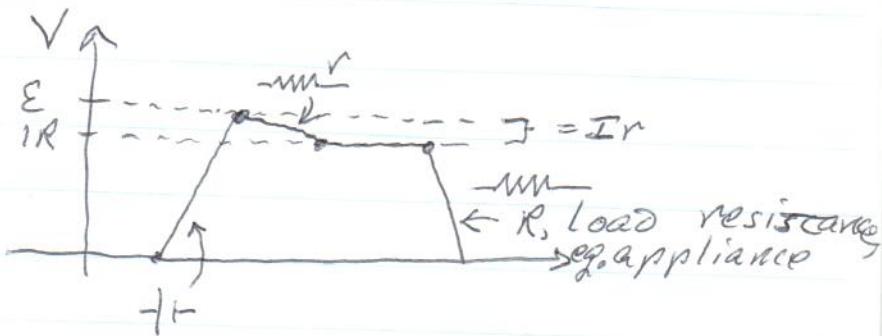

If  $r=0$ , terminal voltage  $= \mathcal{E}$

-  $\mathcal{E}$  is maximum possible voltage a battery can provide between its terminals

In general

$$\Delta V = \mathcal{E} - Ir$$

$\underbrace{\mathcal{E}}$  open circuit voltage  
 $\underbrace{Ir}$  terminal voltage

$$\Delta V = IR = \mathcal{E} - Ir$$

$$\mathcal{E} = I(R+r)$$

$$I = \mathcal{E} / (R+r)$$

$\hookrightarrow$  If  $R \gg r$ , can ignore  $r$ .

## Example:


13. 3

Consider battery with 9V emf, + internal resistance of ~~0.03Ω~~, + placed across a small light having 4Ω resistance.

a) calculate the current, ΔV,

$$I = \frac{\epsilon}{R+r}$$

$$= \frac{9V}{4.03\Omega} = 2.23A$$

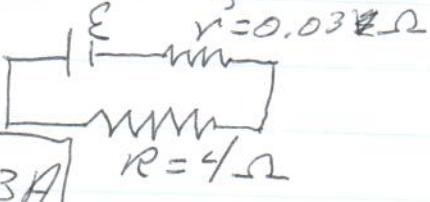

$$\Delta V = Ir = (2.23A)(4\Omega)$$
$$= 8.93V$$

b) calculate power delivered to load resistor

$$P = I^2 R = (2.23A)^2 (4\Omega)$$
$$= 19.9W$$

13.4

Batteries age - their internal resistance increases.

Consider prior example, but  $r = 1\Omega$  now:

$$I = \frac{\mathcal{E}}{R+r} = \frac{9V}{4\Omega + 1\Omega} = \boxed{1.8A}$$

$\downarrow$   
was 2.2A

$$\Delta V = \mathcal{E} - Ir = 9V - (1.8A)(1\Omega)$$
$$= \boxed{7.2V}$$

$\downarrow$   
was 8.9V


# Resistors in Series

13.5

Consider two resistors in series

$$I_1 = I_2$$

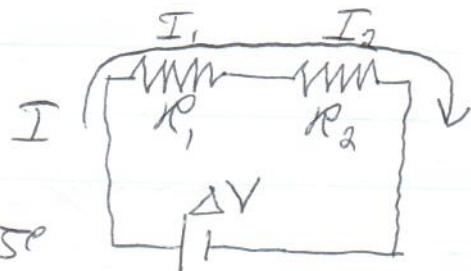- same charge  
passes thru  
both resistors



Potential drops  $\Delta V$  divided between resistors

$$\Delta V = IR_1 + IR_2 \\ = I(R_1 + R_2) = I\bar{R}_{eff}$$

effective resistance

$$\bar{R}_{eff} = R_1 + R_2$$

In general

$$\bar{R}_{eff} = R_1 + R_2 + R_3 + \dots$$

when all in series

## Resistors in Parallel

Two resistors in parallel.

- 2 conditions hold

- at junction A → current splits to go thru 2 resistors

$$\underline{I = I_1 + I_2} \quad \begin{cases} \text{conservation} \\ \text{of charge} \end{cases}$$

- also, same potential difference from A → B

$$\underline{\Delta V = \Delta V_1 = \Delta V_2}$$


so

$$\begin{aligned} I &= I_1 + I_2 = \frac{\Delta V}{R_1} + \frac{\Delta V_2}{R_2} \\ &= \Delta V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \Delta V R_{\text{eff}} \end{aligned}$$

In general,

$$\begin{aligned} \frac{1}{R_{\text{eff}}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \\ \underline{\underline{R_{\text{eff}}}} &= \boxed{\sum_i \frac{1}{R_i}} \end{aligned}$$

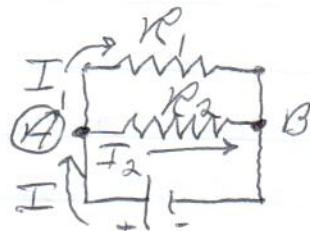( $R_{\text{eff}} < \text{minimum of } R_i$ )



## Example


13.7

A circuit includes a complex array of resistors

$$\Delta V = 120V$$

$$R_1 = 5\Omega$$

$$R_2 = R_6 = 8\Omega$$

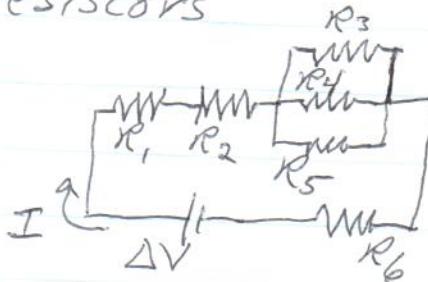

$$R_3 = R_4 = 6\Omega ; R_5 = 3\Omega$$

Calculate the currents.

a)

$$\begin{aligned}
 R_{\text{eff}} &= R_1 + R_2 + R_6 + \left[ \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right]^{-1} \\
 &= 21\Omega + \left[ \frac{2}{6\Omega} + \frac{1}{3\Omega} \right]^{-1} \\
 &= 21\Omega + \frac{3}{2}\Omega = \boxed{22.5\Omega}
 \end{aligned}$$

$$\begin{aligned}
 I &= \Delta V / R_{\text{eff}} = 120V / 22.5\Omega = \boxed{5.33A} \\
 \boxed{I_1 = I_2 = I_6}
 \end{aligned}$$

$$\text{For } I_3 + I_4 + I_5 \quad \Delta V_3 = \Delta V_4 = \Delta V_5$$

$$1) (6\Omega)I_3 = (6\Omega)I_4 = (3\Omega)I_5$$

$$I_3 = I_4 ; I_5 = 2I_4$$

$$I = \boxed{5.33A = I_3 + I_4 + 2I_4 = 4I_3}$$


$$\boxed{I_3 = 1.33A} = I_4$$

$$\boxed{I_5 = 2.67A}$$

## Loop theorem:

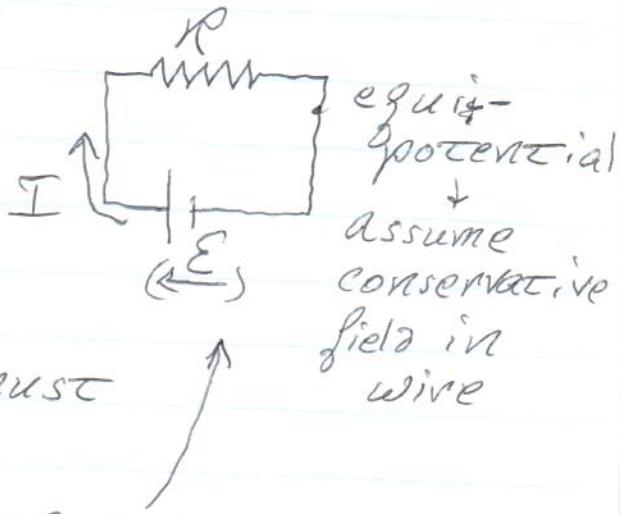13.8

algebraic sum  
of changes in  
potential en-  
countered in  
a complete  
circuit loop must  
be zero.



equi-  
potential  
+  
assume  
conservative  
field in  
wire

$$-iR + E = 0$$

-equivalent to conservation  
of energy

For a resistor traversed in  
current direction  $\rightarrow \Delta V = -iR$


- equals  $+iR$  in opposite direction

When sort of emf traversed in  
emf direction (i.e.  $\theta$  to  $\Theta$ )

$$\Delta V = +E \quad (-E \text{ if opposite direction})$$

## Example

13.9

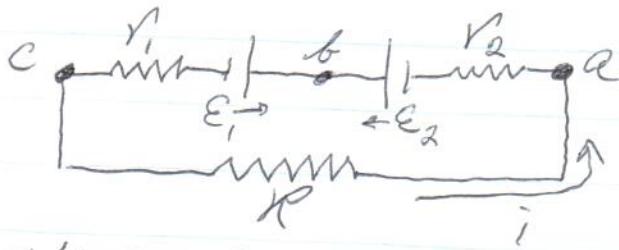

$$E_1 = 2.0V; E_2 = 4.0V$$

$$r_1 = 1.0\Omega; r_2 = 2.0\Omega; R = 5.0\Omega$$

What is the current  $i$ ?

Since 2 emfs and  $E_2 > E_1$ ,

-  $i$  will flow counterclockwise

Note: don't actually need  
to know as we'll see

Using loop theorem:

$$-E_2 + ir_2 + iR + ir_1 + E_1 = 0$$

$$i(r_2 + R + r_1) = E_2 - E_1$$

$$i = \frac{(E_2 - E_1)}{(r_2 + R + r_1)} = \frac{2V}{8\Omega}$$

$$= 0.25A$$

Note signs!

The + sign means our choice  
of direction for ' $i$ ' is correct.

13. 10

Let's assume current going clockwise:

loop rule  $\rightarrow -\mathcal{E}_2 - iR_2 - iR - iR_1 + \mathcal{E}_1 = 0$


$$i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2 + R}$$

$$= \boxed{-0.25A}$$

i.e. current flows counter-clockwise as seen in previous page
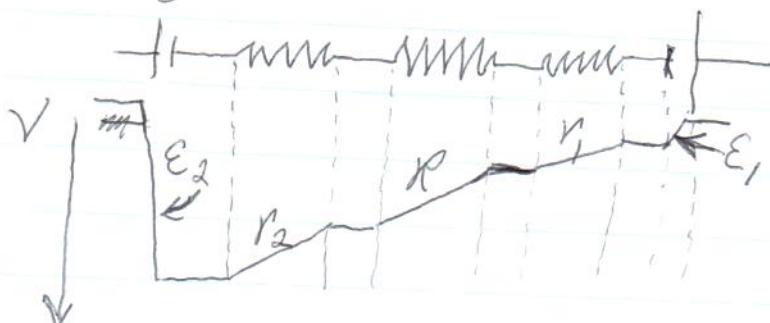
## Potential Differences

Going from  $\textcircled{B}$  to  $\textcircled{A}$



$$\underline{-iR_2 + \mathcal{E}_2} = -(0.25A)(2-2) + 4.5V$$
$$= \underline{\underline{+3.5V}}$$