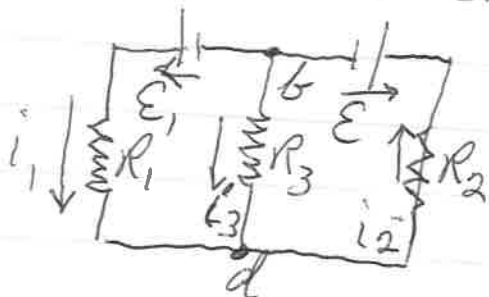


Multiloop Circuits

14.1

In a multiloop circuit, current thru resistors may not be the same



→ 2 junctions
ⓑ + ⓓ

At each junction

- charge flows 'out' on some wires, and 'in' on others

@ ⓑ: i_2 "in" while i_3 "out"

$$i_1 + i_3 = i_2 \quad \left\{ \begin{array}{l} \text{conservation} \\ \text{of charge} \end{array} \right.$$

- or -

$$i_1 - i_2 + i_3 = \boxed{\sum i_i = 0}$$

Junction theorem:

"At any junction, the algebraic sum of currents must be zero."

14.2

How is this useful?

- we want to solve for relationship of currents, \mathcal{E}_i and R_i

left loop, counterclockwise!

$$\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0$$

right loop, clockwise!

$$-i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0$$

↳ need to have consistent direction thru R_3

using the junction rule,

$$i_3 + i_1 - i_2 = 0$$

We can solve for i_1 , i_2 and i_3 .

14.2

$$i_1 = \frac{E_1 (R_2 + R_3) - E_2 R_1}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$i_2 = \frac{E_1 R_3 - E_2 (R_1 + R_3)}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

4

$$i_3 = \ominus \frac{(E_1 R_2 + E_2 R_1)}{R_1 R_3 + R_2 R_3 + R_1 R_2}$$

means i_3 goes 'up',
opposite our choice

Loop & Junction Rules 14.8


of times can use junction rule = one less than # of junctions
(= 1 in prior example)

loops depends on finding new loops that have new unknown currents in each new equation
(= 2 for prior example since 1 loop has 2 new currents & 2nd loop adds 3rd current)

The # of independent equations = # of unknown currents

Example

14.5

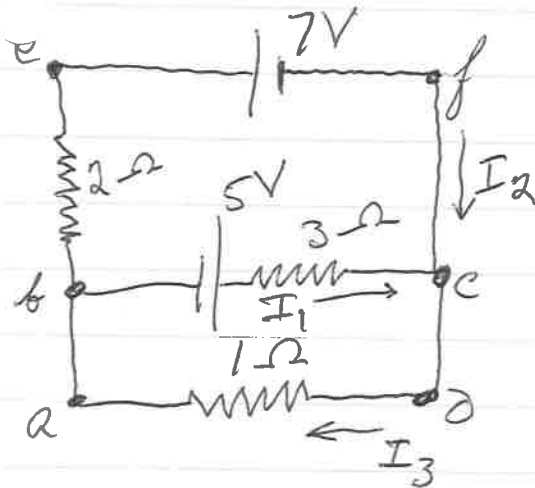

Consider

Cannot reduce to R's in series or parallel.

Write down constraint eq's

① @ c) $I_1 + I_2 = I_3$

② for abcda) $5V - 3\Omega I_1 - 1\Omega I_2 = 0$

③ for befcb) $-7V + 3\Omega I_1 - 5V - 2\Omega I_2 = 0$
 $-12V = 3\Omega I_1 + 2\Omega I_2 =$

Using ① in ②

④ $5V = 4\Omega I_1 + 1\Omega I_2$

Taking $2 \times$ ④ - ③ yields $I_1 = 2A$

in ③ get: $I_2 = -3.0A$


in ① get: $I_3 = -1A$

RC Circuits

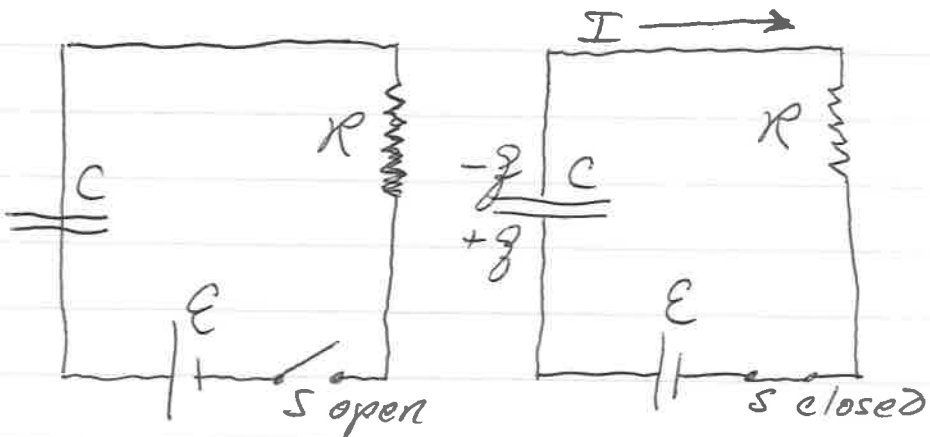14.6

Consider circuits containing R and C in series

- consider dynamic time when capacitor charging



- \mathcal{E} sets up \vec{E} in wires

- charge exchanged between plates and connecting wires

- when capacitor fully charged \rightarrow depends on
- max. charge voltage

$$\rightarrow I = 0$$

\rightarrow no more current

14.7

Consider case when switch 's' is closed,

$$\mathcal{E} - \frac{Q}{C} - IR = 0$$

$Q(t)$ is instantaneous value of charge on capacitor

$$\text{@ } \tau = 0 \quad I_0 = \frac{\mathcal{E}}{R}$$

→ I is a maximum

→ no \vec{E} in capacitor yet

→ ΔV entirely felt across resistor

When charged fully

$$\rightarrow I_0 = 0$$

- $Q = C\mathcal{E}$ (maximum charge)

- ΔV across capacitor

Time-Dependent Charge 14.8

We want analytic expression

use $I = dq/dt$

$$\frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC} = -\frac{(q - C\mathcal{E})}{RC}$$

$$\frac{dq}{q - C\mathcal{E}} = -\frac{1}{RC} dt$$

Integrating + using $q = 0 @ t = 0$

$$\int_0^q \frac{dq}{(q - C\mathcal{E})} = -\frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q - C\mathcal{E}}{0 - C\mathcal{E}}\right) = -\frac{t}{RC}$$


$$-\frac{(q - C\mathcal{E})}{C\mathcal{E}} = e^{-t/RC}$$

$$-q/C\mathcal{E} = -1 + e^{-t/RC}$$

charge for
charging
capacitor

$$q(t) = (C\mathcal{E})(1 - e^{-t/RC})$$


$\rightarrow Q_0$

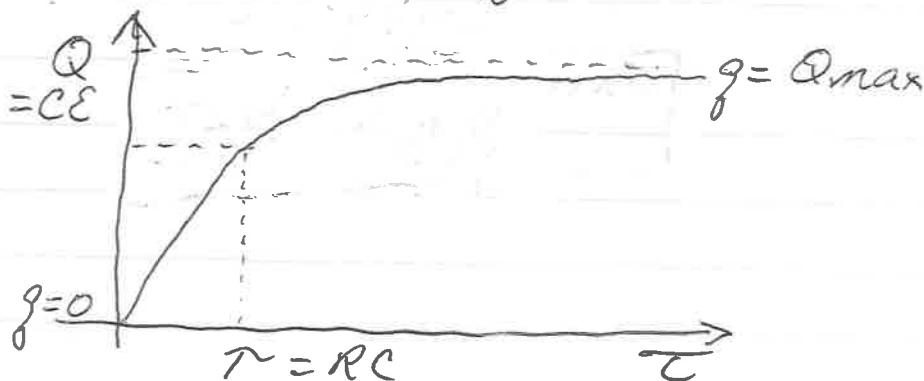

$$\text{Current } \tau = dq/dt$$

$$\underline{\underline{I}} = \frac{dq}{dt} = \frac{\epsilon}{R} (e^{-t/RC})$$

$$= \boxed{I_0 e^{-t/\tau}}$$

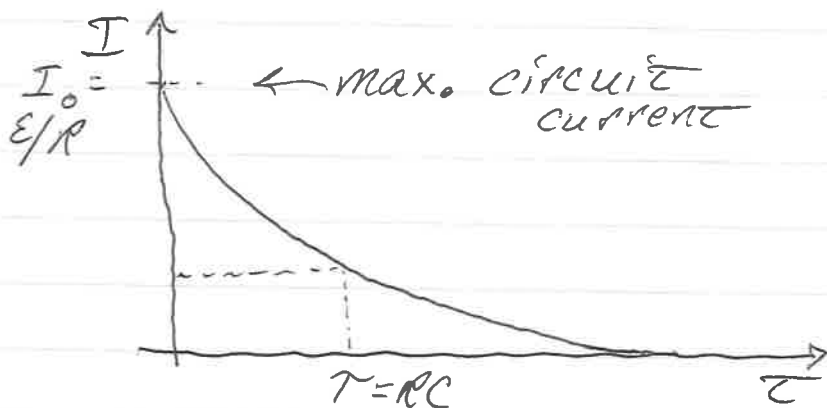

Time constant, $\tau = RC$


- time by which I goes
to $1/e$ of initial I_0
 $\hookrightarrow = \underline{\underline{0.368 I_0}}$

- in 2τ time,

$$\underline{\underline{I}} = e^{-2} I_0 = \underline{\underline{0.135 I_0}}$$

Discharging a Capacitor

14.10

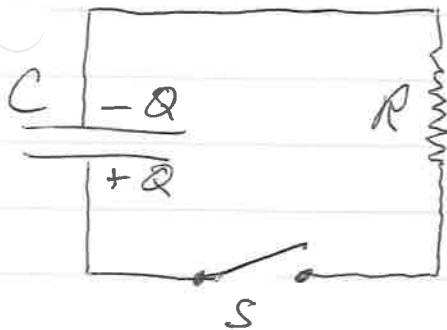

How do Q , I vary?

$$-\frac{q}{C} - IR = 0$$

(loop eq.)

Using $I = dq/dt$

$$-R \frac{dq}{dt} = \frac{q}{C}$$

$$\frac{dq}{q} = -\frac{1}{RC} dt$$


$$\int_{Q_0}^q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q}{Q_0}\right) = -t/RC$$

Therefore $q(t) = Q_0 e^{-t/RC}$

$$I = \frac{dq}{dt} = -\left(\frac{Q_0}{RC}\right) e^{-t/RC}$$

I_0

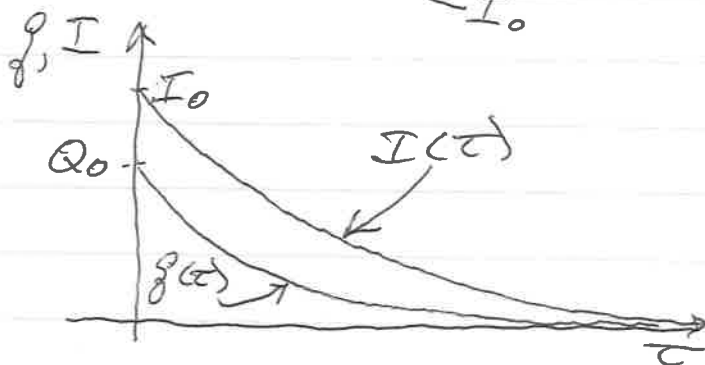

14.11

Example:

A circuit with a charged capacitor and a resistor in series is open.

If $R=3\Omega$ and $C=10\text{nF}$, how long will it take for the charge to reach $\frac{1}{4}$ of its initial value?

$$q(\tau) = Q_0 e^{-\tau/RC}$$

$$\frac{Q_0}{4} = Q_0 e^{-\tau/RC}$$

$$\ln\left(\frac{1}{4}\right) = \ln(e^{-\tau/RC})$$

$$+\ln 4 = +\tau/RC$$

$$\tau = RC \ln 4 = 1.39\tau$$

$$= 1.39(3\Omega)(10 \times 10^{-9}\text{F})$$

$$= 4.2 \times 10^{-8}\text{ sec}$$

$$\boxed{\tau = 42\text{nsec}} \quad !!$$