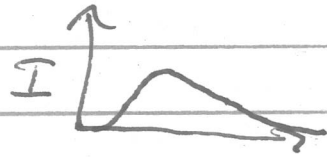


# Electronics

Need to retrieve signal from individual detector sensor

→ eg. current




Several aspects of pulse that are important.

- a) above threshold w/ respect to noise?
- b) what is event rate?
- c) optimal energy measurement
- d) when does signal arrive

For instance, a drift detector such as LAr can accrue charge over long time

- may be  $\gg$  event time

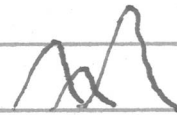

- may need to modify pulse to take part of charge
  - ignore rest
  - ie. juggles energy resolution with event rate

→ problem with overlapping signals

Generally must digitize signal to enable analysis

analog electronics

## Direct Radiative Detection

Energy deposited in a material

- converted to charge pairs (i.e. current)
- generally  $\propto$  energy
- can be very low charge ( $10^{-16}$  C)

Need to integrate + amplify the signal  
since so small: Preamplifier

- have problem that noise can be significant + reduce resolution
- noise more of a problem when capacitances of sensor + preamp large


### White Noise

- variations in apparent signal due to random processes
  - thermal electrons
  - electrical interferences
- will have a range of ~~freq~~ characteristic frequencies
- expected signal will have a more restricted range of frequency components


Shaper: reduce bandwidth + duration of <sup>critical</sup> signal pulse

# Example Analog Pipelines

Direct detection case:

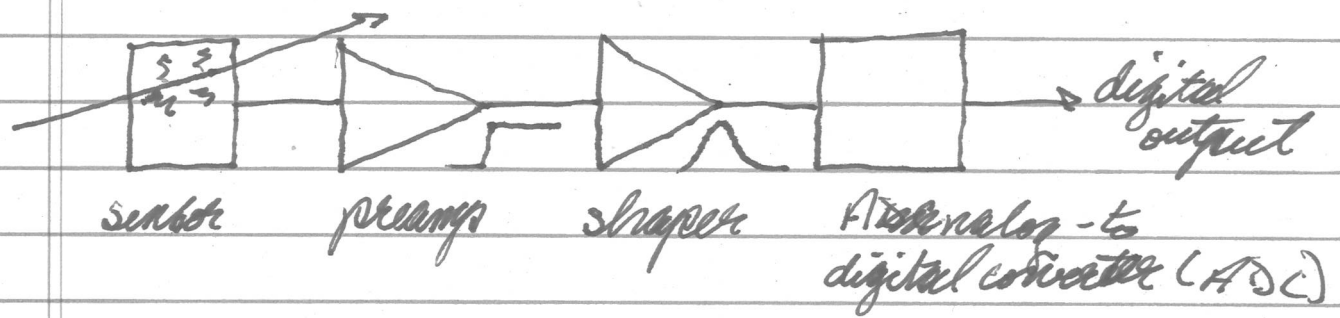

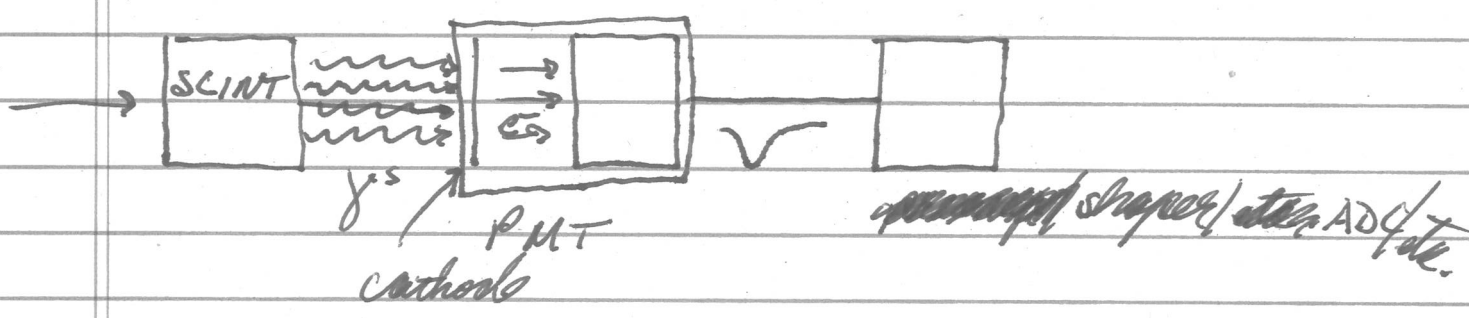
Indirect detection case: (PMT + scintillator)



Some fraction of events will generally be recorded (triggering)

→ until decision made, need to "buffer" or hold analog signals

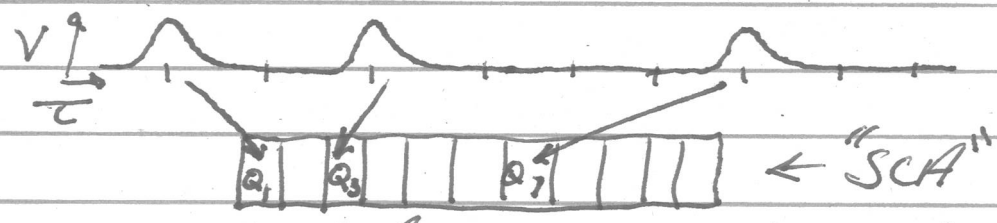- output of preamp/shaper can be used to charge a capacitor




switched capacitor array: each event sent to different capacitor 'cell'

The buffered signals are stored according to timing + control signals in electronics

- <sup>synchronizing</sup> critical to make all cells of a detector for a given event
- you need to know exactly what SCA cells make whole event

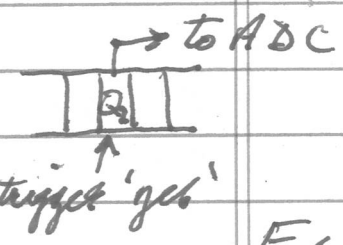- when trigger indicates to readout a given event
- all <sup>relevant</sup> SCA cell contents corresponding to that event are digitized




For wide pulses, may choose to 'sample' pulse several times



eg. ATLAS LAr Calorimeter

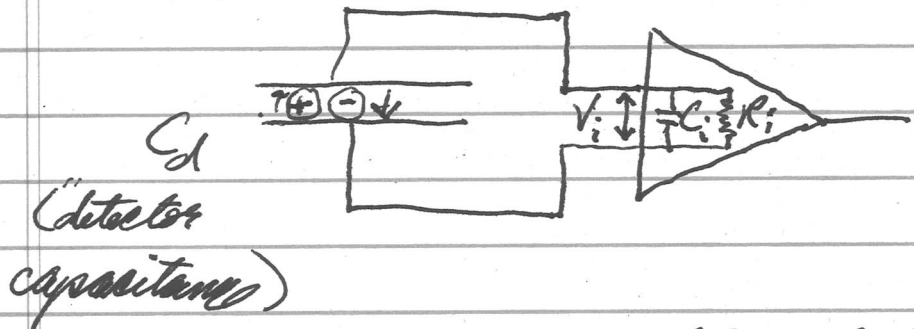
# Charge-sensitive Amplifier

Consider detector element, an ionization medium



- can have a problem that output signal height depends on  $C_i$

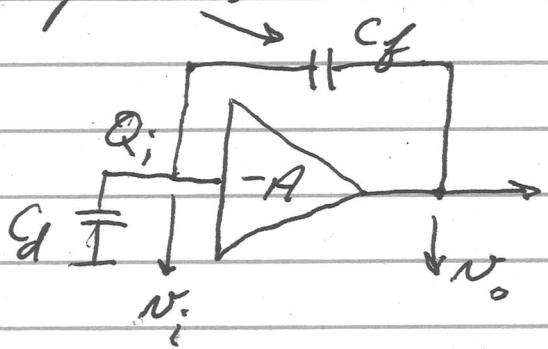Use inverting amplifier and feedback capacitor



( $R_i \sim \infty$ , so no current flows amplifier)

-  $A$  is voltage gain,  $V_o = -AV_i$

$$\therefore \Delta V = V_o = V_o - V_i = (A+1)V_i$$

charge on  $C_f$ !

$$Q_f = C_f V_o = C_f (A+1)V_i$$

6

Because no current in amplifier,

$$Q_f = Q_i$$

$$C_i = \frac{Q_i}{V_i} = C_f (A+1)$$

This gives the voltage output per unit input charge

$$\underline{A_Q} = \frac{\Delta V_o}{\Delta Q_i} = \frac{A \cancel{V_i}}{C_i \cancel{V_i}} = \frac{A}{(A+1)C_f} \sim \boxed{\frac{1}{C_f}} \quad (A \gg 1)$$

→ gain is determined by feedback capacitor

### Calibration

→ can use this system with a test input before the program