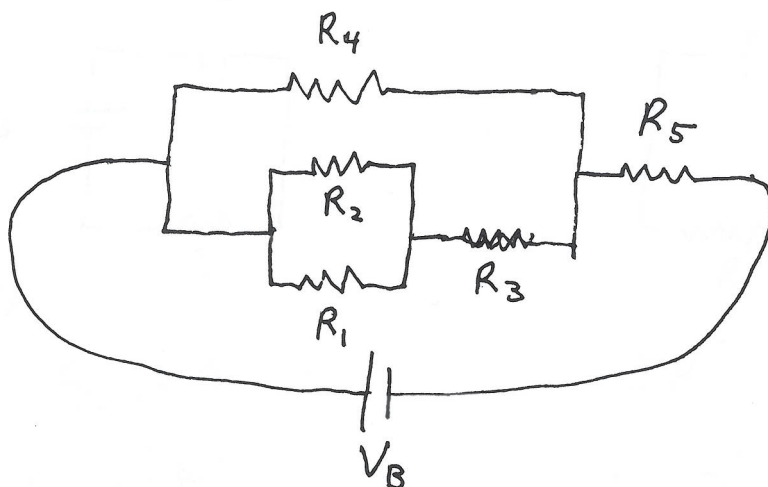



SMU Physics 1308 : Fall 2009

Final Exam

Problem 1 : The figure below shows a circuit with the corresponding resistances $R_1 = 2\Omega$, $R_2 = 7\Omega$, $R_3 = 11\Omega$, $R_4 = 13\Omega$, $R_5 = 17\Omega$. If the battery has the voltage $V_0 = 5V$, find the currents I_1, I_2, I_3, I_4, I_5 .



reduce to :

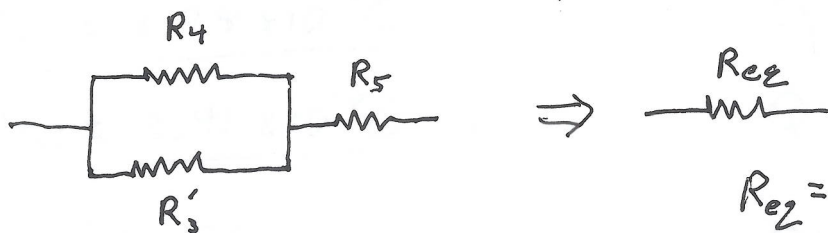

$$R_{eq} = R_5 + \left(\frac{1}{R_4} + \frac{1}{R_3'} \right)^{-1} = \underline{\underline{23.39\Omega}}$$

$$R_3' = R_3 + \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \underline{\underline{12.56\Omega}}$$

$$I_5 = \frac{V_B}{R_{eq}} = \underline{\underline{0.214A}}$$

$$V_4 = V_B - I_5 R_5 = \underline{\underline{1.37V}}$$

$$I_4 = \frac{V_4}{R_4} = \underline{\underline{0.105A}}$$

V_{12} : Voltage across R_1, R_2

$$I_3 = \frac{V_4}{R_3'} = \underline{\underline{0.109A}}$$

$$V_{12} = V_4 - I_3 R_3 = \underline{\underline{0.169V}}$$


$$I_2 = \frac{V_{12}}{R_2} = \underline{\underline{0.024A}}$$

Note : $I_1 + I_2 = I_3$

$$I_3 + I_4 = I_5$$

$$I_1 = \frac{V_{12}}{R_1} = \underline{\underline{0.085A}}$$

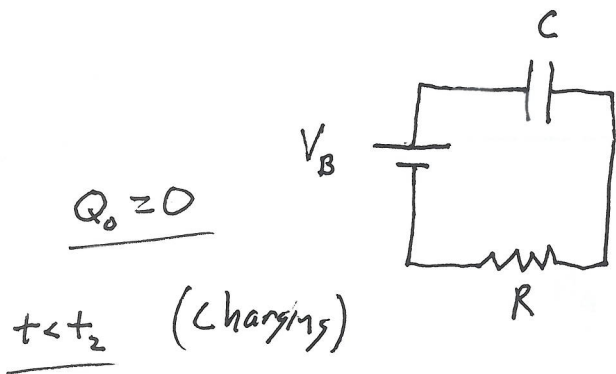Problem 2 : The RC circuit shown below has $R = 12\Omega$ and $C = 1.0 \times 10^{-6} \text{ F}$. Initially ($t = 0$) there is $Q_0 = 0$ on the capacitor, at which time the battery $V_B = 7 \text{ V}$ is turned on. Find the charge $Q(t_1)$ at $t_1 = 4 \times 10^{-6} \text{ s}$. At $t_2 = 8 \times 10^{-6} \text{ s}$ the battery is replaced by a wire and the capacitor begins to discharge. Find the charge $Q(t_2)$ (which is the new Q_0 for the discharging capacitor) and the charge $Q(t_3)$ at $t_3 = 12 \times 10^{-6} \text{ s}$. Also find the currents $I_0, I(t_1), I(t_2), I(t_3)$.



$$V_B - IR - Q/C = 0$$

$$Q = CV_B(1 - e^{-t/RC})$$

$$Q(t_1) = \underline{1.98 \times 10^{-6} \text{ C}}$$


$$Q(t_2) = \underline{3.41 \times 10^{-6} \text{ C}}$$

$$I = (V_B - Q/C)/R$$

$$I_0 = V_B/R = \underline{0.583 \text{ A}}$$

$$I(t_1) = \underline{0.418 \text{ A}}$$

$$I(t_2) = \underline{0.299 \text{ A}}$$

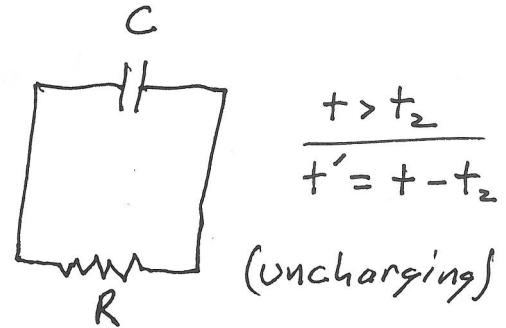

$$-IR - Q/C = 0$$

$$Q = Q_0' e^{-t'/RC}$$

$$Q_0' = Q(t_2)$$


$$Q = Q(t_2) e^{-(t-t_2)/RC}$$

$$Q(t_3) = \underline{2.44 \times 10^{-6} \text{ C}}$$

$$I = -Q/RC$$

$$I(t_3) = \underline{-0.203 \text{ A}}$$

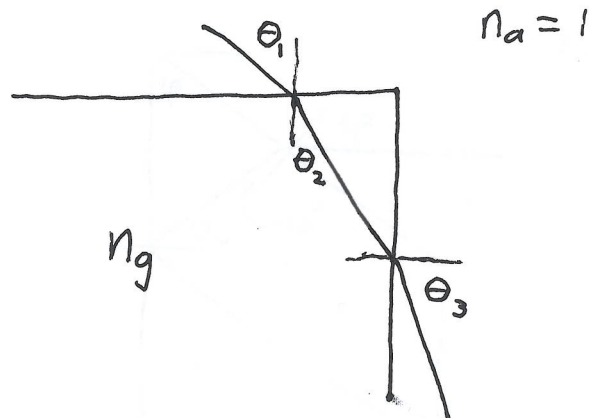Problem 3 : As shown in the figure below, a ray of light is incident from air ($n_a = 1$) at an angle $\theta_1 = 50^\circ$ from the vertical on a piece of glass which makes a right angle. The light ray bends to an angle θ_2 from the vertical upon passing into the glass, after which it exits the glass at an angle $\theta_3 = 67^\circ$ from the horizontal. Find the index of refraction n_g of the glass, and find the angle θ_2 . You will need $\sin^2(\theta) + \cos^2(\theta) = 1$.



$$n_a \sin \theta_1 = n_g \sin \theta_2$$

$$n_g \sin(90 - \theta_2) = n_a \sin \theta_3$$



$$\sin \theta_1 = n_g \sin \theta_2$$

$$\sin \theta_3 = n_g \cos \theta_2$$


$$\sin^2 \theta_1 + \sin^2 \theta_3 = n_g^2$$

$$n_g = (\sin^2 \theta_1 + \sin^2 \theta_3)^{1/2} = \underline{\underline{1.198}}$$

$$\sin \theta_2 = \sin \theta_1 / n_g$$

$$\theta_2 = \underline{\underline{39.77^\circ}}$$

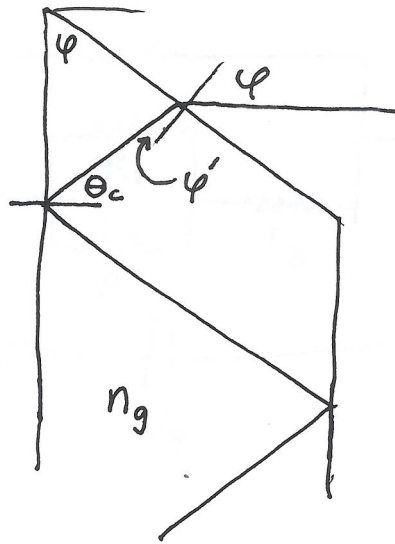Problem 4 : The figure below shows a piece of glass of refractive index $n_g = 1.6$ which is cut at an angle φ such that a ray which enters the glass from the surrounding air $n_a = 1.0$ along the horizontal line shown will reflect off the interior surfaces of the glass. Find the smallest angle φ above which this total internal reflection is possible, and find the corresponding reflection angle θ_c . Find the smallest index of refraction n_c such that this scenario is possible (this corresponds to requiring that $\tan(\varphi) = \sin(\varphi)/\cos(\varphi) > 0$). You will need $\sin(\varphi - \theta_c) = \sin(\varphi)\cos(\theta_c) - \cos(\varphi)\sin(\theta_c)$.



$$n_a = 1$$

$$\sin \varphi = n_g \sin \varphi'$$

$$\varphi + 90 - \theta_c + 90 - \varphi' = 180$$

$$\varphi' = \varphi - \theta_c$$

$$\text{TIR: } n_g \sin \theta_c = 1$$

$$\sin \varphi = n_g \sin(\varphi - \theta_c) = n_g (\sin \varphi \cos \theta_c - \cos \varphi \sin \theta_c)$$

$$\tan \varphi = n_g \cos \theta_c \tan \varphi - \underbrace{n_g \sin \theta_c}_{=1}$$

$$\tan \varphi = (n_g \cos \theta_c - 1)^{-1}$$

$$n_g \cos \theta_c = n_g (1 - \sin^2 \theta_c)^{1/2} = n_g (1 - n_g^{-2})^{1/2} = (n_g^2 - 1)^{1/2}$$

$$\tan \varphi = ((n_g^2 - 1)^{1/2} - 1)^{-1}$$

$\tan \varphi > 0$
requires:

$$n_g = 1.6 : \quad \varphi = \underline{\underline{76^\circ}}$$

$$n_g > n_c = \underline{\underline{\sqrt{2}}}$$