
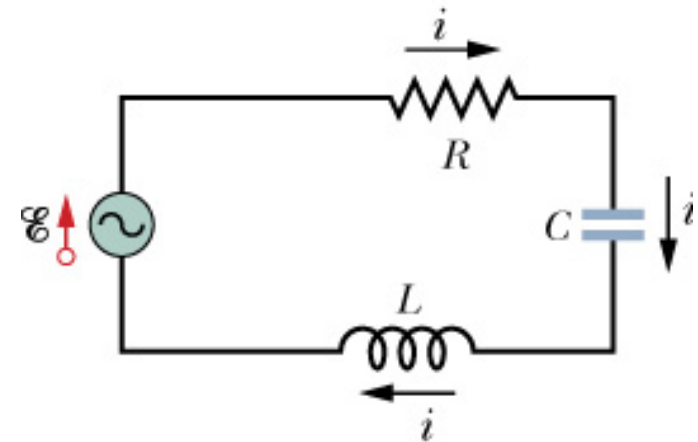
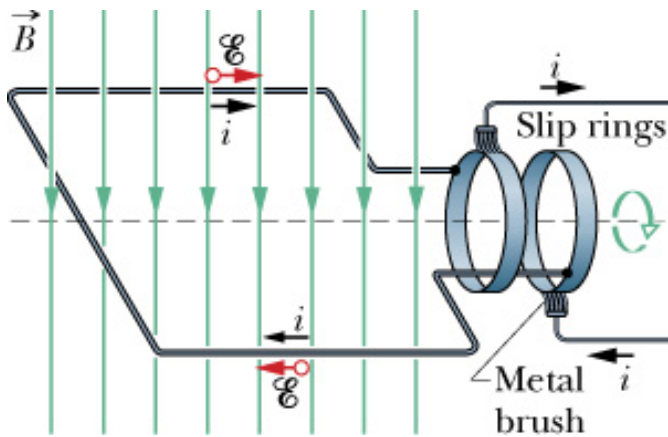
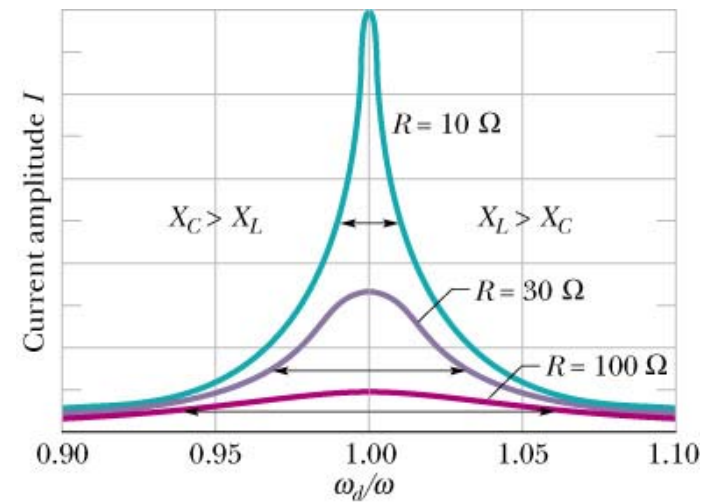
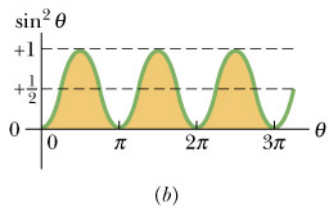



Chapter 21: RLC Circuits

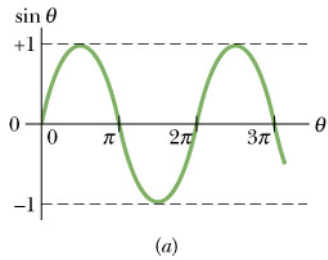

Voltage and Current in RLC Circuits

→ AC emf source: "driving frequency" f
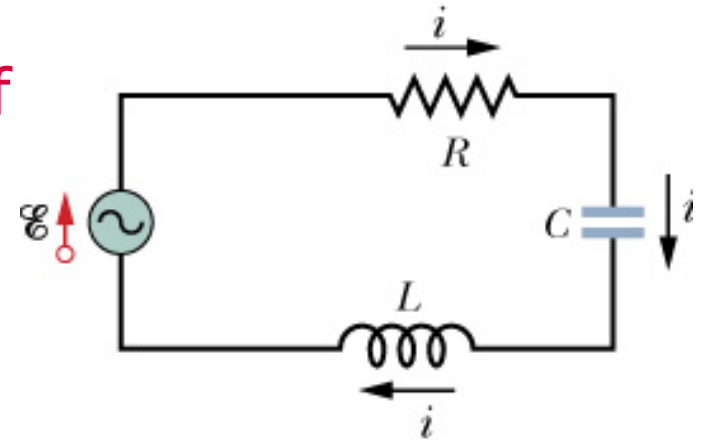
$$\varepsilon = \varepsilon_m \sin \omega t \quad \omega = 2\pi f$$



→ If circuit contains only R + emf source, current is simple

$$i = \frac{\varepsilon}{R} = I_m \sin(\omega t) \quad I_m = \frac{\varepsilon_m}{R} \quad (\text{current amplitude})$$

→ If L and/or C present, current is *not* in phase with emf

$$i = I_m \sin(\omega t - \phi) \quad I_m = \frac{\varepsilon_m}{Z}$$

→ Z , ϕ shown later

AC Source and Resistor Only


→ Driving voltage is $\varepsilon = \varepsilon_m \sin \omega t$

→ Relation of current and voltage

$$i = \varepsilon / R$$

$$i = I_m \sin \omega t \quad I_m = \frac{\varepsilon_m}{R}$$

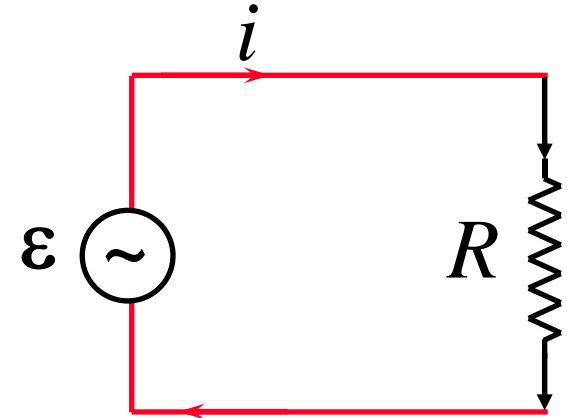◆ Current is *in phase* with voltage ($\phi = 0$)



AC Source and Capacitor Only

→ Voltage is $v_C = \frac{q}{C} = \varepsilon_m \sin \omega t$

→ Differentiate to find current

$$q = C \varepsilon_m \sin \omega t$$

$$i = dq / dt = \omega C V_C \cos \omega t$$

→ Rewrite using phase (check this!)


$$i = \omega C V_C \sin(\omega t + 90^\circ)$$

→ Relation of current and voltage

$$i = I_m \sin(\omega t + 90^\circ) \quad I_m = \frac{\varepsilon_m}{X_C} \quad (X_C = 1 / \omega C)$$

→ "Capacitive reactance": $X_C = 1 / \omega C$

◆ Current "leads" voltage by 90°

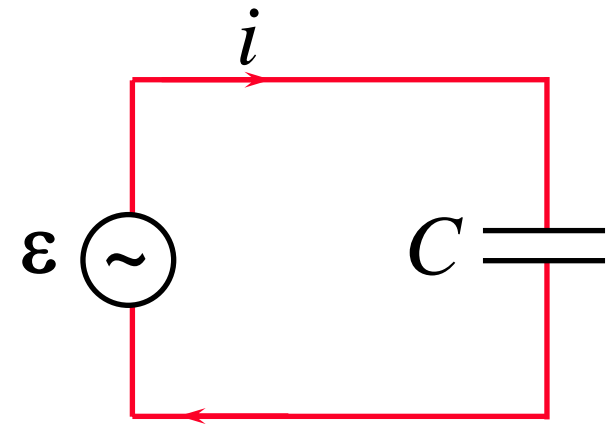

AC Source and Inductor Only

→ Voltage is $v_L = L di / dt = \varepsilon_m \sin \omega t$

→ Integrate di/dt to find current:

$$di / dt = (\varepsilon_m / L) \sin \omega t$$

$$i = -(\varepsilon_m / \omega L) \cos \omega t$$

→ Rewrite using phase (check this!)


$$i = (\varepsilon_m / \omega L) \sin(\omega t - 90^\circ)$$

→ Relation of current and voltage

$$i = I_m \sin(\omega t - 90^\circ) \quad I_m = \frac{\varepsilon_m}{X_L} \quad (X_L = \omega L)$$

→ "Inductive reactance": $X_L = \omega L$

◆ Current "lags" voltage by 90°

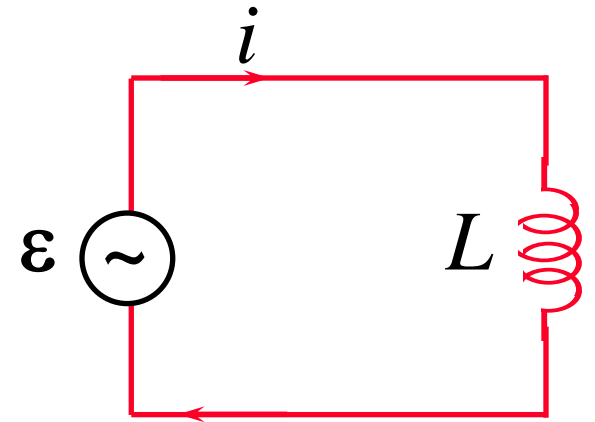

General Solution for RLC Circuit

→ We *assume* steady state solution of form $i = I_m \sin(\omega t - \phi)$

- ◆ I_m is current amplitude
- ◆ ϕ is phase by which current "lags" the driving EMF
- ◆ Must determine I_m and ϕ

→ Plug in solution: differentiate & integrate $\sin(\omega t - \phi)$

$$i = I_m \sin(\omega t - \phi)$$

$$\frac{di}{dt} = \omega I_m \cos(\omega t - \phi)$$

$$q = -\frac{I_m}{\omega} \cos(\omega t - \phi)$$

Substitute



$$L \frac{di}{dt} + Ri + \frac{q}{C} = \varepsilon_m \sin \omega t$$



$$I_m \omega L \cos(\omega t - \phi) + I_m R \sin(\omega t - \phi) - \frac{I_m}{\omega C} \cos(\omega t - \phi) = \varepsilon_m \sin \omega t$$

General Solution for RLC Circuit (2)

$$I_m \omega L \cos(\omega t - \phi) + I_m R \sin(\omega t - \phi) - \frac{I_m}{\omega C} \cos(\omega t - \phi) = \varepsilon_m \sin \omega t$$

→ Expand sin & cos expressions

$$\sin(\omega t - \phi) = \sin \omega t \cos \phi - \cos \omega t \sin \phi$$

$$\cos(\omega t - \phi) = \cos \omega t \cos \phi + \sin \omega t \sin \phi$$

} High school trig!

→ Collect $\sin \omega t$ & $\cos \omega t$ terms separately

$$(\omega L - 1/\omega C) \cos \phi - R \sin \phi = 0$$

$$I_m (\omega L - 1/\omega C) \sin \phi + I_m R \cos \phi = \varepsilon_m$$

} $\cos \omega t$ terms

} $\sin \omega t$ terms

→ These equations can be solved for I_m and ϕ (next slide)

General Solution for RLC Circuit (3)

→ Solve for ϕ and I_m

$$\tan \phi = \frac{\omega L - 1/\omega C}{R} \equiv \frac{X_L - X_C}{R} \quad I_m = \frac{\mathcal{E}_m}{Z}$$

→ R , X_L , X_C and Z have dimensions of resistance

$$X_L = \omega L$$

Inductive "reactance"

$$X_C = 1/\omega C$$

Capacitive "reactance"

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Total "impedance"

→ This is where ϕ , X_L , X_C and Z come from!

AC Source and RLC Circuits

$$I_m = \frac{\varepsilon_m}{Z}$$

Maximum current

$$\tan \phi = \frac{X_L - X_C}{R}$$

Phase angle

$$X_L = \omega L \quad (\omega = 2\pi f)$$


Inductive reactance

$$X_C = 1/\omega C$$

Capacitive reactance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Total impedance

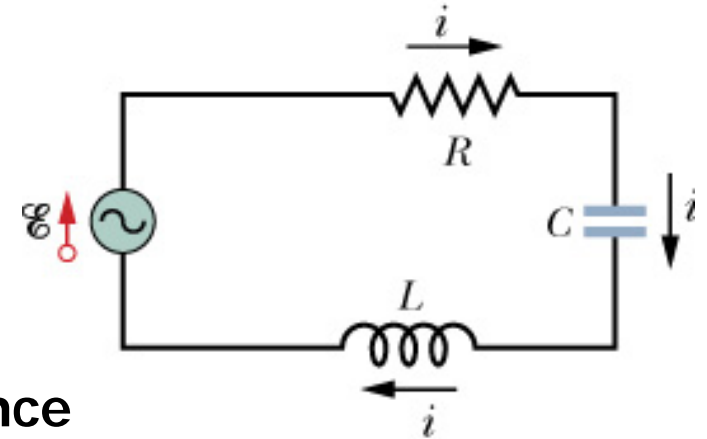

ϕ = angle that current "lags" applied voltage

What is Reactance?

Think of it as a frequency-dependent resistance

$$X_C = \frac{1}{\omega C}$$

Shrinks with increasing ω


$$X_L = \omega L$$

Grows with increasing ω

$$("X_R" = R)$$

Independent of ω

Pictorial Understanding of Reactance

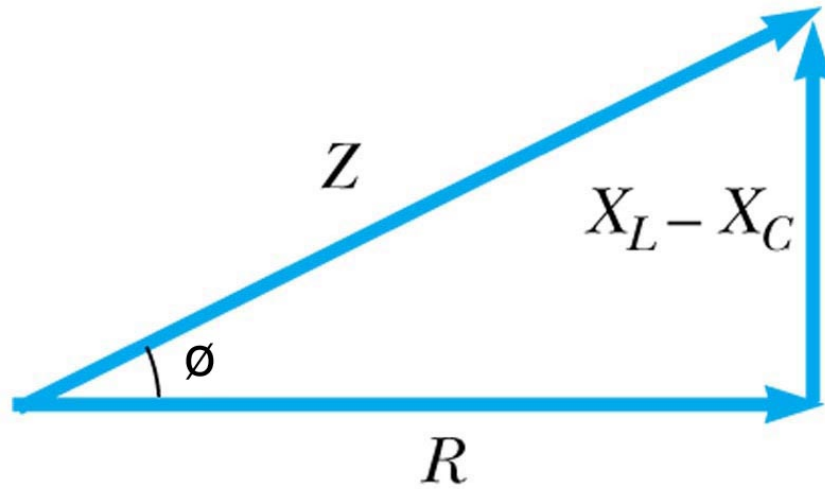

(c)

© 2003 Thomson - Brooks Cole

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\cos \phi = \frac{R}{Z}$$

Summary of Circuit Elements, Impedance, Phase Angles

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$



R

0°



X_C

-90°



X_L

$+90^\circ$




$$\sqrt{R^2 + X_C^2}$$

Negative,
between -90° and 0°



$$\sqrt{R^2 + X_L^2}$$

Positive,
between 0° and 90°

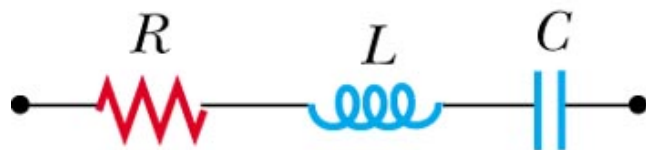

$$\sqrt{R^2 + (X_L - X_C)^2}$$

Negative if $X_C > X_L$
Positive if $X_C < X_L$

Quiz


→ Three identical EMF sources are hooked to a single circuit element, a resistor, a capacitor, or an inductor. The current amplitude is then measured as a function of frequency. Which one of the following curves corresponds to an inductive circuit?

◆ (1) a

◆ (2) b

◆ (3) c

◆ (4) Can't tell without more info

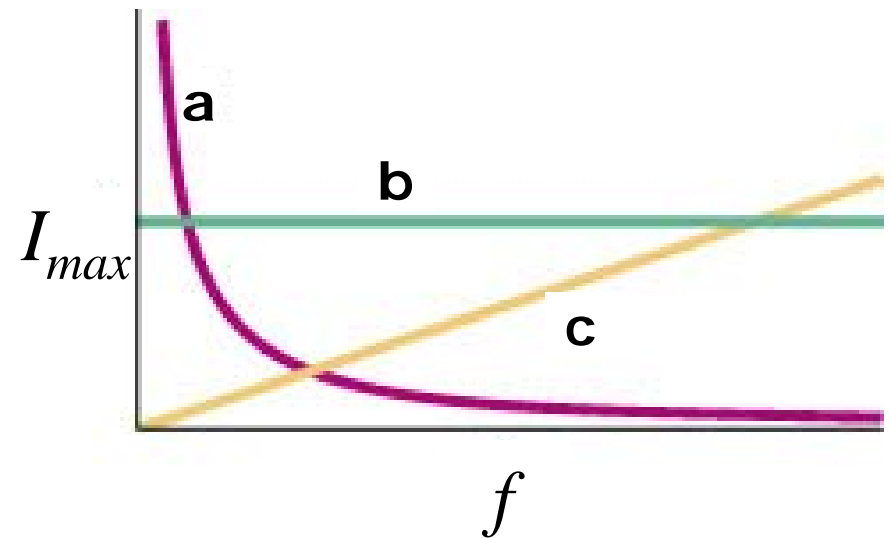

$$X_L = \omega L \quad (\omega = 2\pi f)$$


$$I_{max} = \varepsilon_{max} / X_L$$

For inductor, higher frequency gives higher reactance, therefore lower current

RLC Example 1

→ Below are shown the driving emf and current vs time of an RLC circuit. We can conclude the following

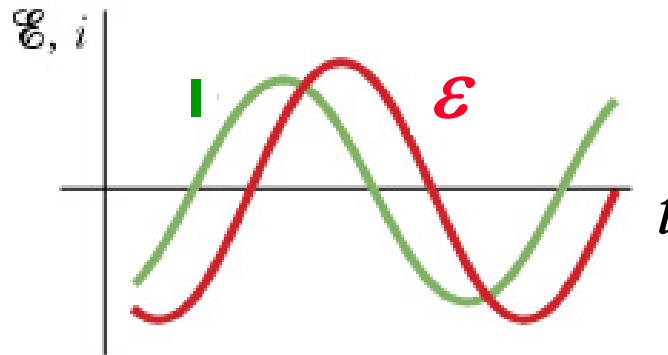- ◆ Current “leads” the driving emf ($\phi < 0$)
- ◆ Circuit is capacitive ($X_C > X_L$)



RLC Example 2

→ $R = 200\Omega$, $C = 15\mu\text{F}$, $L = 230\text{mH}$, $\varepsilon_{\text{max}} = 36\text{V}$, $f = 60\text{ Hz}$

◆ $X_L = 2\pi \times 60 \times 0.23 = 86.7\Omega$

◆ $X_C = 1 / (2\pi \times 60 \times 15 \times 10^{-6}) = 177\Omega$

◆ $Z = \sqrt{200^2 + (86.7 - 177)^2} = 219\Omega$

◆ $I_{\text{max}} = \varepsilon_{\text{max}} / Z = 36 / 219 = 0.164\text{ A}$

◆ $\phi = \tan^{-1} \left(\frac{86.7 - 177}{200} \right) = -24.3^\circ$

$X_C > X_L$
Capacitive circuit

Current leads emf
(as expected)

$$i = 0.164 \sin(\omega t + 24.3^\circ)$$

Resonance

→ Consider impedance vs frequency

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

→ Z is minimum when $\omega L = 1/\omega C$ $\omega = \omega_0 = 1/\sqrt{LC}$

◆ This is resonance!

→ At resonance

◆ Impedance = Z is minimum

◆ Current amplitude = I_m is maximum


I_{\max} vs Frequency and Resonance

→ Circuit parameters: $C = 2.5\mu\text{F}$, $L = 4\text{mH}$, $\varepsilon_{\max} = 10\text{v}$

◆ $f_0 = 1 / 2\pi(LC)^{1/2} = 1590\text{ Hz}$

◆ Plot I_{\max} vs f
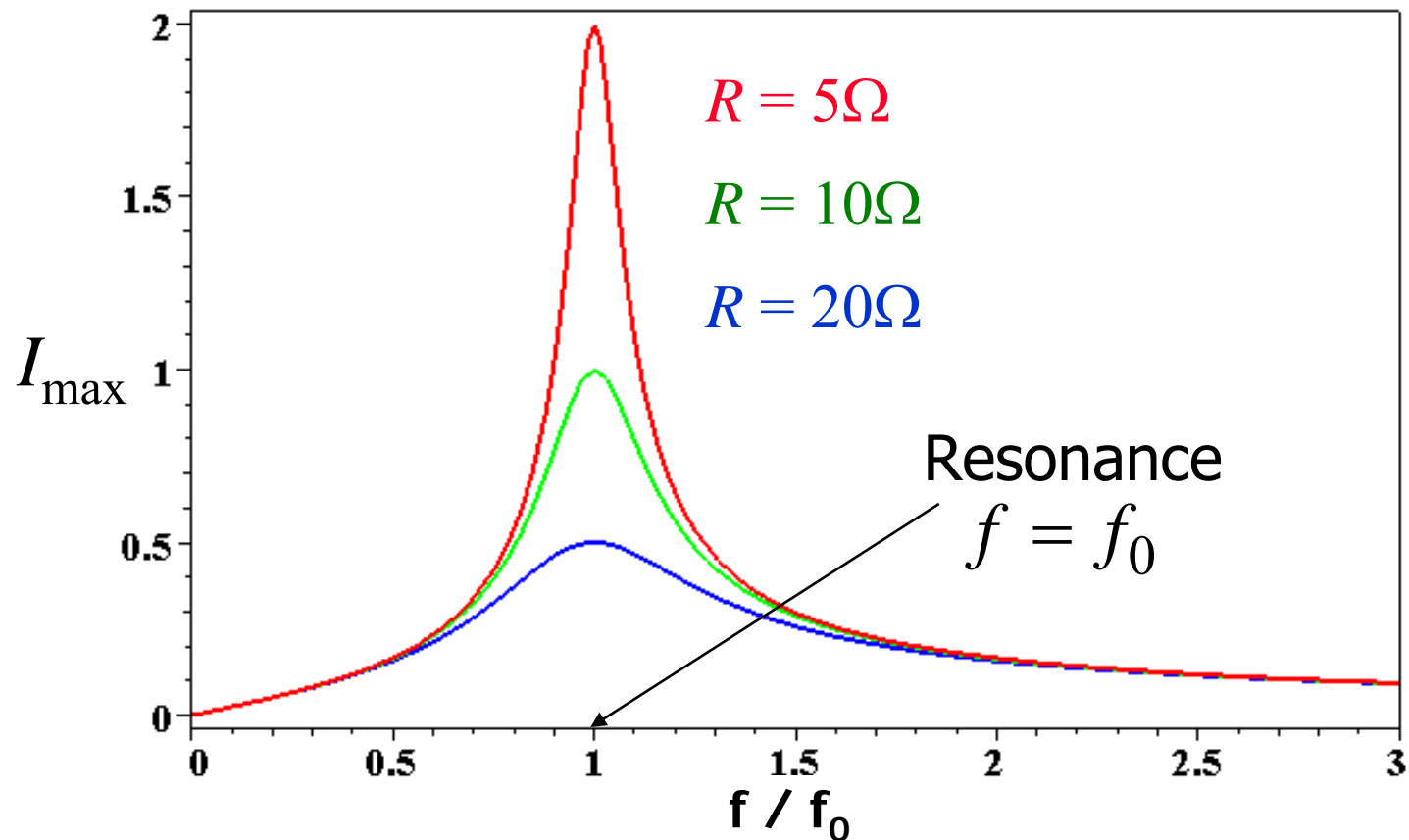
$$I_{\max} = 10 / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$



Power in AC Circuits

→ Instantaneous power emitted by circuit: $P = i^2 R$

$$P = I_m^2 R \sin^2(\omega_d t - \phi) \leftarrow \text{Instantaneous power oscillates}$$

→ More useful to calculate power averaged over a cycle

◆ Use $\langle \dots \rangle$ to indicate average over a cycle

$$\langle P \rangle = I_m^2 R \langle \sin^2(\omega_d t - \phi) \rangle = \frac{1}{2} I_m^2 R$$

→ Define RMS quantities to avoid $\frac{1}{2}$ factors in AC circuits

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$\mathcal{E}_{\text{rms}} = \frac{\mathcal{E}_m}{\sqrt{2}}$$

$$P_{\text{ave}} = I_{\text{rms}}^2 R$$

→ House current

$$\text{◆ } V_{\text{rms}} = 110\text{V} \Rightarrow V_{\text{peak}} = 156\text{V}$$


Power in AC Circuits

→ Power formula $P_{\text{ave}} = I_{\text{rms}}^2 R$ $I_{\text{rms}} = I_{\text{max}} / \sqrt{2}$

→ Rewrite using $I_{\text{rms}} = \frac{\mathcal{E}_{\text{rms}}}{Z}$ $P_{\text{ave}} = \frac{\mathcal{E}_{\text{rms}}}{Z} I_{\text{rms}} R = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi$

$$P_{\text{ave}} = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$\cos \phi = \frac{R}{Z}$$

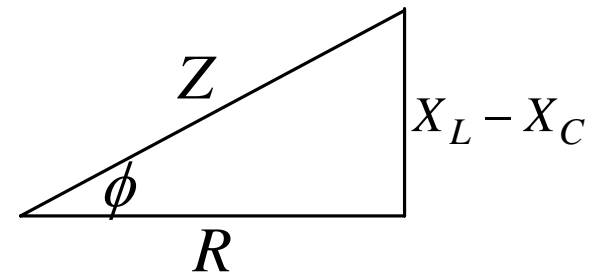

→ $\cos \phi$ is the "power factor"

- ◆ To maximize power delivered to circuit \Rightarrow make ϕ close to zero
- ◆ Max power delivered to load happens at resonance
- ◆ E.g., too much inductive reactance (X_L) can be cancelled by increasing X_C (e.g., circuits with large motors)

Power Example 1

→ $R = 200\Omega$, $X_C = 150\Omega$, $X_L = 80\Omega$, $\varepsilon_{\text{rms}} = 120\text{V}$, $f = 60\text{ Hz}$

◆ $Z = \sqrt{200^2 + (80 - 150)^2} = 211.9\Omega$

◆ $I_{\text{rms}} = \varepsilon_{\text{rms}} / Z = 120 / 211.9 = 0.566\text{ A}$

◆ $\phi = \tan^{-1}\left(\frac{80 - 150}{200}\right) = -19.3^\circ$ ← Current leads emf
Capacitive circuit

◆ $\cos \phi = 0.944$

◆ $P_{\text{ave}} = \varepsilon_{\text{rms}} I_{\text{rms}} \cos \phi = 120 \times 0.566 \times 0.944 = 64.1\text{ W}$

◆ $P_{\text{ave}} = I_{\text{rms}}^2 R = 0.566^2 \times 200 = 64.1\text{ W}$

} Same

Power Example 1 (cont)

→ $R = 200\Omega$, $X_C = 150\Omega$, $X_L = 80\Omega$, $\varepsilon_{\text{rms}} = 120\text{V}$, $f = 60\text{ Hz}$

→ How much capacitance must be added to maximize the power in the circuit (and thus bring it into resonance)?

◆ Want $X_C = X_L$ to minimize Z , so must decrease X_C

$$\text{◆ } X_C = 150\Omega = 1/2\pi fC \qquad C = 17.7\mu\text{F}$$

$$\text{◆ } X_{C_{\text{new}}} = X_L = 80\Omega \qquad C_{\text{new}} = 33.2\mu\text{F}$$


◆ So we must add $15.5\mu\text{F}$ capacitance to maximize power

Power vs Frequency and Resonance

→ Circuit parameters: $C = 2.5\mu\text{F}$, $L = 4\text{mH}$, $\varepsilon_{\text{max}} = 10\text{v}$


◆ $f_0 = 1 / 2\pi(LC)^{1/2} = 1590\text{ Hz}$

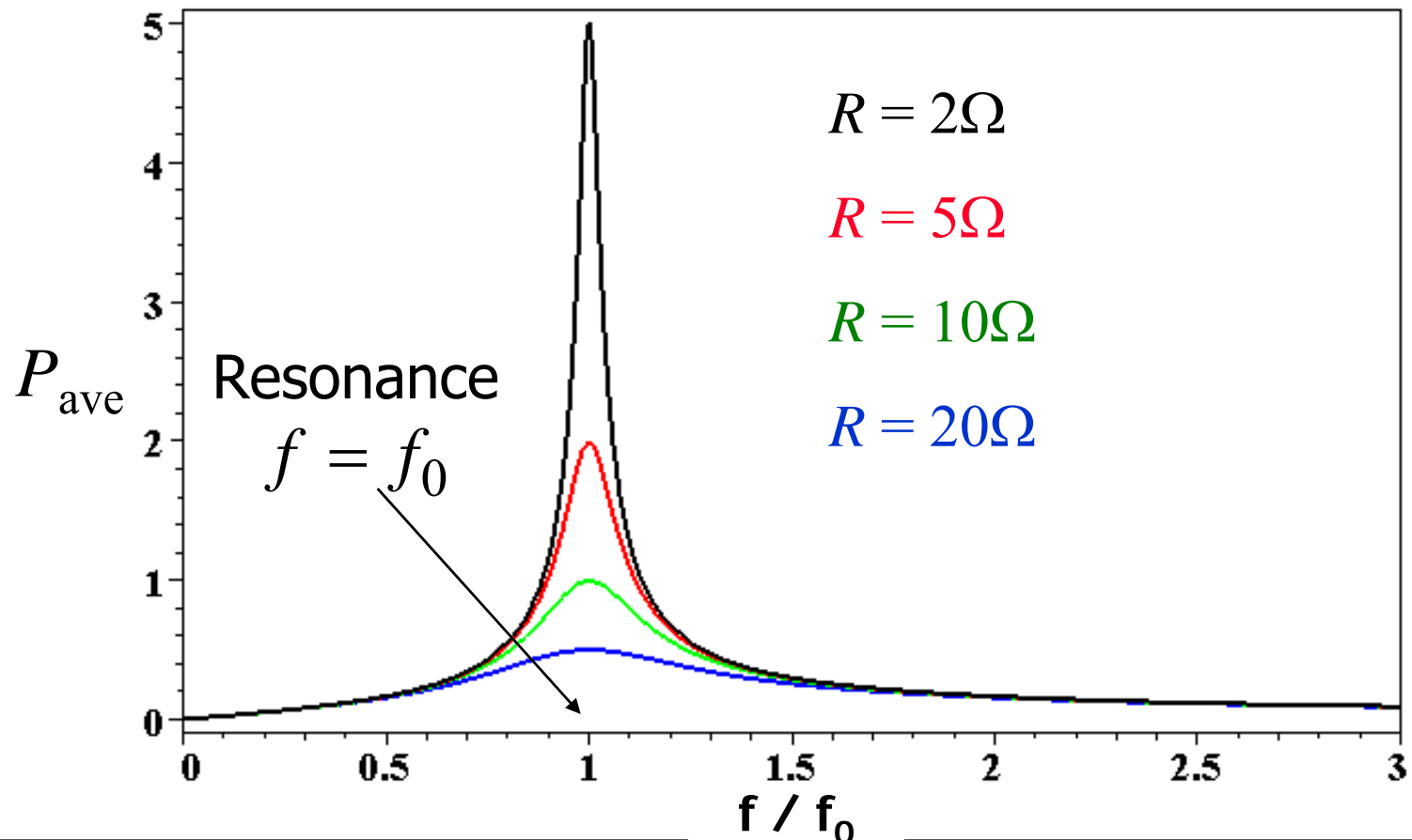◆ Plot P_{ave} vs f for different R values



Resonance Tuner is Based on Resonance

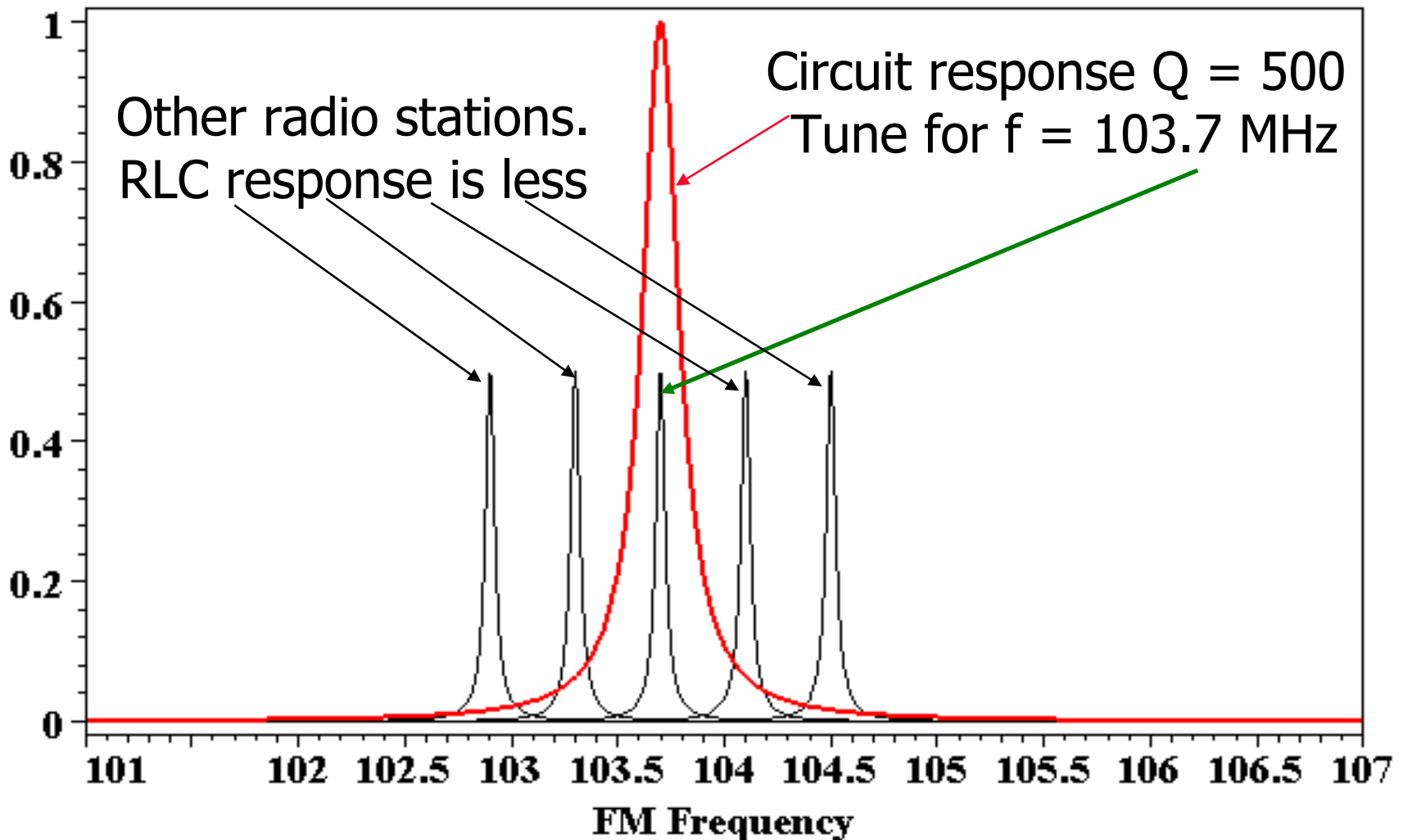Vary C to set resonance frequency to 103.7 (ugh!)



Quiz

→ A generator produces current at a frequency of 60 Hz with peak voltage and current amplitudes of 100V and 10A, respectively. What is the average power produced if they are in phase?

◆ (1) 1000 W

◆ (2) 707 W

◆ (3) 1414 W

◆ (4) 500 W

◆ (5) 250 W

$$P_{\text{ave}} = \frac{1}{2} \varepsilon_{\text{peak}} I_{\text{peak}} = \varepsilon_{\text{rms}} I_{\text{rms}}$$

Quiz

→ The figure shows the current and emf of a series RLC circuit. To increase the rate at which power is delivered to the resistive load, which option should be taken?


◆ (1) Increase R

◆ (2) Decrease L

◆ (3) Increase L

◆ (4) Increase C

$$\tan \phi = \frac{X_L - X_C}{R}$$

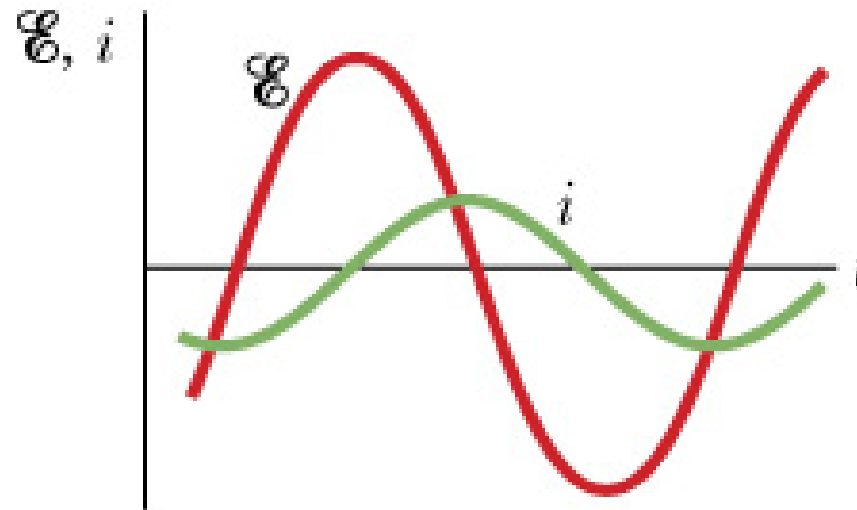

Current lags applied emf ($\phi > 0$), thus circuit is inductive. Either
(1) Reduce X_L by decreasing L or
(2) Cancel X_L by increasing X_C (decrease C).

Example: LR Circuit

→ Variable frequency EMF source with $\varepsilon_m = 6\text{V}$ connected to a resistor and inductor. $R = 80\Omega$ and $L = 40\text{mH}$.

◆ At what frequency f does $V_R = V_L$?

$$X_L = \omega L = R \Rightarrow \omega = 2000 \quad f = 2000 / 2\pi = 318\text{Hz}$$

◆ At that frequency, what is phase angle ϕ ?

$$\tan \phi = X_L / R = 1 \Rightarrow \phi = 45^\circ$$

◆ What is the current amplitude and RMS value?

$$I_{\text{max}} = \varepsilon_{\text{max}} / \sqrt{80^2 + 80^2} = 6 / 113 = 0.053\text{A}$$

$$I_{\text{rms}} = I_{\text{max}} / \sqrt{2} = 0.037\text{A}$$


$$i = 0.053 \sin(\omega t - 45^\circ)$$

Transformers

→ Purpose: change alternating (AC) voltage to a bigger (or smaller) value

Input AC voltage in the "primary" turns produces a flux
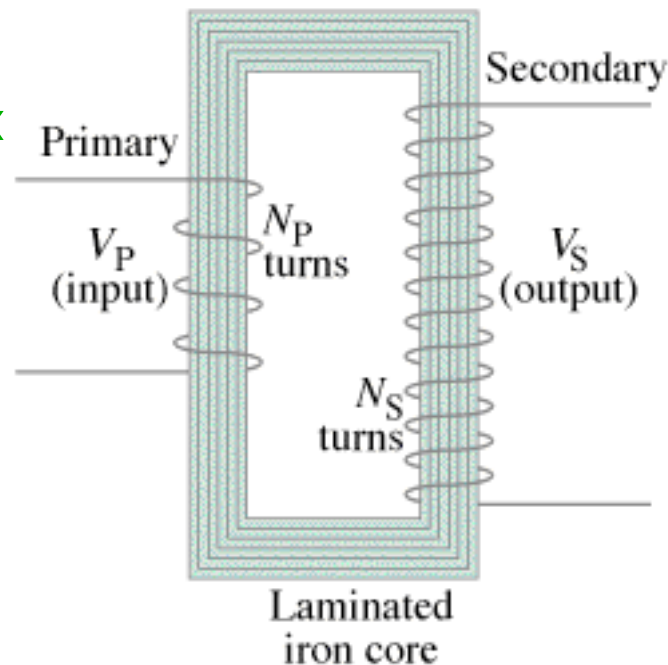
$$V_p = N_p \frac{\Delta\Phi_B}{\Delta t}$$



Changing flux in "secondary" turns induces an emf

$$V_s = N_s \frac{\Delta\Phi_B}{\Delta t}$$

$$V_s = V_p \frac{N_s}{N_p}$$


Transformers

→ Nothing comes for free, however!

- ◆ Increase in voltage comes at the cost of current.
- ◆ Output power cannot exceed input power!
- ◆ power in = power out
- ◆ (Losses usually account for 10-20%)

$$i_p V_p = i_s V_s$$
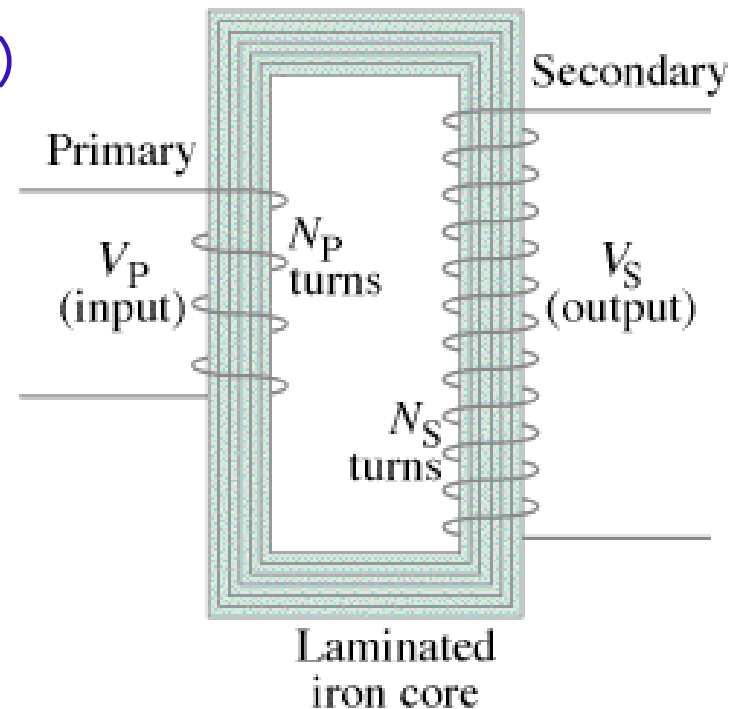
$$\frac{i_s}{i_p} = \frac{V_p}{V_s} = \frac{N_p}{N_s}$$



Transformers: Sample Problem


→ A transformer has 330 primary turns and 1240 secondary turns. The input voltage is 120 V and the output current is 15.0 A. What is the output voltage and input current?

$$V_s = V_p \frac{N_s}{N_p} = 120 \left(\frac{1240}{330} \right) = 451 \text{ V}$$


“Step-up”
transformer

$$i_p V_p = i_s V_s \quad \longrightarrow \quad i_p = i_s \frac{V_s}{V_p} = 15 \left(\frac{451}{120} \right) = 56.4 \text{ A}$$

Transformers


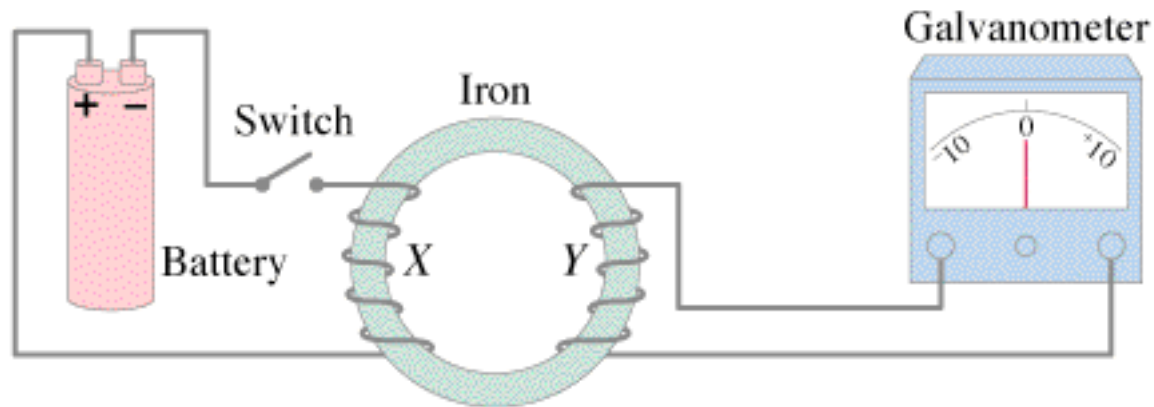


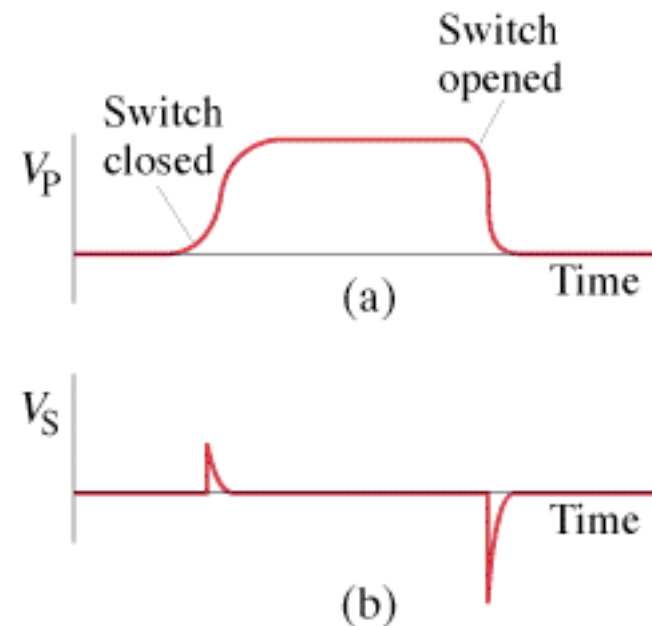- This is how first experiment by Faraday was done
- He only got a deflection of the galvanometer when the switch is opened or closed
- Steady current does not make induced emf.



Applications

Microphone

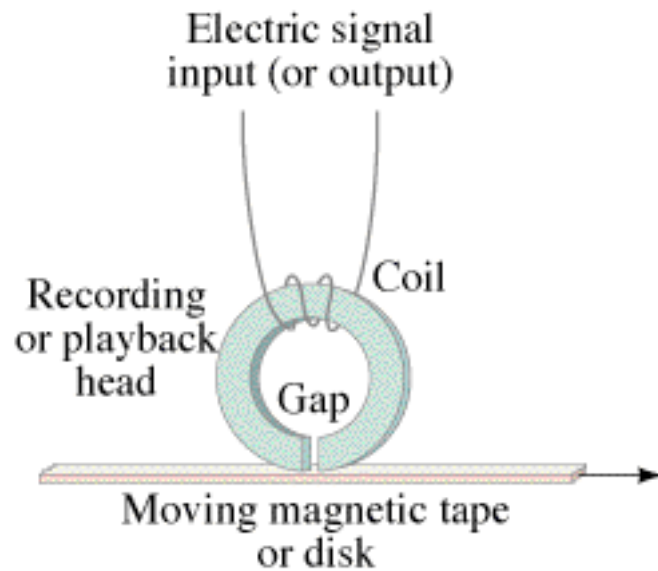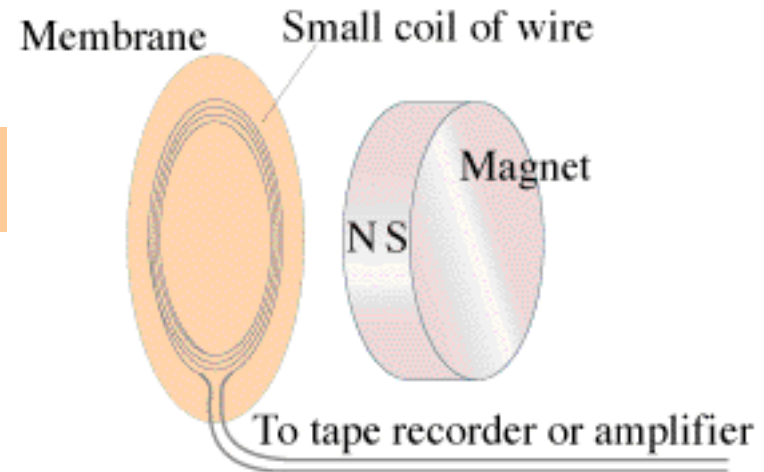

Tape recorder


ConcepTest: Power lines

→ At large distances, the resistance of power lines becomes significant. To transmit maximum power, is it better to transmit (high V , low i) or (high i , low V)?

- ◆ (1) high V , low i
- ◆ (2) low V , high i
- ◆ (3) makes no difference

Power loss is i^2R

Electric Power Transmission

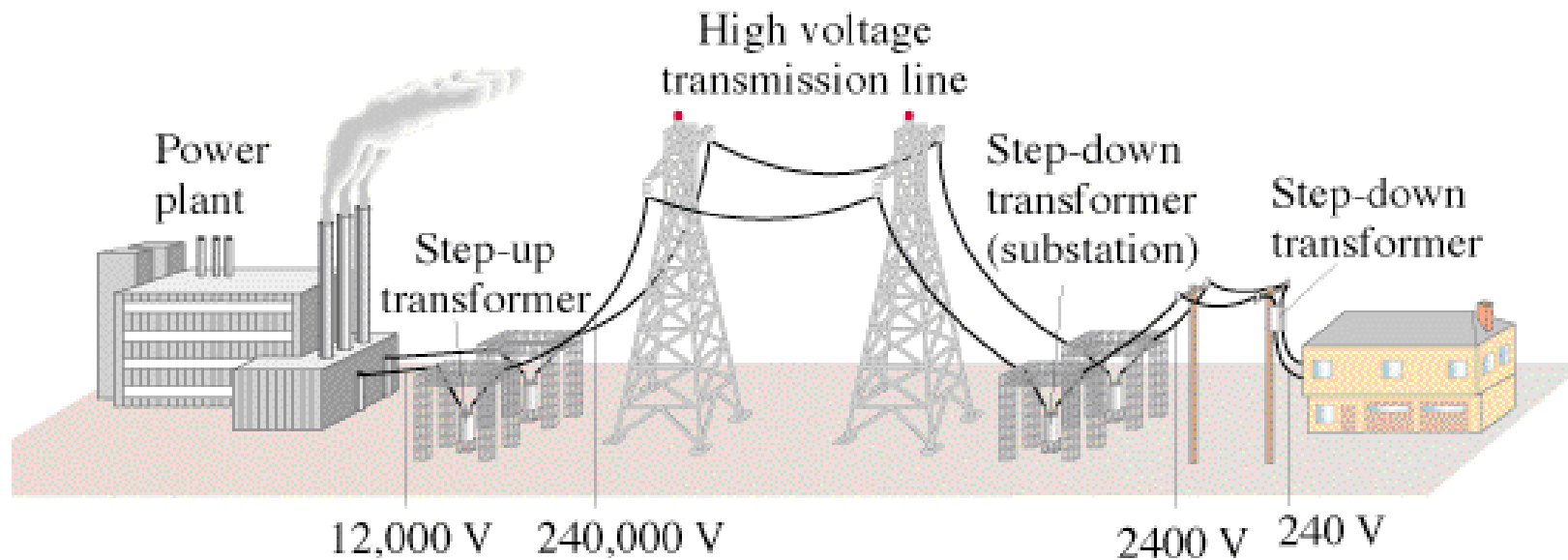

i^2R : 20x smaller current \Rightarrow 400x smaller power loss