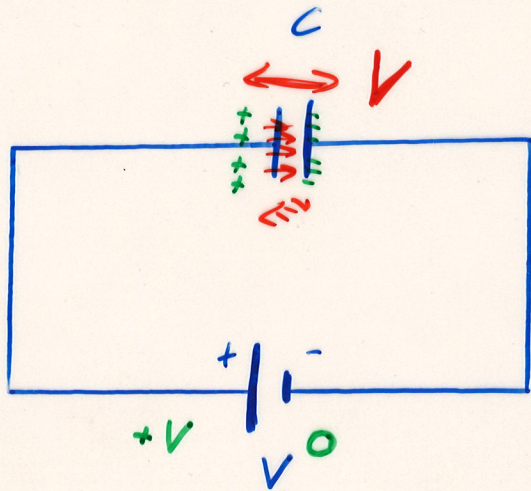



Circuits


In a circuit containing batteries and capacitors, current flows until all of the capacitors are fully charged. Then no more current flows. This is the steady state. The current is not changing; it is zero (a constant).



$i = 0$
Steady State


Capacitors in Series

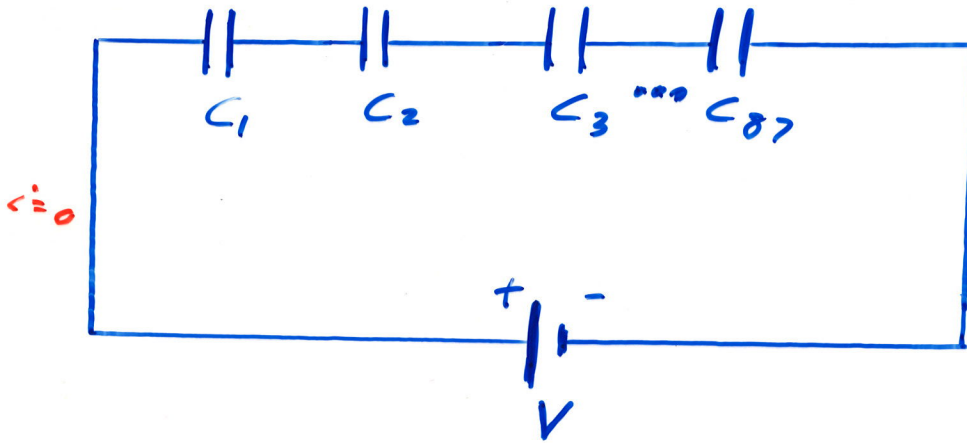

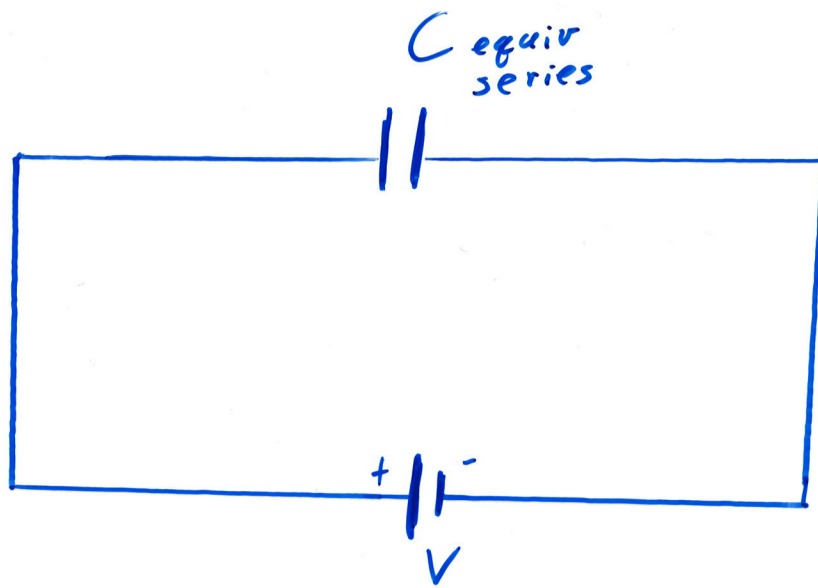

$$\frac{1}{C_{\text{equiv series}}} = \sum_{i=1}^N \frac{1}{C_i}$$

Capacitors in Parallel

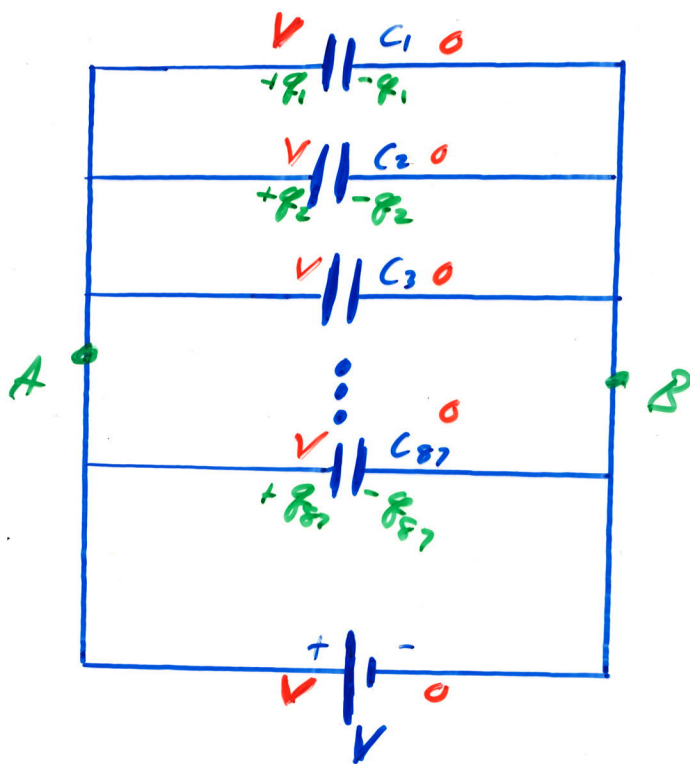

$$Q_1 = C_1 V_1$$
$$Q_2 = C_2 V_2$$

⋮

$$V_1 = V_2 = \dots = V_n = V_{\text{battery}} = V$$


Total charge held by all capacitors

$$Q_{\text{TOT}} = Q_1 + Q_2 + \dots + Q_n$$

$$= C_1 V_1 + C_2 V_2 + \dots + C_n V_n$$

$$= (C_1 + C_2 + \dots + C_n) V$$
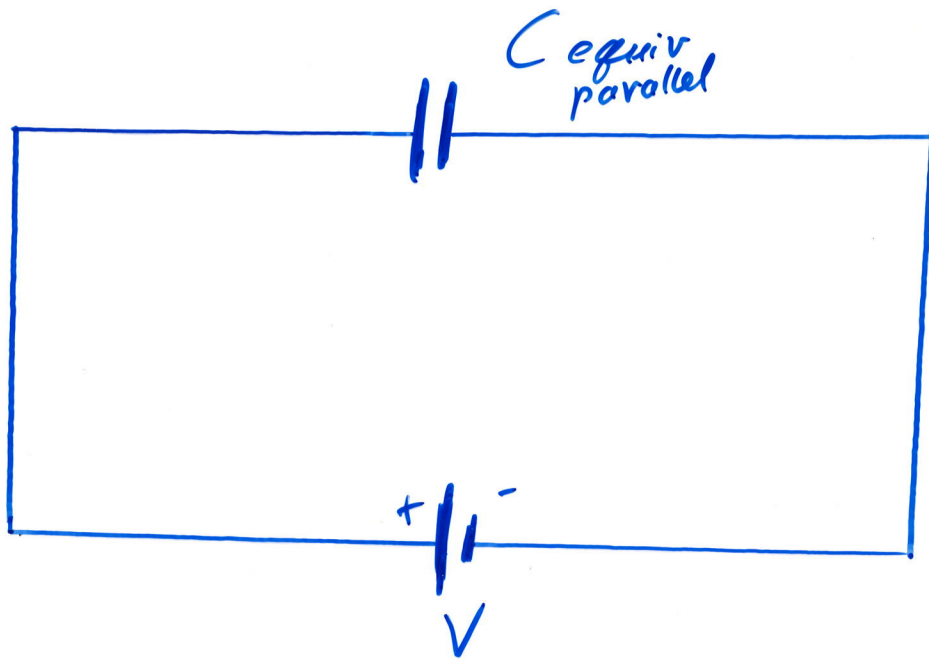
$$Q_{\text{TOT}} = C_{\text{equiv parallel}} V$$



$$C_{\text{equiv parallel}} = \sum_{i=1}^N C_i$$

What idea did we use?

The potential difference between two points, A and B, in the circuit can be obtained by following any path through the circuit.


Kirchhoff's Loop Rule:

The algebraic sum of the changes in potential encountered in a complete traversal of any circuit must be zero.

Now consider circuits containing batteries and resistors, but **no capacitors**. In the steady state, a non-zero constant current flows through the circuit forever.


$$V = iR$$


"Ohm's Law"

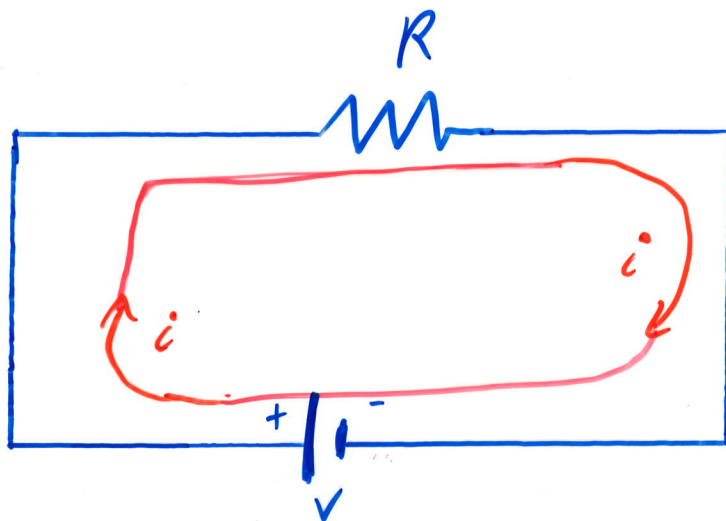

The current must be the same on both sides of the resistor because charge can not "pile up" anywhere in the circuit.

Resistors in Series

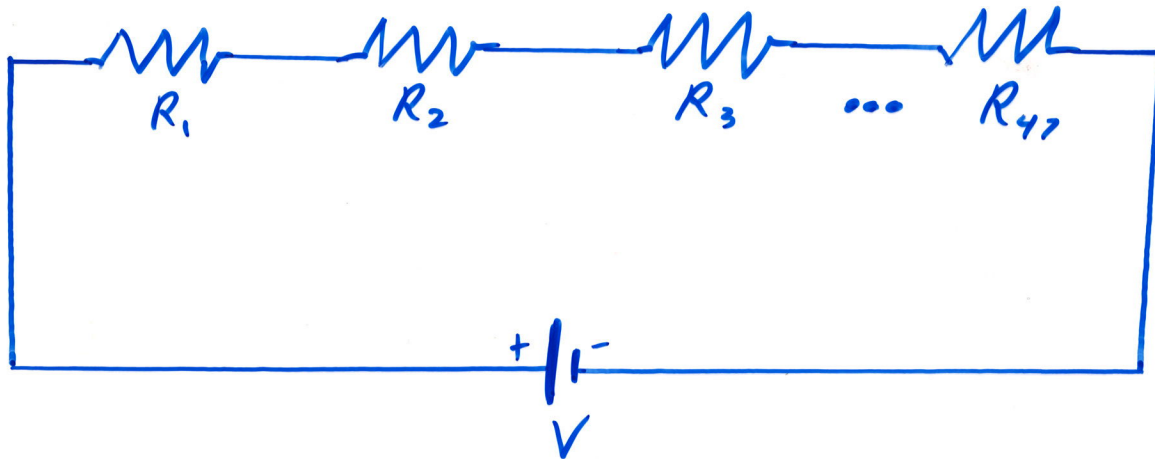

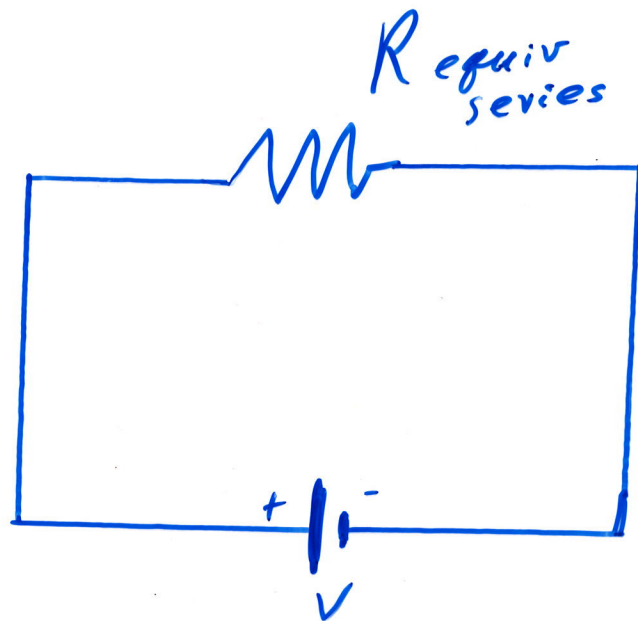



$$R_{\text{equiv series}} = \sum_{i=1}^N R_i$$

loads like

$$C_{\text{equiv parallel}} = \sum_{i=1}^N C_i$$

Resistors in Parallel

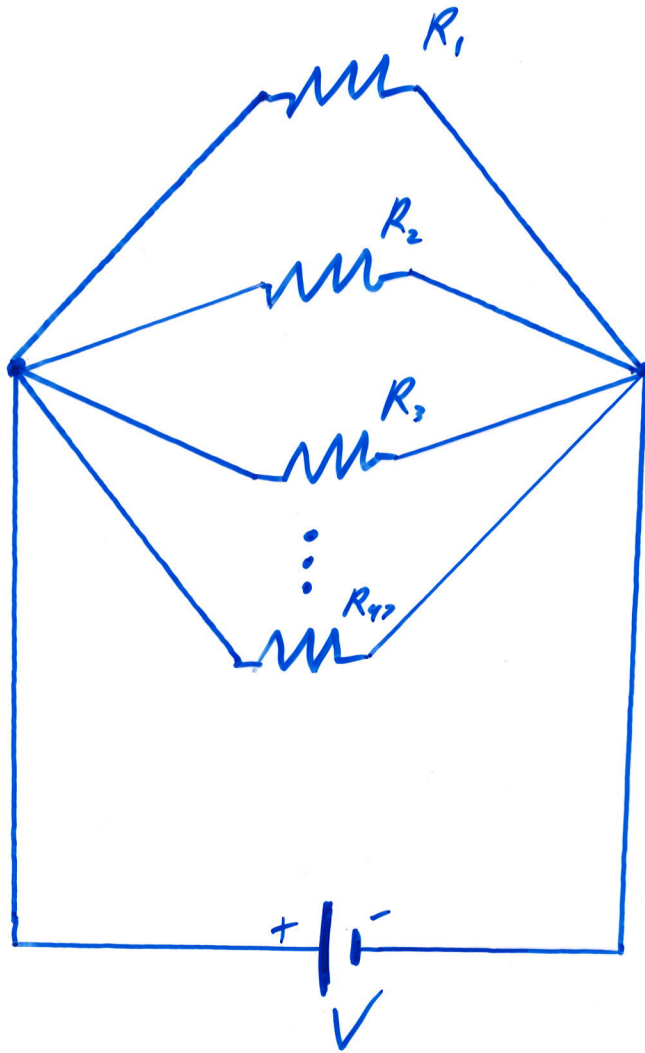

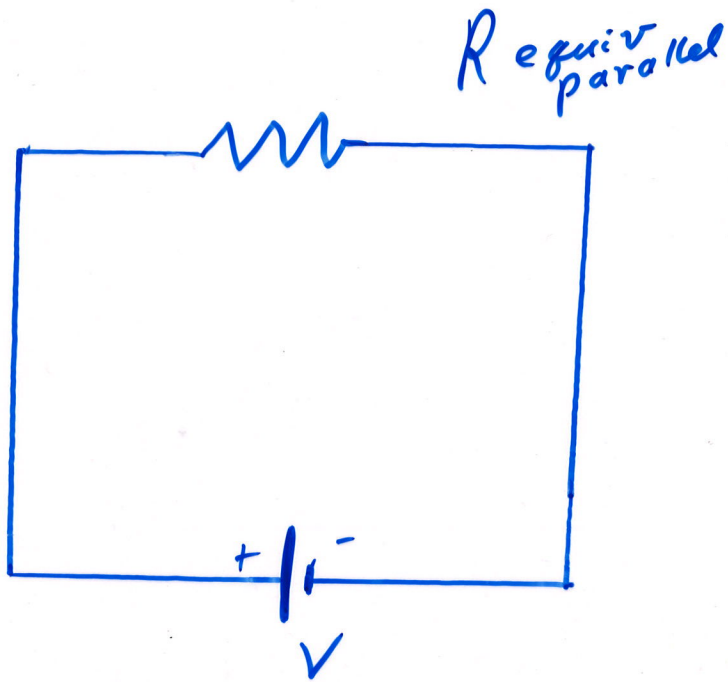

$$\frac{1}{R_{\text{equiv parallel}}} = \sum_{i=1}^N \frac{1}{R_i}$$

looks like

$$\frac{1}{C_{\text{equiv series}}} = \sum_{i=1}^N \frac{1}{C_i}$$

What principle did we use
this time?


Electric charge is conserved,
so it can't "pile up" anywhere
in the circuit. Whatever charge
flows into a junction must flow
out.

Kirchhoff's Junction Rule:

The sum of the currents
approaching any junction must
be equal to the sum of the
currents leaving that junction.


Steady state: Charge Conservation
implies Current Conservation

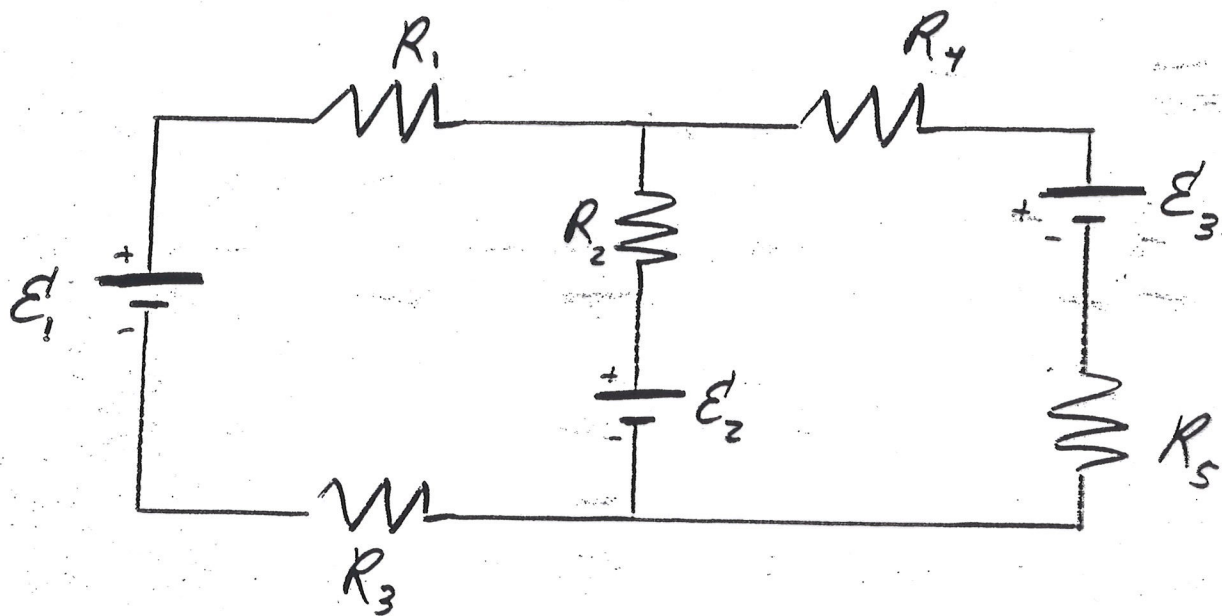Circuits containing more than one Battery



Circuits containing more than one Battery

P. 800

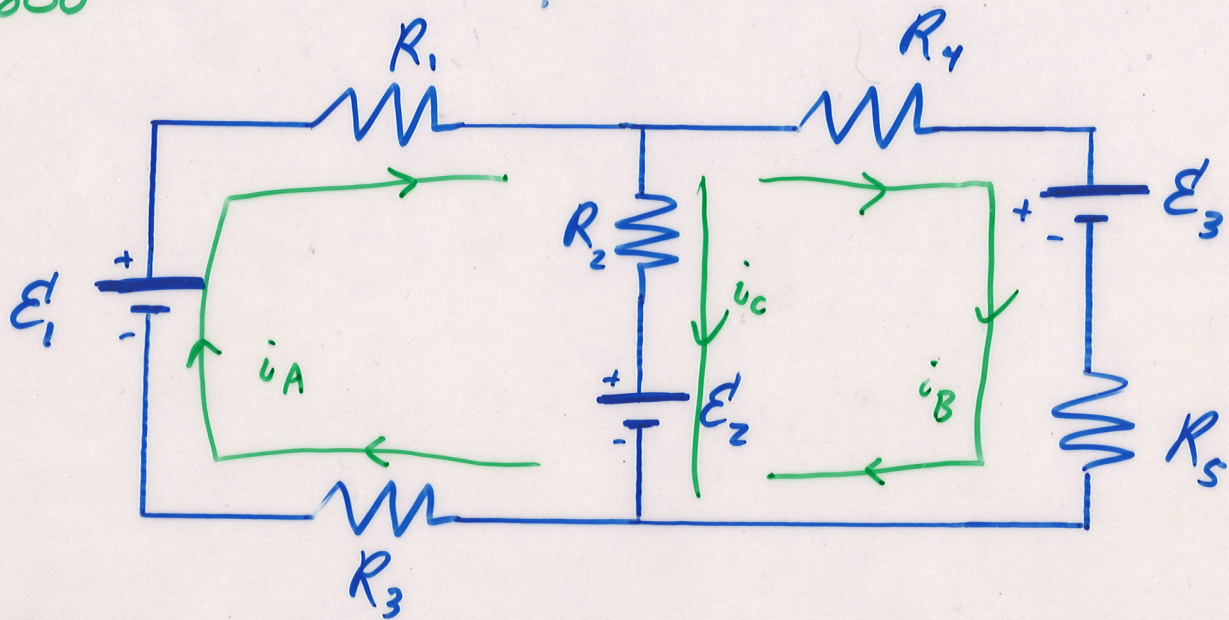

- 1) Try to reduce the circuit by replacing R 's in series and R 's in parallel with their equivalents.
- 2) Draw currents with directions.
- 3) Kirchhoff's Junction Rule
- 4) Kirchhoff's Loop Rule
- 5) Solve same number of simultaneous equations.


None of the resistors are in series or parallel. Now what?

series \rightarrow same current

parallel \rightarrow same voltage


RC Circuits

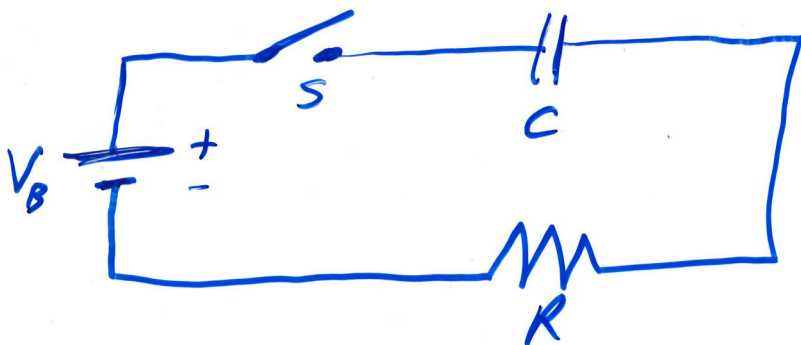Circuits containing a Resistor, a Capacitor, and possibly a battery, in series.



If you wait long enough, the steady state is boring: $i = 0$.

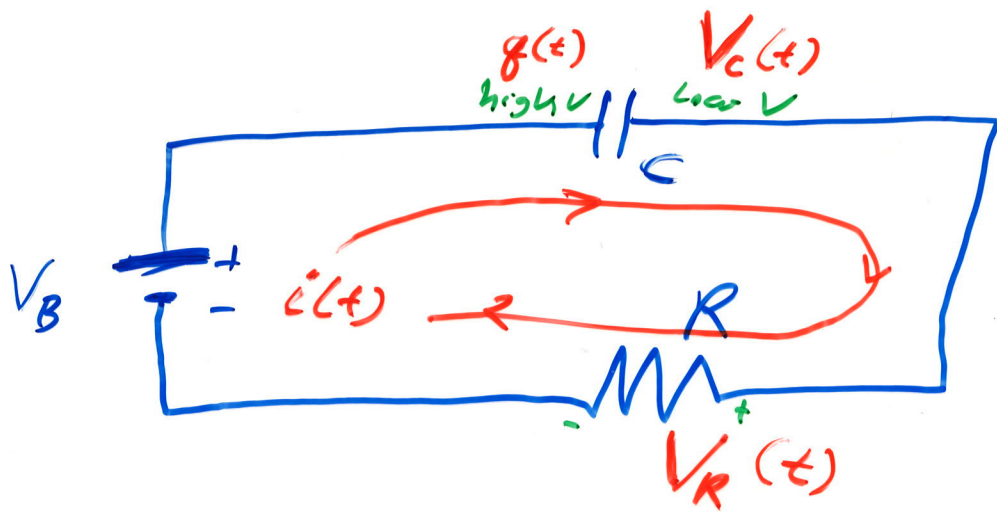But this is our first opportunity to study a *time-dependent* current $i(t)$.



At any time t , Kirchhoff's Loop Rule

gives:

$$0 = V_B - V_C(t) - V_R(t)$$

$$0 = V_B - \frac{q(t)}{C} - i(t)R$$

$$q(t) = C V_C(t)$$

$$V_R(t) = i(t)R$$

but the current is the time rate of change of the charge!

$$i(t) = \frac{d}{dt} [q(t)]$$

This is a differential equation.

A solution will tell you the charge at any time. That is, the solution is not a number, but rather a function of time $q(t)$.

$$0 = V_B - \frac{q(t)}{C} - R \frac{d}{dt}[q(t)]$$

Guess:

Try a solution of the form:

$$q(t) = A e^{-t/RC} + B$$

↖ constants ↗

$$i(t) = \frac{d}{dt}[q(t)] = -\frac{A}{RC} e^{-t/RC}$$

$$\frac{d}{dt} e^{-\frac{t}{z}} = \left(-\frac{1}{z}\right) e^{-\frac{t}{z}}$$

where z is a constant

Substitute :

$$0 = V_B - \frac{Ae^{-t/RC} + B}{C} + R \left[\frac{-A}{RC} e^{-t/RC} \right]$$

$$0 = V_B - \underbrace{\frac{A}{C} e^{-t/RC}} - \frac{B}{C} + \underbrace{\frac{A}{C} e^{-t/RC}}$$

$$V_B = \frac{B}{C} \Rightarrow B = CV_B$$

"A" is still not fixed

$$q(t) = A e^{-t/RC} + CV_B$$

Fix A with a so-called

boundary condition : the charge on the capacitor at $t=0$ is zero.

The capacitor is neutral before the switch is closed.

$$q(0) = 0$$

$$0 = q(0) = A e^{-\frac{0}{RC}} + C V_B = A + C V_B$$

$$\Rightarrow A = -C V_B = -B$$

Solution:

$$q(t) = C V_B (1 - e^{-t/RC})$$

$$i(t) = \frac{d}{dt}[q(t)] = \frac{C V_B}{RC} e^{-t/RC} = \frac{V_B}{R} e^{-t/RC}$$

$$V_C(t) = \frac{q(t)}{C} = V_B (1 - e^{-t/RC})$$

$$V_R(t) = i(t)R = V_B e^{-t/RC}$$

Check the solution!

$$0 \stackrel{?}{=} V_B - V_C(t) - V_R(t)$$

$$= \underline{V_B} - \underline{V_B(1 - e^{-t/RC})} - \underline{V_B e^{-t/RC}} = 0 \quad \checkmark$$

Consider some special times:


$t=0$

$$q(0) = 0$$
$$i(0) = \frac{V_B}{R}$$

$$V_C(0) = 0$$

$$V_R(0) = V_B$$

What does this mean?

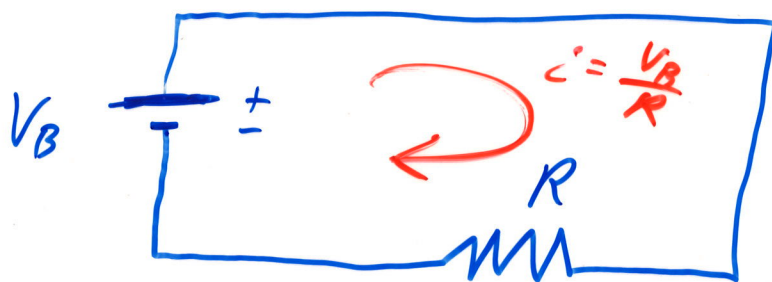

no capacitor!


$t=\infty$

$$q(\infty) = C V_B$$
$$i(\infty) = 0$$

$$V_C(\infty) = V_B$$

$$V_R(\infty) = 0$$

What does this mean?

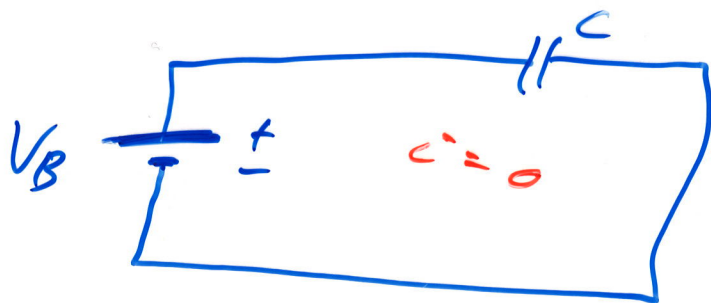

no resistor!

Capacitive Time Constant

RC has the dimension of time

$$[RC] = T$$

In MKS units: $1 \Omega \cdot F = 1 \text{ second}$

In the time RC , the charge on the capacitor has increased from


$$q(0) = 0 \quad \text{to}$$

$$q(RC) = CV_B \left(1 - e^{-\frac{RC}{RC}}\right)$$



$$= CV_B (1 - e^{-1})$$

$$\approx 63\% CV_B$$

that is 63% of its fully charged value.

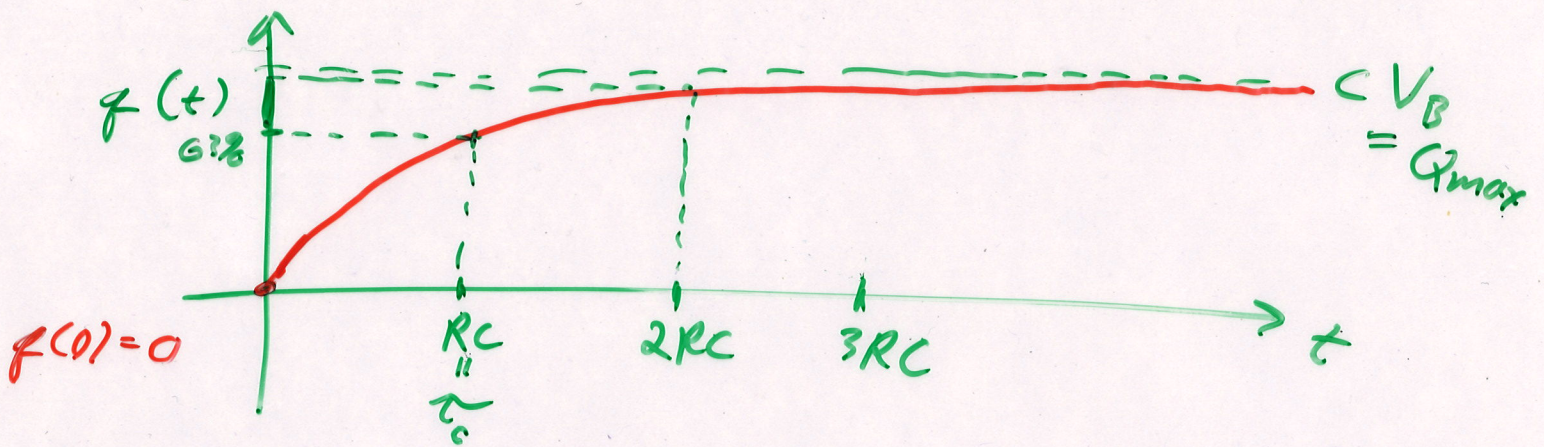
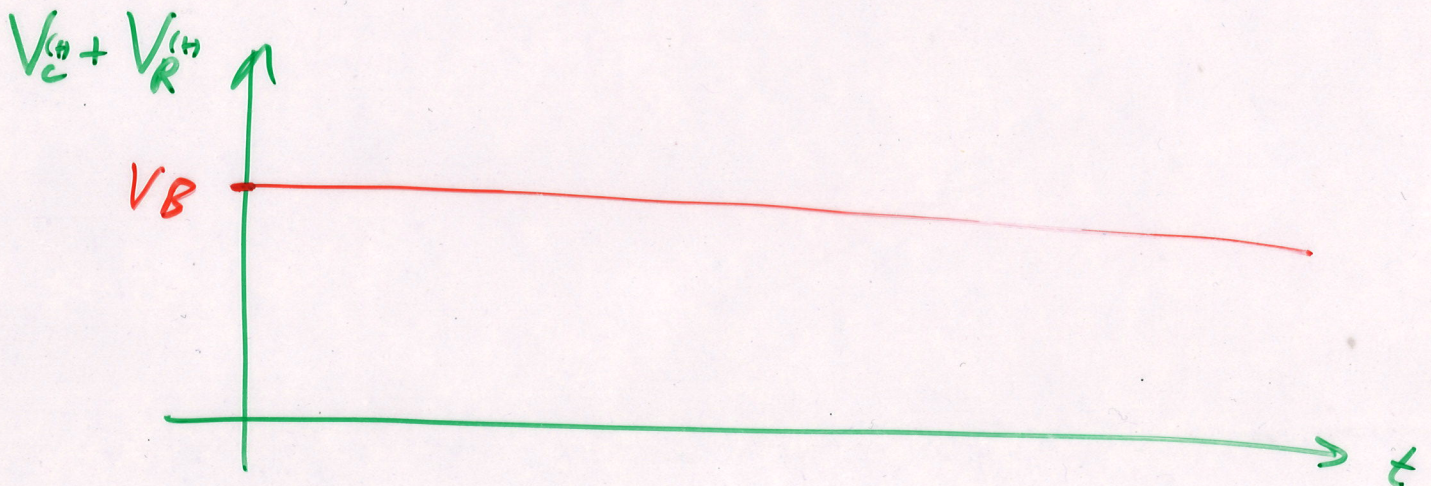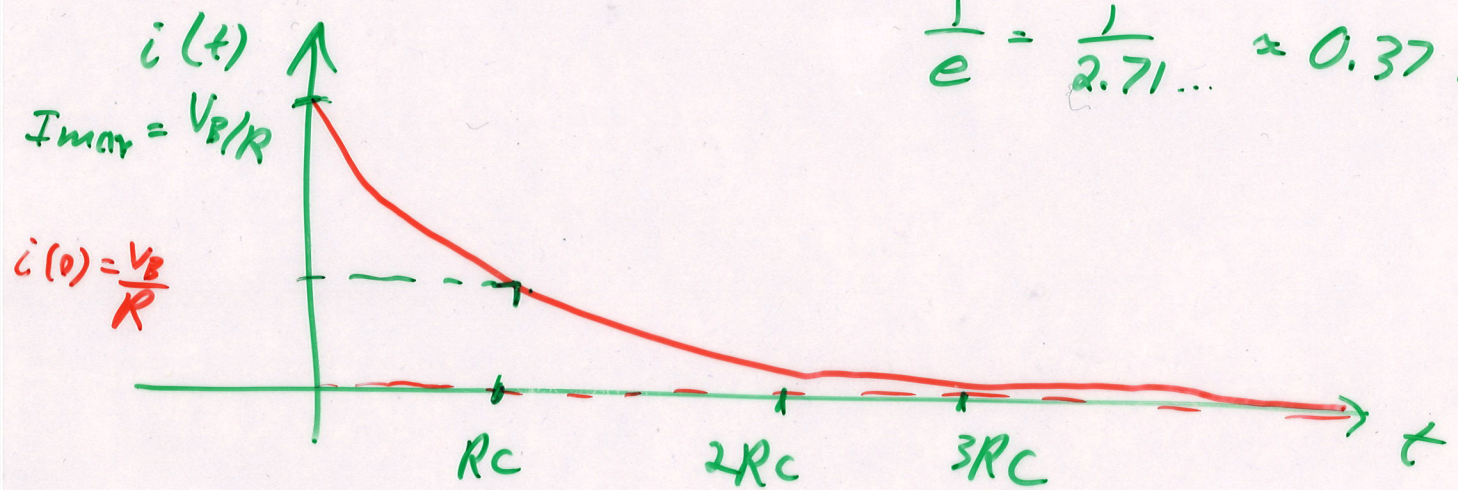
$$\frac{1}{e} = \frac{1}{2.71...} \approx 0.37 = 37\%$$



Capacitors easily pass
changing currents (they block
steady currents)

Filter (Surge Protector)

