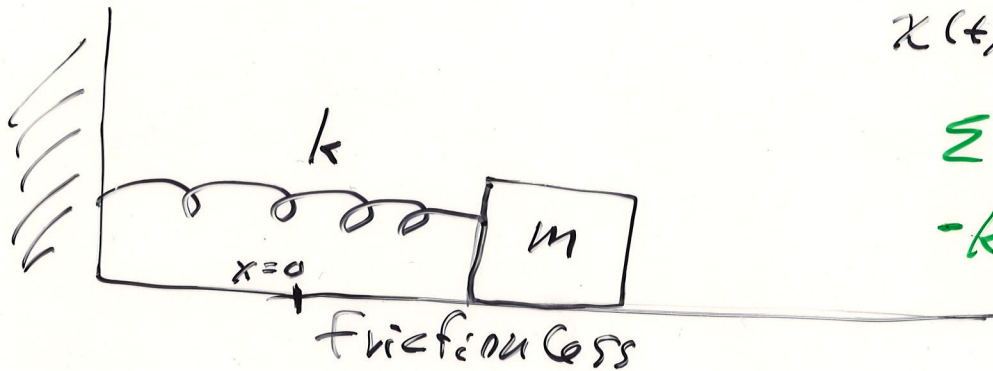


A trip down memory lane



$$x(t), v(t)$$

$$\Sigma F_x = m a_x$$

$$-kx = m \frac{d^2 x}{dt^2}$$

$$\frac{d^2 x}{dt^2} + \frac{k}{m} x = 0$$

Differential equation

$$X \quad x(t) = 3t^2 + 5$$

$$\frac{dx}{dt} = v(t) = 6t$$

$$\frac{d^2 x}{dt^2} = a(t) = 6$$

$$6 + \frac{k}{m}(3t^2 + 5) = 0$$

must be true at all times

$$x(t) = A \sin(\omega t + \varphi)$$

↔ arbitrary ↔

$$v(t) = \frac{dx}{dt} = A\omega \cos(\omega t + \varphi)$$

$$a(t) = \frac{dv}{dt} = \frac{d^2 x}{dt^2} = -A\omega^2 \sin(\omega t + \varphi)$$

$$-A\omega^2 \sin(\omega t + \varphi) + \frac{k}{m} A \sin(\omega t + \varphi) = 0$$

$$\omega = \sqrt{\frac{k}{m}}$$

ω is angular frequency
units of $\frac{\text{rad}}{\text{s}} \rightarrow \text{MKS}$

f is linear frequency
unit of $\text{Hz} = \frac{1}{\text{sec}} = \frac{\text{cycles}}{\text{sec}} = \frac{\text{rev}}{\text{sec}}$


$$f = \frac{\omega}{2\pi}$$

T is period of oscillation

$$f = \frac{1}{T}$$

$$T = \frac{2\pi}{\omega}$$

Deja vu all over again

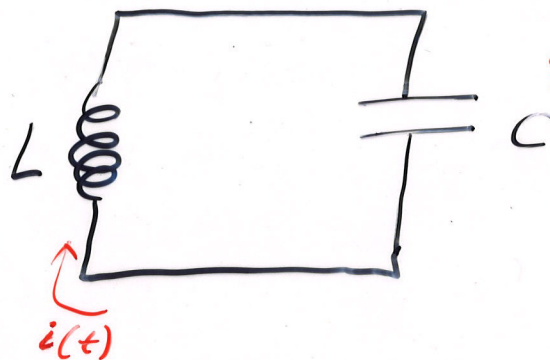

$$q = CV$$

$$V = \frac{q}{C}$$

$$i(t) = \frac{dq}{dt}$$

$$\frac{di}{dt} = \frac{d^2q}{dt^2}$$

Kirchhoff's Loop Rule

$$V_C + V_L = 0$$

$$\frac{q(t)}{C} + L \frac{di}{dt} = 0$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC} q = 0$$

solution: $q(t) = A \cos(\omega t + \phi)$

$$i(t) = \frac{dq}{dt} = -A\omega \sin(\omega t + \phi)$$

$$\frac{di}{dt} = \frac{d^2q}{dt^2} = -A\omega^2 \cos(\omega t + \phi)$$

$$= -\omega^2 q(t)$$

$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$


$$-\omega^2 q^{(+)} + \frac{1}{LC} q^{(+)} = 0$$

$$\Rightarrow \omega = \sqrt{\frac{1}{LC}}$$

natural angular
frequency


$$[\omega] = \frac{1}{T} \quad \text{units} \quad \frac{\text{rad}}{\text{s}}$$

$x(t), v(t)$


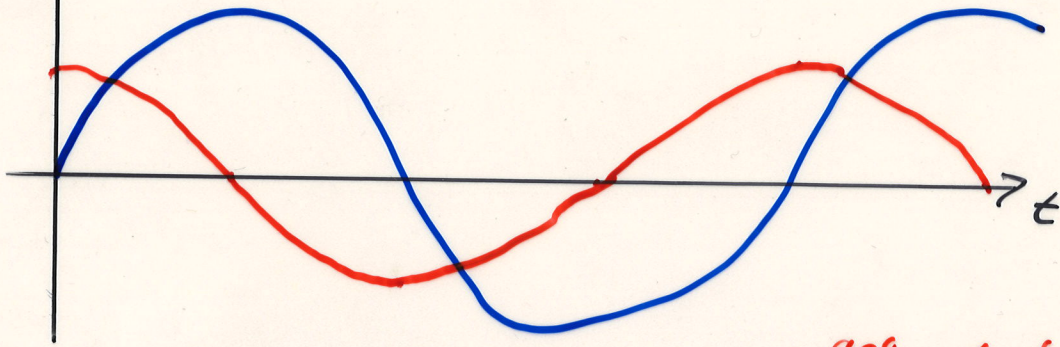


90° out of phase

$V_c(t), \dot{i}_L(t)$

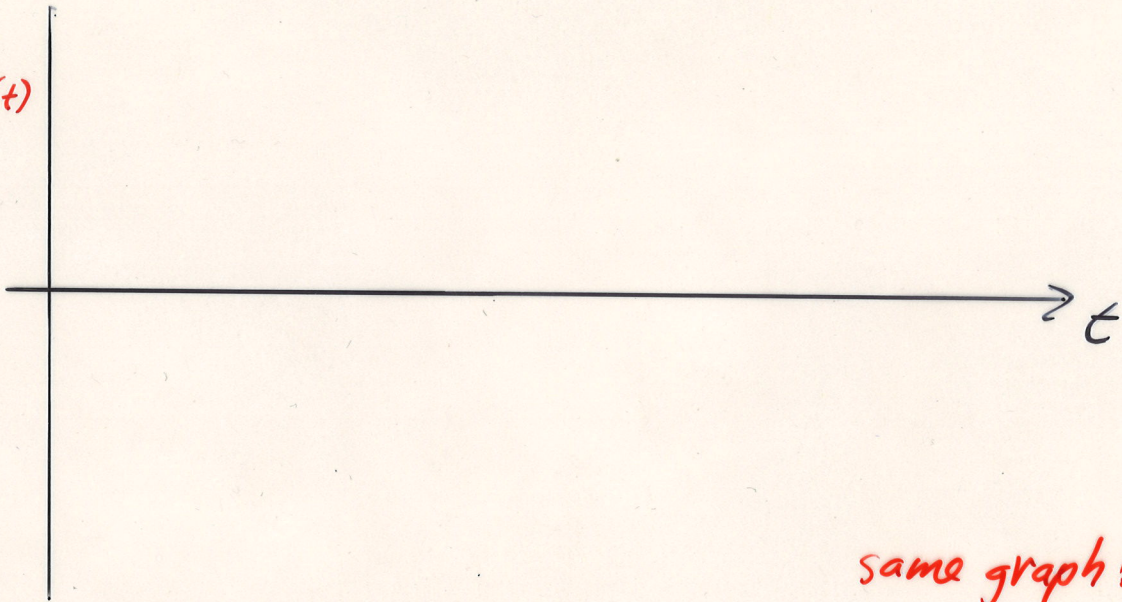

same graph!

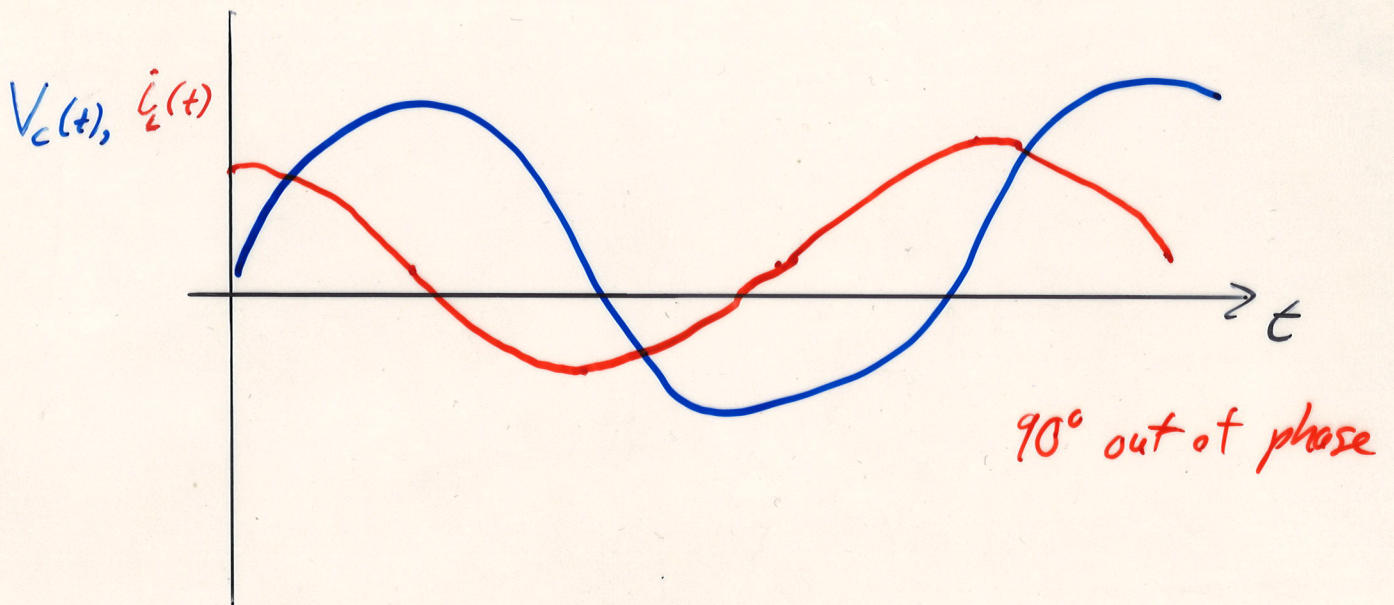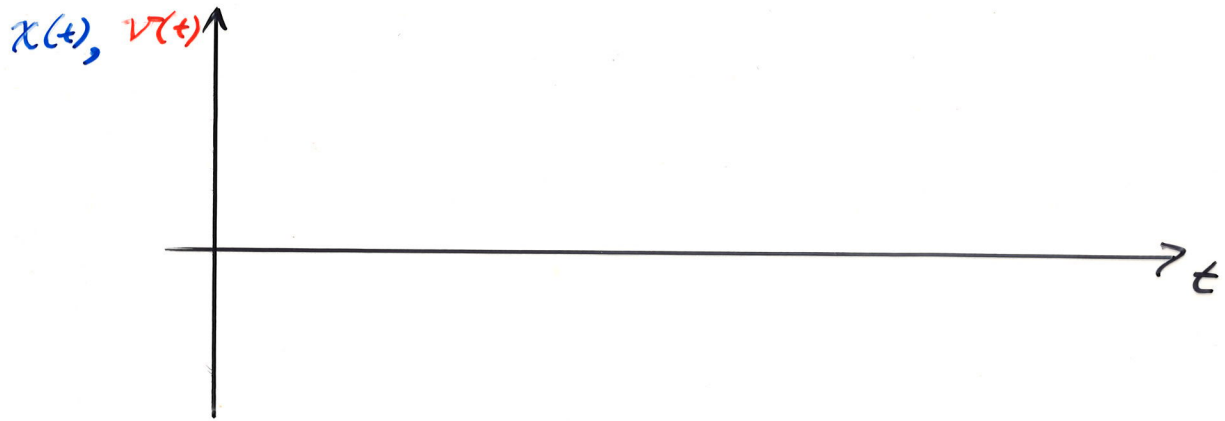

Conservation of Energy

Mech

$$E = K + U$$
$$= \frac{1}{2}mv^2 + \frac{1}{2}kx^2$$

Conserved $\Rightarrow \frac{dE}{dt} = 0$ ($E = \text{constant}$)

$$0 = \frac{dE}{dt} = \frac{1}{2}m(2v) \underbrace{\frac{dv}{dt}}_a + \frac{1}{2}k(2x) \underbrace{\frac{dx}{dt}}_v$$

chain rule

$$0 = mva + kvx = v(ma + kv)$$

either $v=0$ for all times rest

$$\text{or } ma + kv = 0 = m \frac{dx^2}{dt^2} + kv$$

Elec

$$E_{\text{total}} = U_E + U_B$$
$$= \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} L i^2$$

oscillation

Inductors store energy.
(so do capacitors!)

Capacitors store energy in the electric
field:

$$U_E = \frac{1}{2} C V^2 = \frac{1}{2} \frac{Q^2}{C}$$


$$Q = CV$$

Inductors store energy in the magnetic
field:

$$U_B = \frac{1}{2} L i^2$$

Resistance

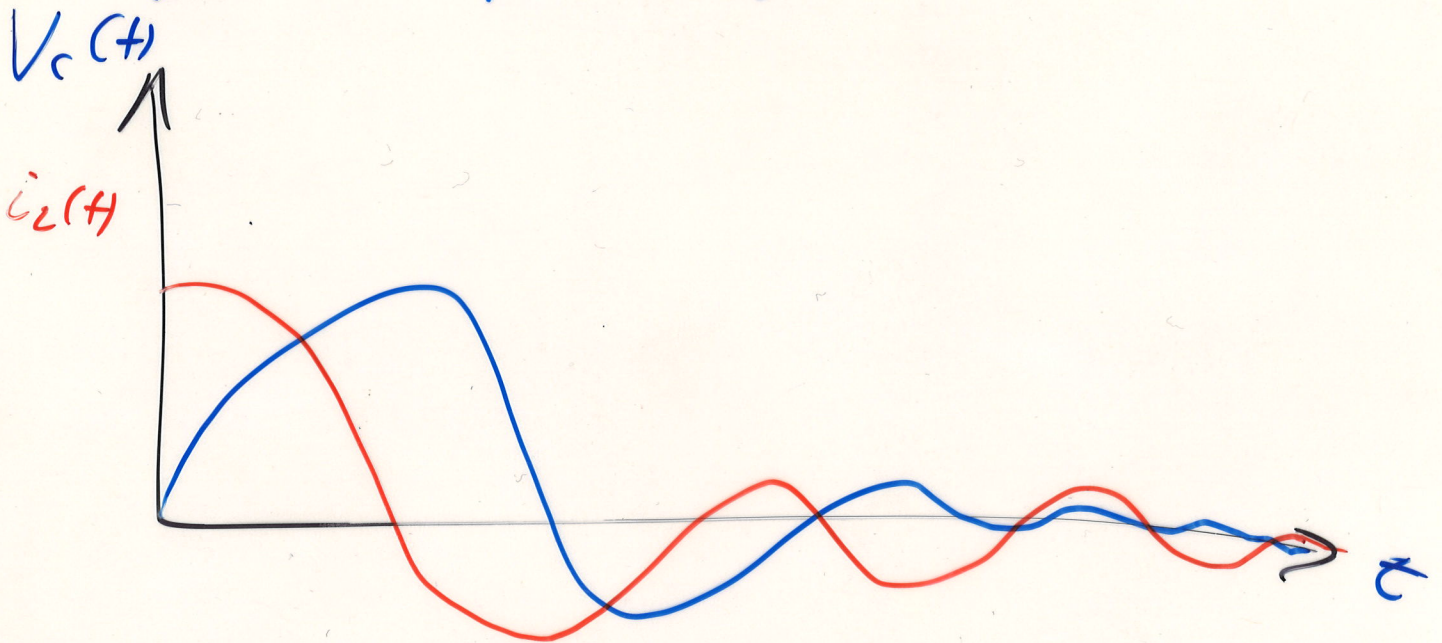If you add a resistor to an LC circuit then some energy from the electric and magnetic fields is converted into heat by the resistor. The oscillations die out exponentially.



Mechanical - Electrical Correspondences

x

$$v = \frac{dx}{dt}$$

m

k

large $k \leftrightarrow$ stiff spring

$m \uparrow$

$k \downarrow$

$$\omega = \sqrt{\frac{k}{m}}$$

q

$$i = \frac{dq}{dt}$$

L

$\frac{1}{C}$

small capacitor

$L \uparrow$


$C \uparrow$

$$\omega = \sqrt{\frac{1}{LC}}$$

eg. $L = 1 \text{ mH}$ $C = 1 \mu\text{F}$

$$\omega = 32,000 \frac{\text{rad}}{\text{s}}$$

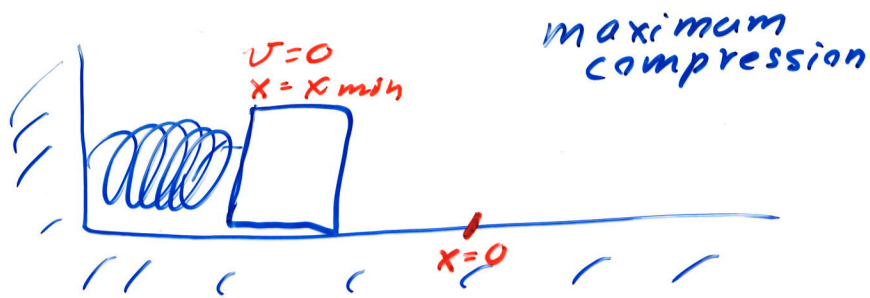
$$f = \frac{\omega}{2\pi} = 5000 \frac{\text{cycles}}{\text{s}} = 5000 \text{ Hz}$$



$t=0$

$$U = \frac{1}{2} k x_{min}^2 = \frac{1}{2} k A^2$$

$$K = 0$$

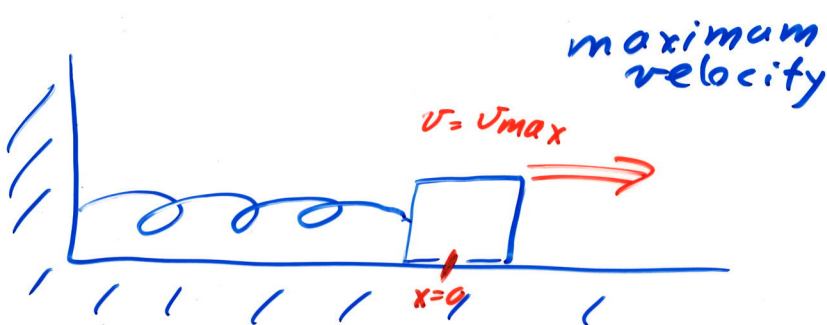


$t = \frac{1}{4}$ cycle

$$U = 0$$

$$K = \frac{1}{2} m v_{max}^2 = \frac{1}{2} k A^2$$

$t = \frac{1}{2}$ cycles

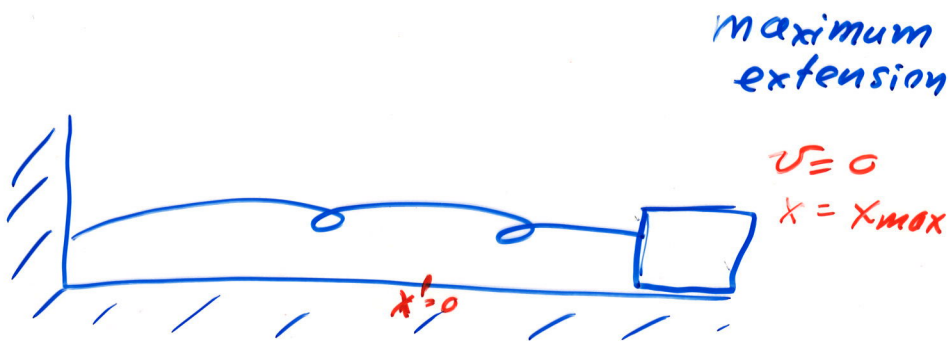


$$U = \frac{1}{2} k x_{max}^2 = \frac{1}{2} k A^2$$

$$K = 0$$

$$U_E = \frac{1}{2} \frac{q_{\max}^2}{C}$$

$$U_B = 0$$

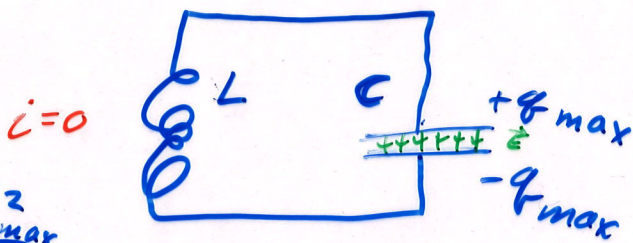


Capacitor
fully charged
(positive on the
top plate)

$$t = 0$$

$$U_E = 0$$

$$U_B = \frac{1}{2} L i_{\max}^2$$

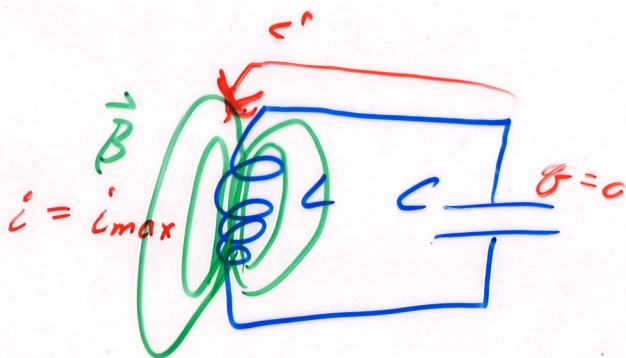


Capacitor
discharged

$$t = \frac{1}{4} \text{ cycle}$$

$$t = \frac{1}{2} \text{ cycle}$$

$$U_E = \frac{1}{2} \frac{q_{\max}^2}{C}$$

$$U_B = 0$$

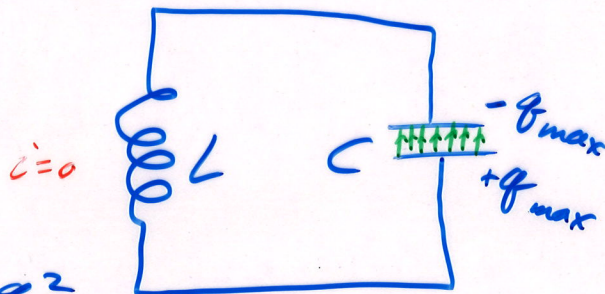

Capacitor
fully charged
(but positive on
the bottom plate)

AC Circuits

(Alternating ~~Current~~ ^{Voltage})

Consider a source of potential difference (seat of emf, voltage supply) whose voltage varies sinusoidally with time

$$V(t) = \underbrace{V_0}_{\text{Maximum Voltage}} \sin(\omega t - \phi)$$




Put a resistor in a circuit with this Alternating Voltage. Demo

In the U.S. $V_0 = 163$ volts

$$f = 60 \text{ Hz} = 60 \frac{\text{cycles}}{\text{sec}}$$

$$\omega = 2\pi f = 377 \frac{\text{rad}}{\text{sec}}$$

A purely resistive circuit

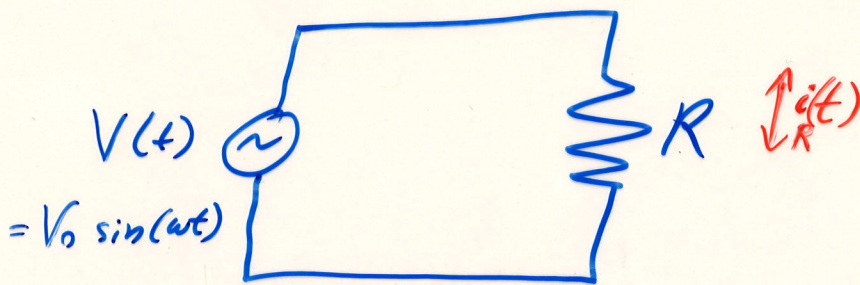


Voltage across the resistor:

$$V_R = V_0 \sin(\omega t)$$

Current through the resistor:


$$i_R = \frac{V_R}{R} = \frac{V_0 \sin(\omega t)}{R}$$

$$V = iR$$

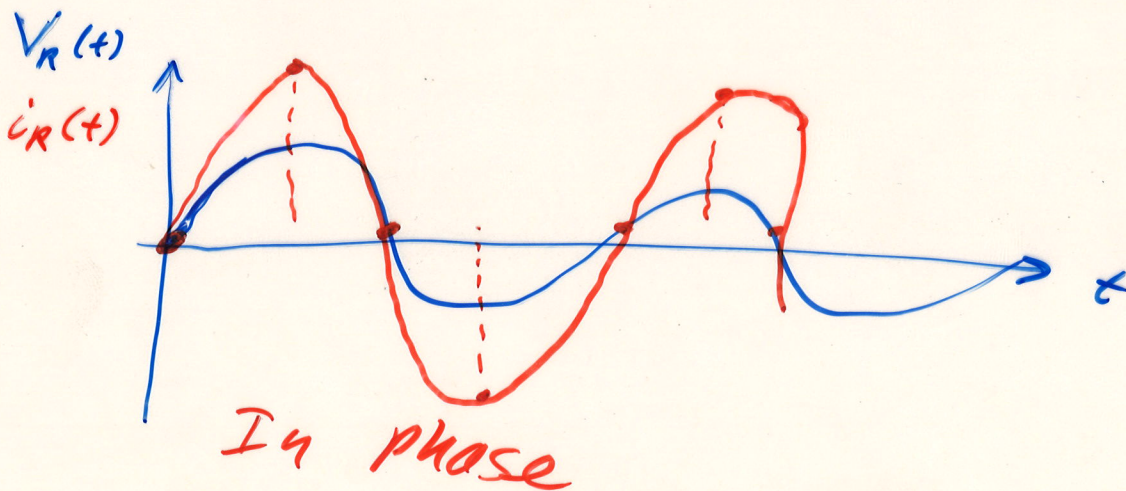


$i(t)$ and $V_R(t)$
in phase.

Phasors

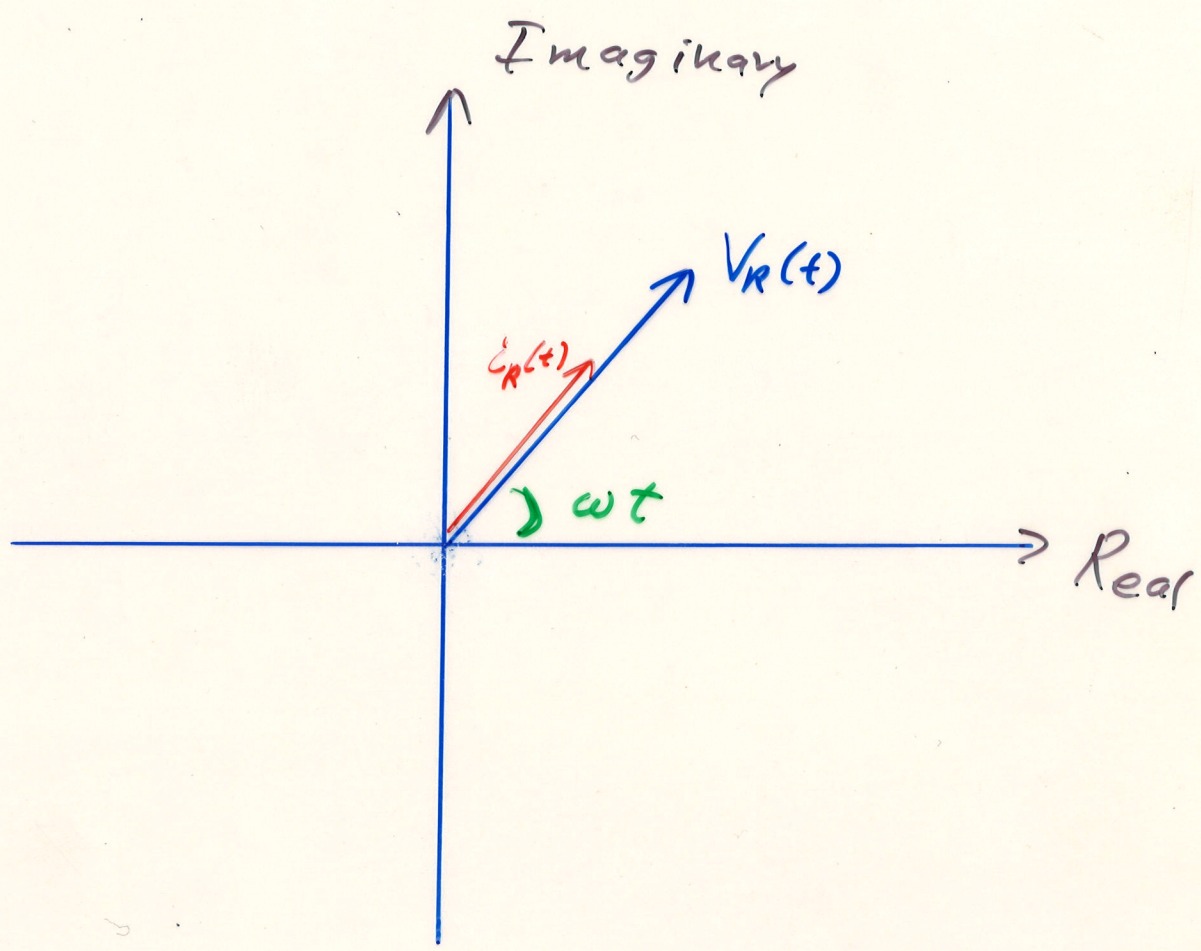

A purely capacitive circuit

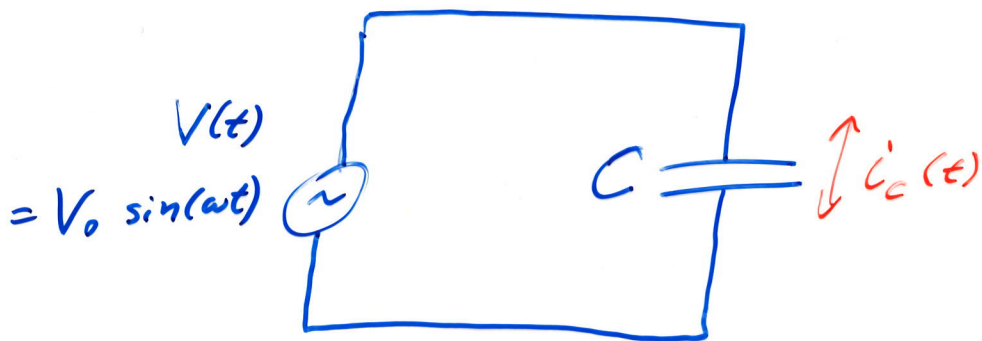

Voltage across the capacitor:

$$V_c(t) = V_0 \sin(\omega t)$$

$$q(t) = C V_c(t)$$

Charge on capacitor plate:

$$q_c(t) = C V_c(t) = C V_0 \sin(\omega t)$$

Current through the capacitor

$$\begin{aligned} i_c(t) &= \frac{dq_c}{dt} = \omega C V_0 \cos(\omega t) \\ &= \omega C V_0 \sin(\omega t + 90^\circ) \end{aligned}$$

↑ change to radians

This will look similar to the purely resistive result: $i_R = \frac{V_R}{R} = \frac{V_0}{R} \sin(\omega t)$

if we define the "capacitive reactance"

$$\chi_c \equiv \frac{1}{\omega C}$$



then
$$i_c = \omega C V_0 \sin(\omega t + 90^\circ)$$
$$= \frac{V_0}{\chi_c} \sin(\omega t + 90^\circ)$$

Think of the capacitive reactance as the "resistance" of a capacitor to alternating current flow.

Also, note that the current i_c is 90° ahead of the voltage V_c .


ICE

Phasors ready, Captain.

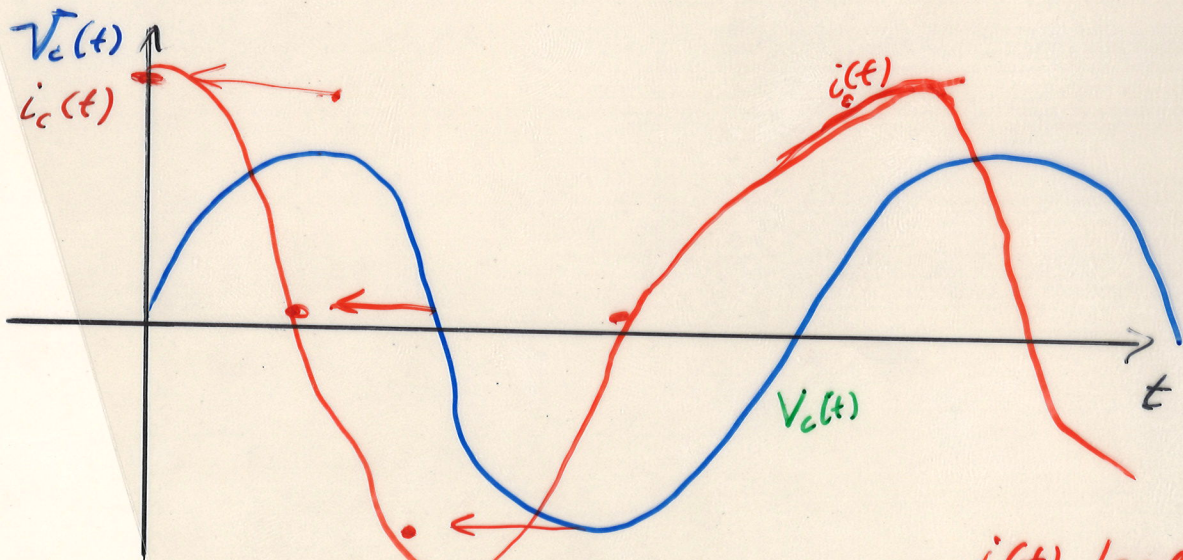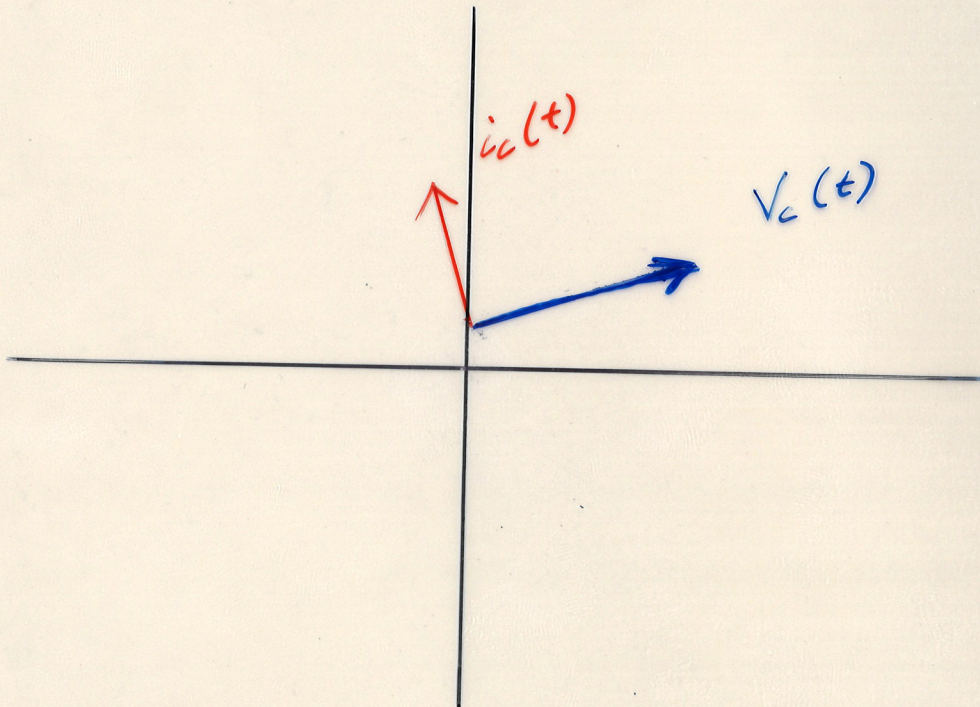

$i(t)$ leads $V_c(t)$
by 90°

A purely inductive circuit

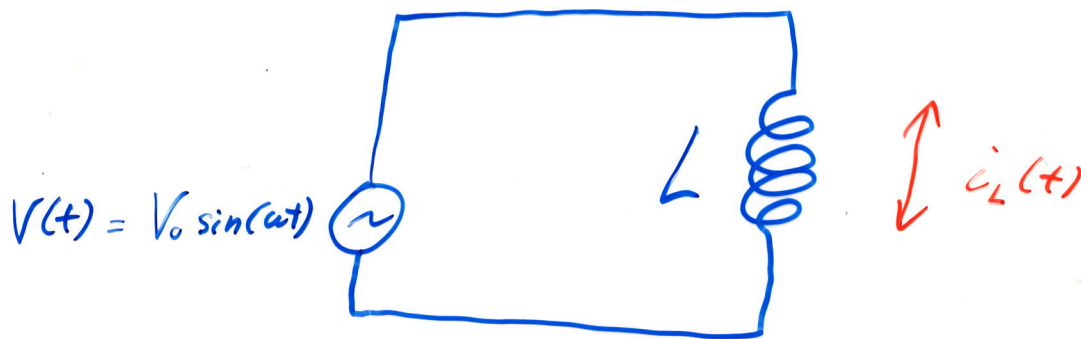

Voltage across the inductor:

$$V_L(t) = V_0 \sin(\omega t)$$

For an inductor

$$V_L = L \frac{di}{dt} \quad \frac{di}{dt} = \frac{V_0 \sin(\omega t)}{L}$$

Current through the inductor

$$i_L = \int \left(\frac{di}{dt} \right) dt = \frac{V_0}{L} \int \sin(\omega t) dt$$

$$= -\frac{V_0}{L\omega} \cos(\omega t)$$

$$= \frac{V_0}{L\omega} \sin(\omega t - 90^\circ)$$

We can make this resemble the purely resistive result

$$i_R = \frac{V_R}{R} = \frac{V_0}{R} \sin(\omega t)$$

if we define the "inductive reactance"

$$X_L \equiv \omega L$$

then

$$i_L = \frac{V_0}{\omega L} \sin(\omega t - 90^\circ)$$



$$= \frac{V_0}{X_L} \sin(\omega t - 90^\circ)$$

Think of the inductive reactance as the "resistance" of an inductor to alternating current flow.

Note that this time, the current i_L is 90° behind the voltage V_L .

ELI

Phasor Diagram

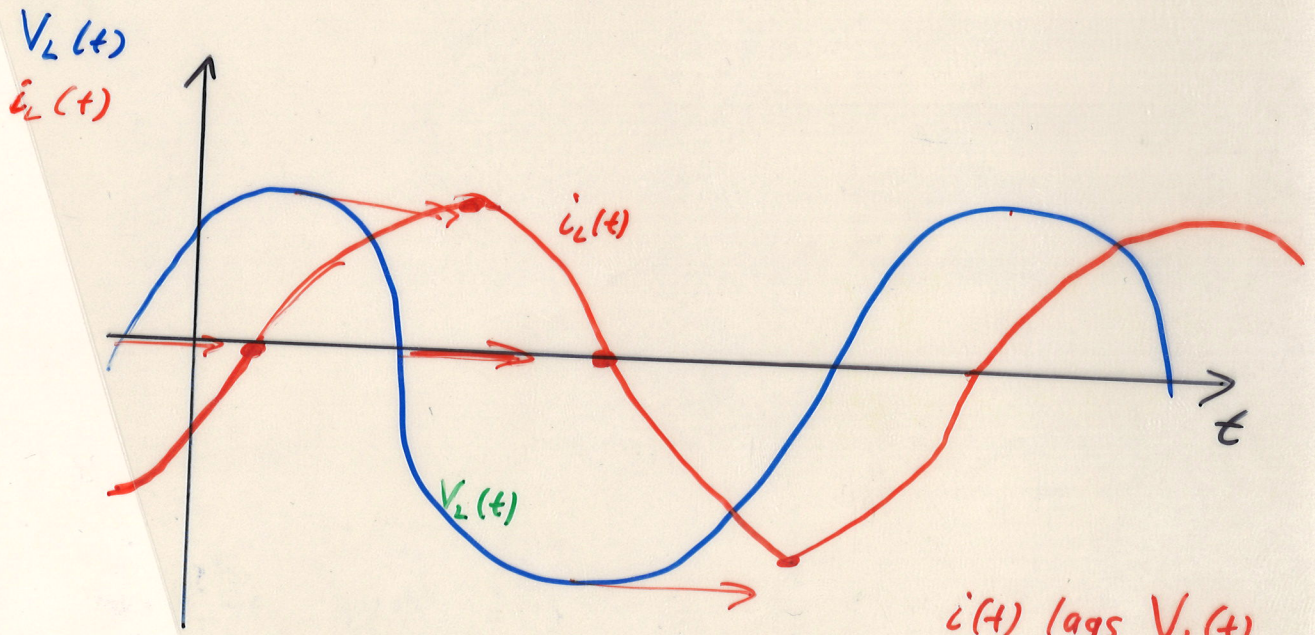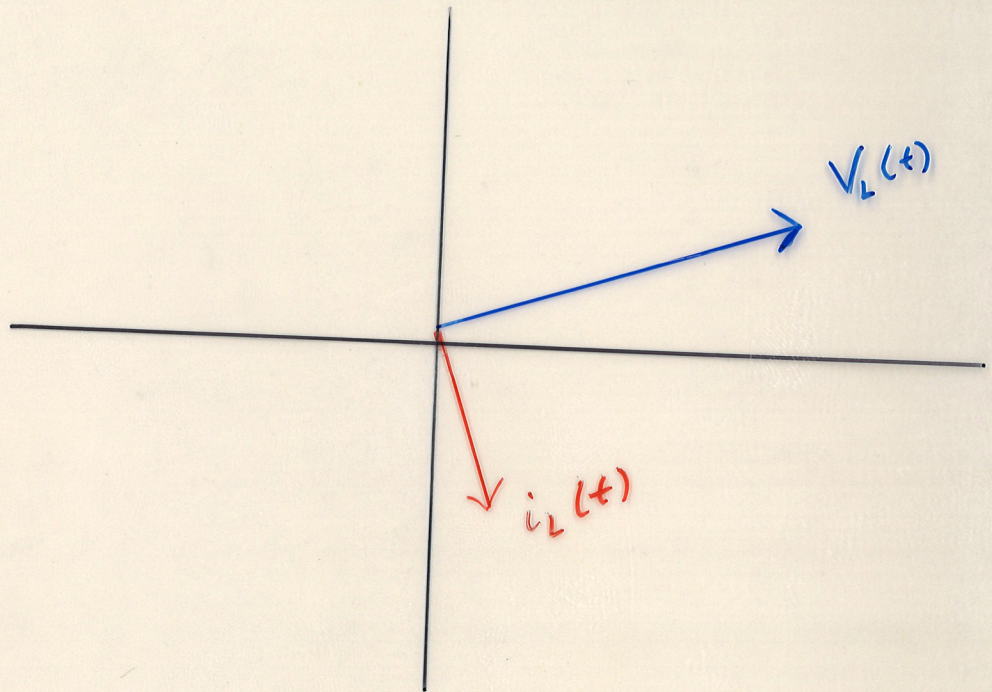

$i(t)$ lags $V_L(t)$
by 90°

Reactance

$$X_c = \frac{1}{\omega C}$$

This is small for large angular frequencies

A capacitor offers almost no "resistance" to high-frequency AC flow, but a capacitor offers infinite "resistance" to very low-frequency AC (that is, DC) flow.

$\rightarrow \omega = 0$


$$X_L = \omega L$$

This is large for large angular frequencies

For DC flow, an inductor looks like a resistance-less piece of wire.

However, an inductor offers considerable resistance to high-frequency AC flow.

A series RLC circuit

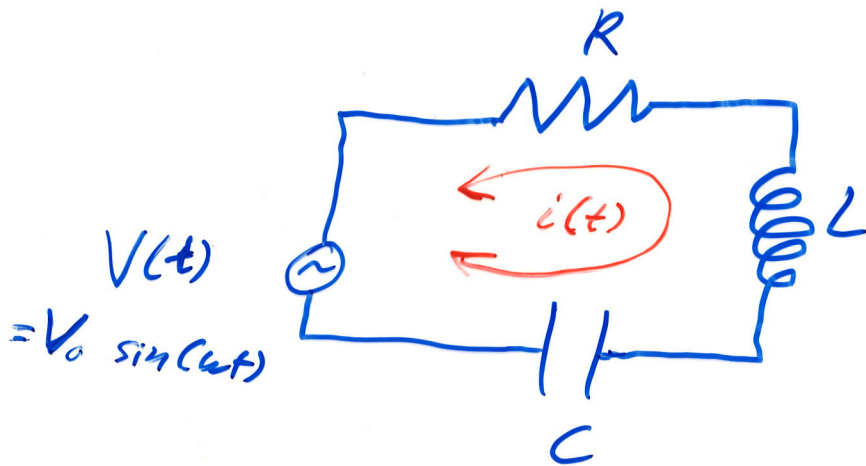

Kirchhoff's Loop Rule is valid at any instant.


$$V_{\text{supply}}(t) - V_R(t) - V_L(t) - V_C(t) = 0$$

$$\text{At } t_1) \quad 100 - 100 - 25 + 25 = 0$$

$$\text{At } t_2) \quad 0 - 0 - (-25) - 25 = 0$$

Phasor Diagram

ELI-ICE

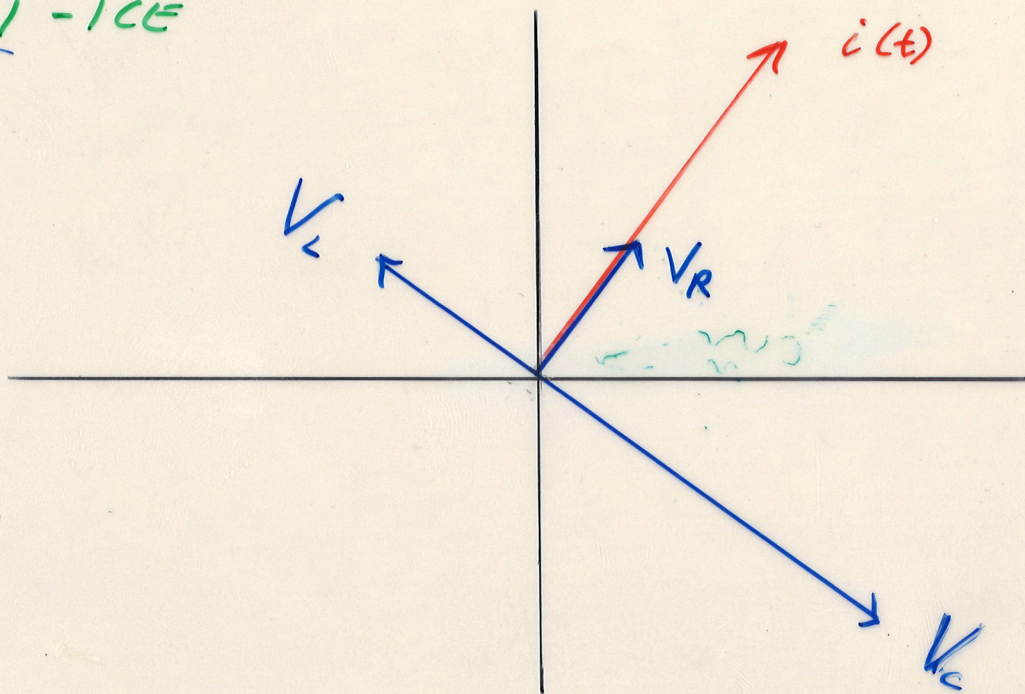

The three voltages: V_R , V_L , V_C add like vectors

$$\begin{aligned} V_o^2 &= V_R^2 + (V_L - V_C)^2 \\ &= (iR)^2 + (iX_L - iX_C)^2 \end{aligned}$$

$$V_o = i \sqrt{R^2 + (X_L - X_C)^2} \equiv iZ$$

$$Z = \sqrt{R^2 + (\chi_L - \chi_C)^2}$$

is called the impedance of the AC circuit. It is frequency - dependent.

$$\chi_C = \frac{1}{\omega C}$$

$$\chi_L = \omega L$$

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

Resonance occurs when Z is a minimum; $Z = R$

$$\text{When } \omega L - \frac{1}{\omega C} = 0 \quad \text{or} \quad \omega L = \frac{1}{\omega C}$$

$$\text{or } \omega^2 = \frac{1}{LC} \quad \text{or} \quad \omega = \sqrt{\frac{1}{LC}}$$


$Y = \frac{1}{Z}$ is called the

Admittance

$$Y = \frac{1}{\sqrt{R^2 + (X_C - X_L)^2}}$$

At resonance Z is a minimum

Y is a maximum

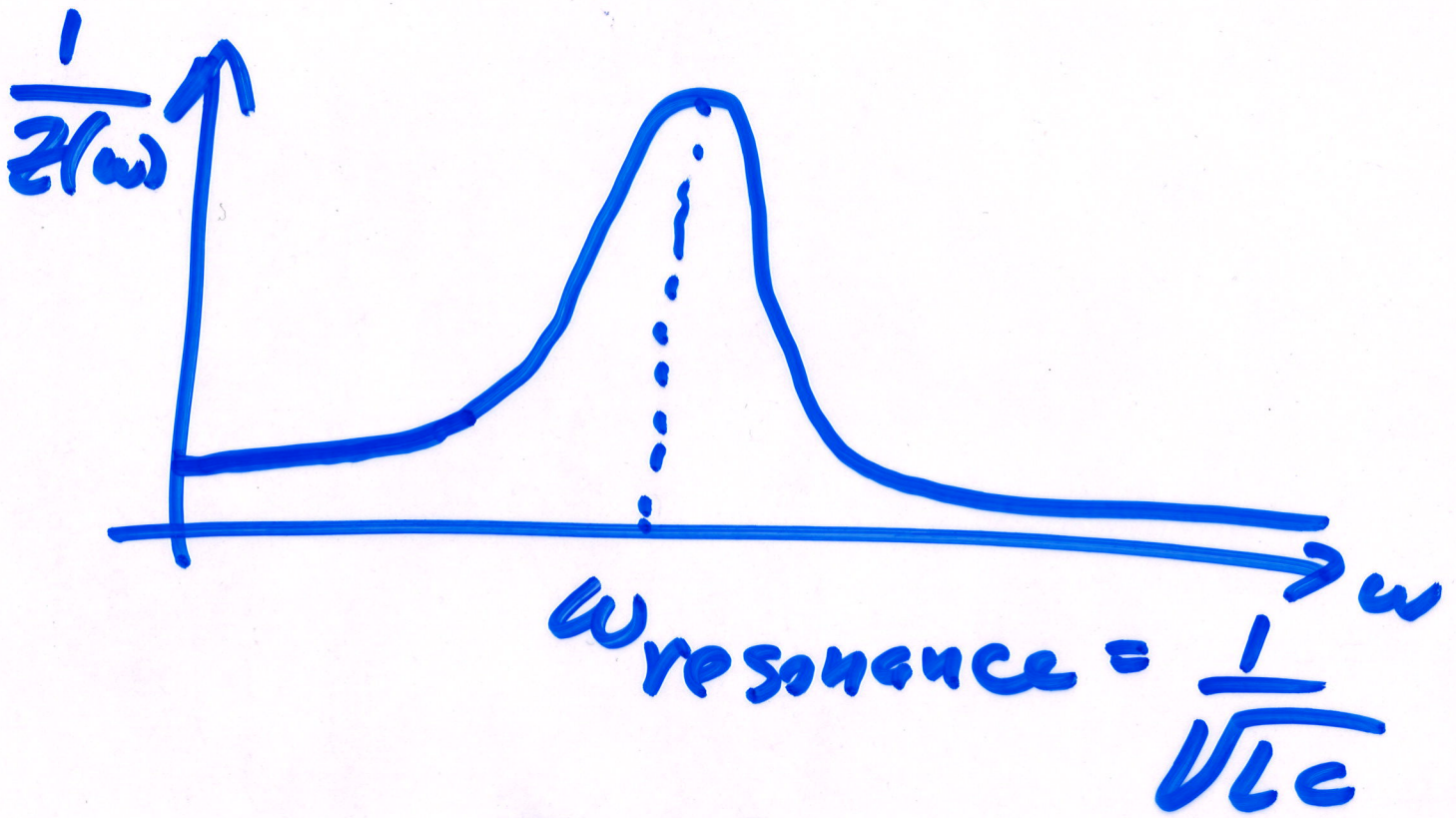

$$Z = R$$

↑
at
resonance

AC Problems

$$\text{Find } i_{\max} = \frac{V_{\text{source}}^{\max}}{Z} = \frac{V_{\text{source}}^{\max}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$V_{R \max} = i_{\max} R \quad - \quad \times \quad i_{\max} = \frac{V_{\text{source}}^{\max}}{R}$$

$$V_{C \max} = i_{\max} X_C = i_{\max} \frac{1}{\omega C} \quad -$$

$$V_{L \max} = i_{\max} X_L = i_{\max} \omega L \quad -$$

$$P_{\max} = i_{\max}^2 R$$

$$P_{\text{AVG}} = \frac{1}{2} P_{\max} = \frac{1}{2} i_{\max}^2 R = (i_{\text{rms}})^2 R$$


$$i_{\text{rms}} = \frac{i_{\max}}{\sqrt{2}}$$

$$V_0 = V_{\max} \sin(\omega t)$$

$$R = 20 \Omega$$

$$V_0 = (12V) \sin(100t)$$

$$V_{\max} = 12V$$

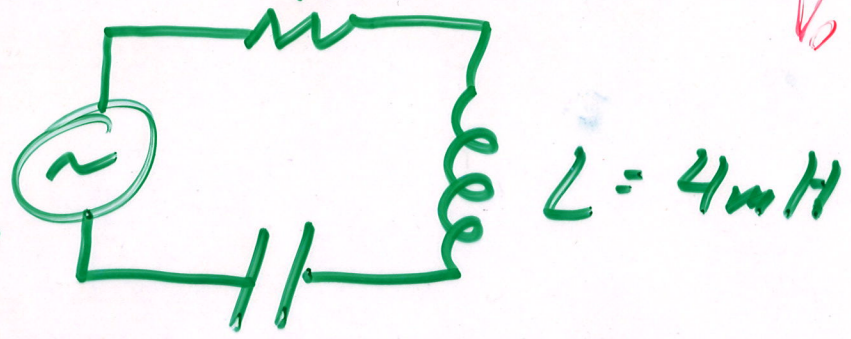

$$L = 4 \text{ mH}$$

$$\omega = 100 \frac{\text{rad}}{\text{s}}$$

$$C = 10 \text{ nF}$$

$$\text{mille} = 10^{-3}$$
$$\text{nano} = 10^{-9}$$

$$Z = \sqrt{R^2 + (\chi_L - \chi_C)^2}$$

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} =$$

$$Z = \sqrt{(20 \Omega)^2 + \left[(100 \frac{\text{rad}}{\text{s}})(4 \text{ mH}) - \frac{1}{(100 \frac{\text{rad}}{\text{s}})(10 \text{ nF})} \right]^2}$$

$$Z = 10^6 \Omega = 1 \text{ M}\Omega$$

$$I_{\max} = \frac{V_{\max}}{Z} = \frac{12V}{1 \text{ M}\Omega} = 12 \mu A$$


$$V_{R \max} = i_{\max} \cdot R = (12 \mu A) 20 \Omega = 240 \mu V$$

$$V_{L \max} = i_{\max} X_L = i_{\max} \omega L$$

$$= (12 \mu A) (100 \frac{\text{rad}}{\text{s}}) (4 \text{ mH}) = 4.8 \times 10^{-6} \text{ V}$$

$$V_{C \max} = i_{\max} X_C = \frac{i_{\max}}{\omega C} = \frac{12 \mu A}{(100 \frac{\text{rad}}{\text{s}}) (10 \text{ nF})}$$

$$\approx 12 \text{ V}$$

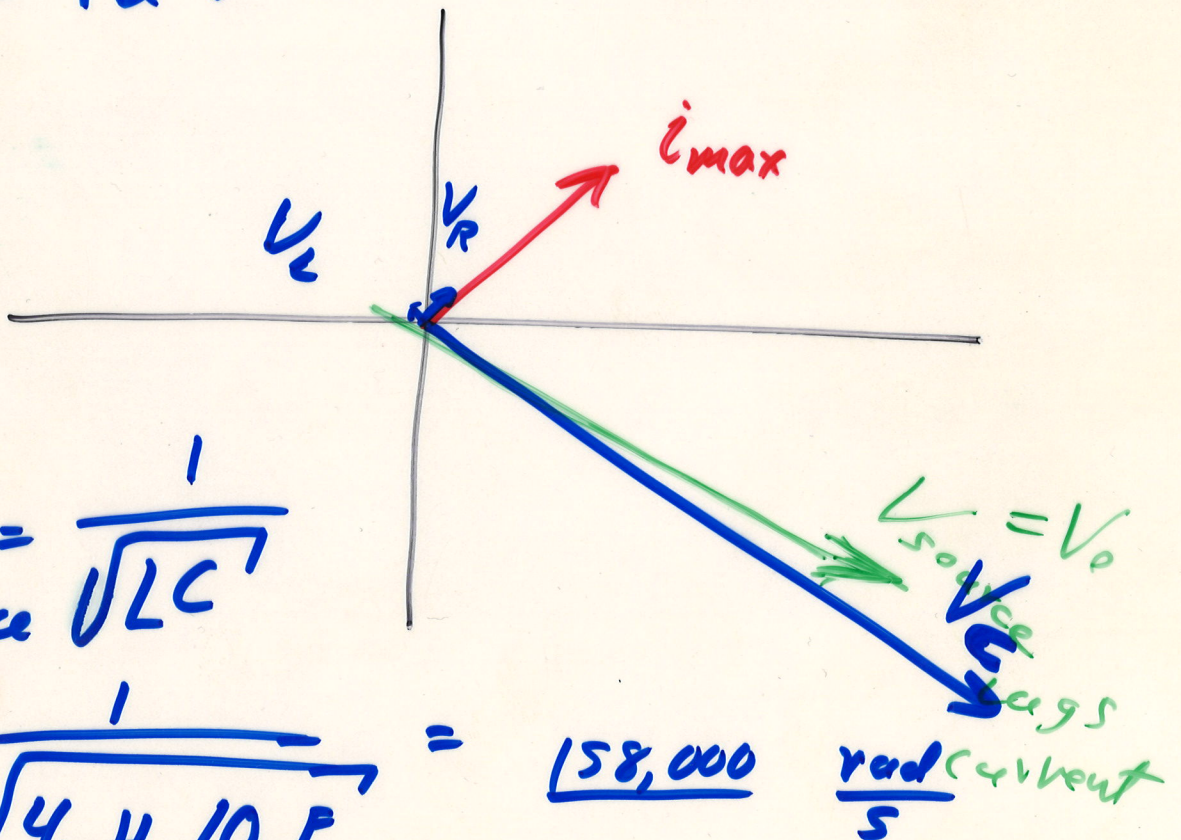

$$\omega_{\text{Resonance}} = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{4 \text{ mH} \cdot 10 \text{ nF}}} = \underline{158,000} \frac{\text{rad}}{\text{s}}$$

This circuit is capacitive

- $V_C > V_L$

- $X_C > X_L$

- V_S lags current i'

- ω is ~~at~~ below resonance

$100 \frac{\text{rad}}{\text{s}}$

$158.1 \frac{\text{rad}}{\text{s}}$

$\omega_{\text{res}} = \frac{1}{\sqrt{LC}}$

AC Power

purely resistive

$$P_{\text{inst}} = [i(t)]^2 R = [i_{\text{max}} \sin(\omega t)]^2 R$$
$$= (i_{\text{max}})^2 R \sin^2(\omega t)$$

$$P_{\text{AVG}} = ?$$

Average value of $\sin^2(\omega t) = ?$

$$\langle \sin^2 \rangle = \frac{1}{2\pi} \int_0^{2\pi} \sin^2 \theta \, d\theta = \frac{1}{2\pi} \pi = \frac{1}{2}$$

$$= \frac{1}{4\pi} \int_0^{4\pi} \sin^2 \theta \, d\theta = \frac{1}{4\pi} 2\pi = \boxed{\frac{1}{2}}$$

$$P_{\text{AVG}} = \frac{1}{2} (i_{\text{max}})^2 R = \left(\frac{i_{\text{max}}}{\sqrt{2}} \right)^2 R \equiv i_{\text{RMS}}^2 R$$

$$i_{\text{RMS}} = \frac{i_{\text{max}}}{\sqrt{2}}$$

RMS \rightarrow root mean square


$$i_{\text{RMS}} = \frac{i_{\text{max}}}{\sqrt{2}}$$

$$V_{\text{RMS}} = \frac{V_{\text{max}}}{\sqrt{2}}$$

$$V_{\text{RMS}} = 120 \text{ volts AC}$$

$$V_{\text{max}} = \sqrt{2} V_{\text{RMS}} = \sqrt{2} 120 \text{ volts} = 170 \text{ volts}$$

Transformer

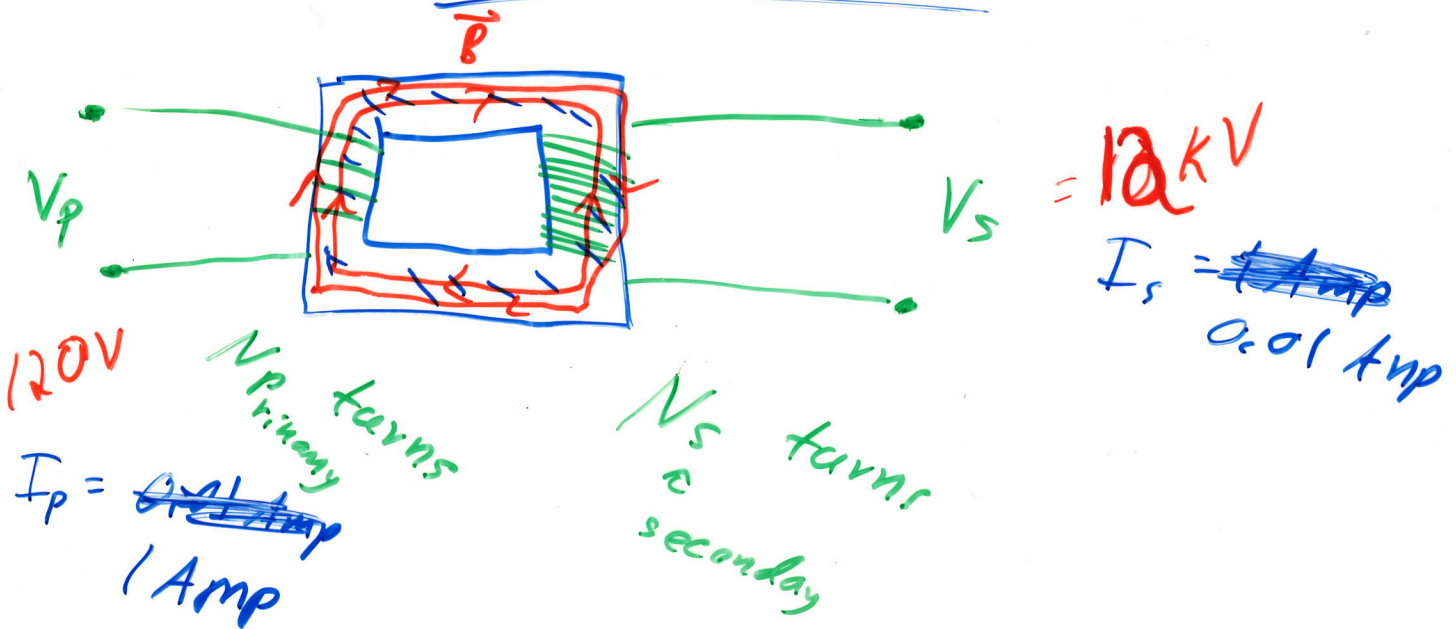

Energy Conservation - Power Cons.
time


$$P_p = I_p V_p = P_s = I_s V_s$$

rms rms rms rms

$$\frac{V_p}{N_p} = \frac{V_s}{N_s} \Rightarrow I_p N_p = I_s N_s$$

Magnetic Dipole Moment

For a flat current loop, the magnetic dipole moment is a vector $\vec{\mu}$ with magnitude $|\vec{\mu}| = i \cdot \text{Area}$ and direction given by the right-hand rule

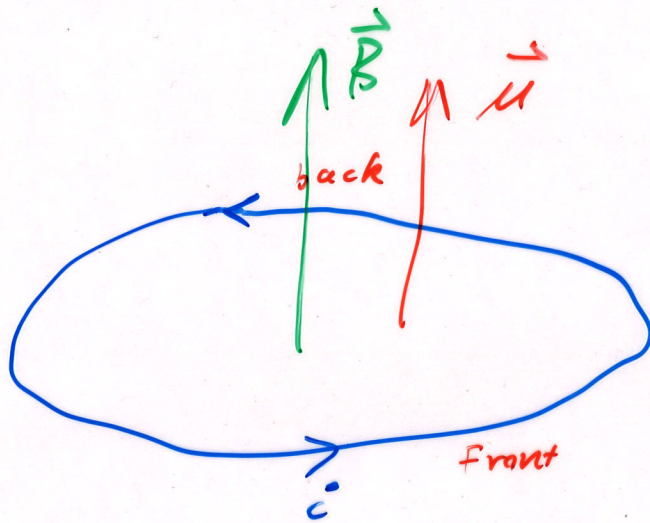

If $\text{Area} \rightarrow 0$ and $i \rightarrow \infty$ with $i \cdot \text{Area} = \text{const.}$ we get a pure dipole magnetic field.

