
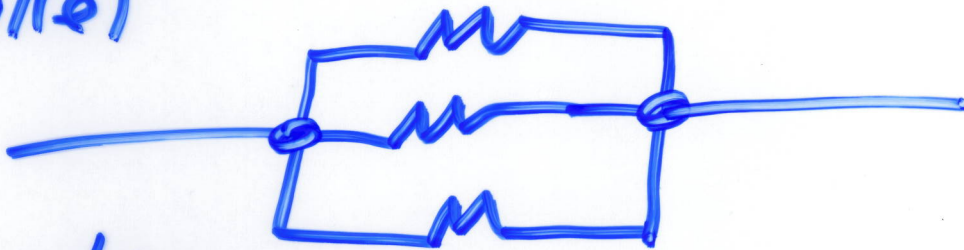



Series 
(same current)

parallel



(same voltage across)

neither

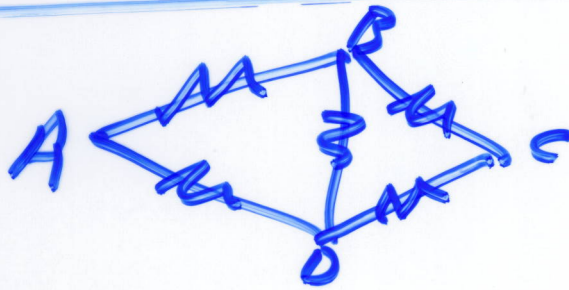

~~Measure~~
Determine


Resistance.




Measure voltage } V
across R

Measure current } I
through R

$$R = \frac{V}{I}$$

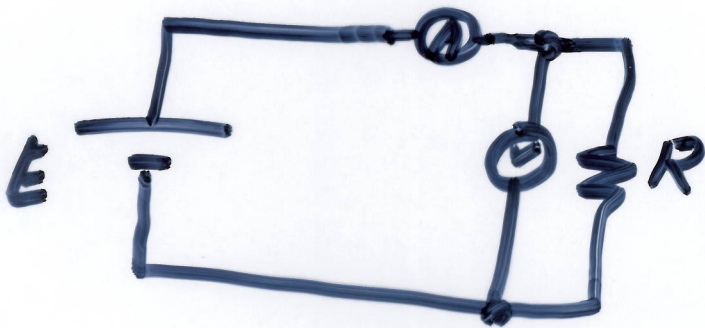

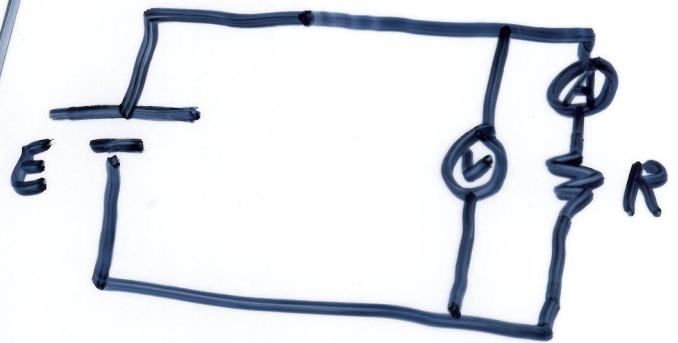
$$R_{\text{calc}} = \frac{V}{I_R + I_V} < R_{\text{true}}$$



$$R_{\text{calc}} = \frac{V_R + V_A}{I} > R_{\text{true}}$$

~~Measure~~
Determine

Resistance.


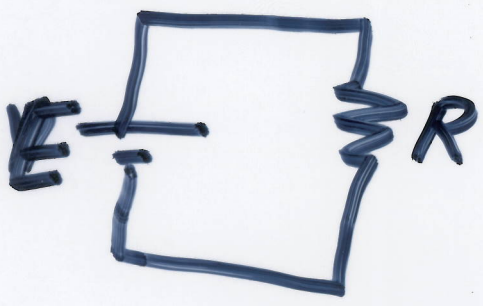


Measure voltage } V
across R

Measure current } I
through R

$$R = \frac{V}{I}$$

Suppose R is small ~ 10 Ω

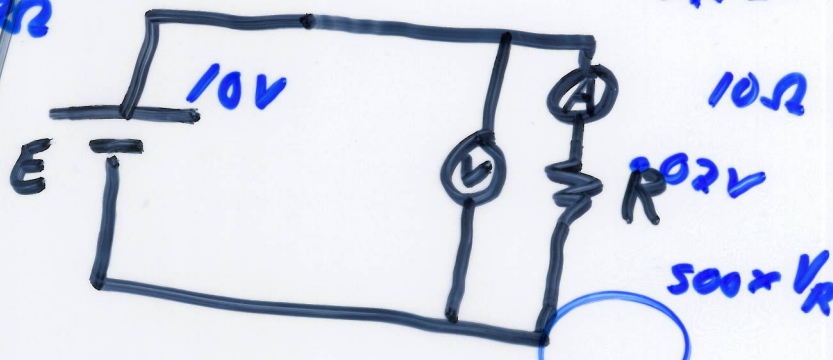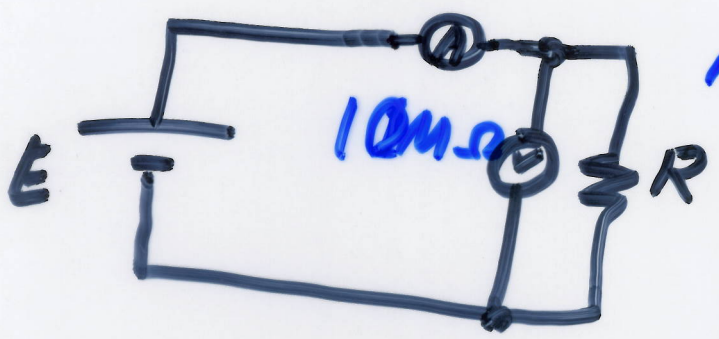

9.98V
5kΩ

10V
10Ω
202V

$$R_{calc} = \frac{V}{I_R + I_V}$$

$$R_{calc} = \frac{V_R + V_A}{I} > R_{true}$$

< R_{true}
use for small R

~~Measure~~
Determine

Resistance.





Measure voltage } V
across R

Measure current } I
through R

$$R = \frac{V}{I}$$

Large $R \sim 10M\Omega$

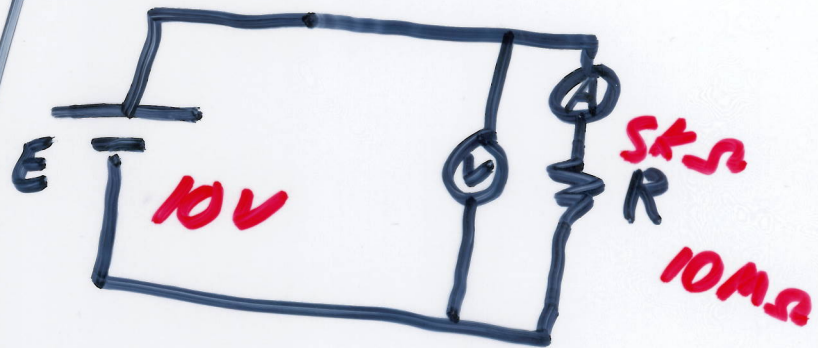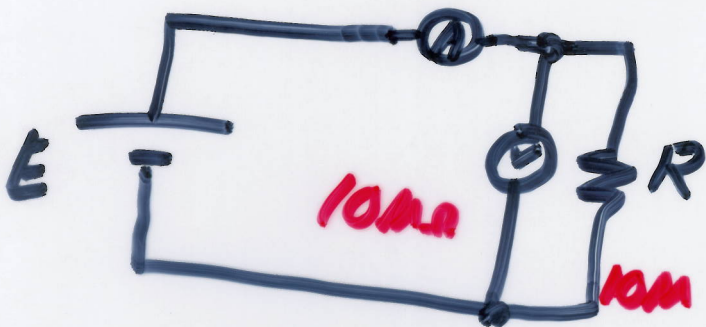

$$R_{calc} = \frac{V}{I_R + I_V}$$

$\leftarrow R_{true} \sim I_R$

$$R_{calc} = \frac{V_R + V_A}{I}$$

$\leftarrow R_{true}$


USE this for
Large R



- 0 Black
- 1 Brown
- 2 Red
- 3 Orange
- 4 Yellow
- 5 Green
- 6 Blue
- 7 Violet
- 8 Grey
- 9 White


$$20 \times 10^3 = \cancel{20} 20K \Omega$$

Voltage Divider / Thévenin's Theorem

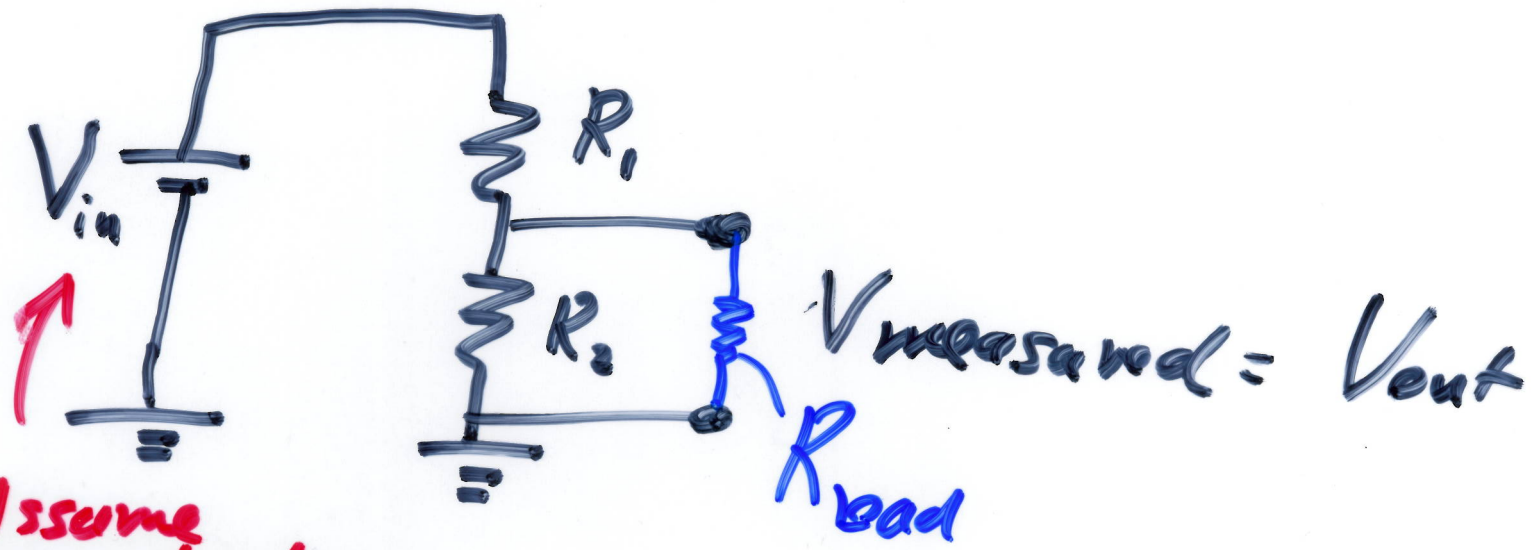


$$I = \frac{V_{in}}{R_1 + R_2}$$
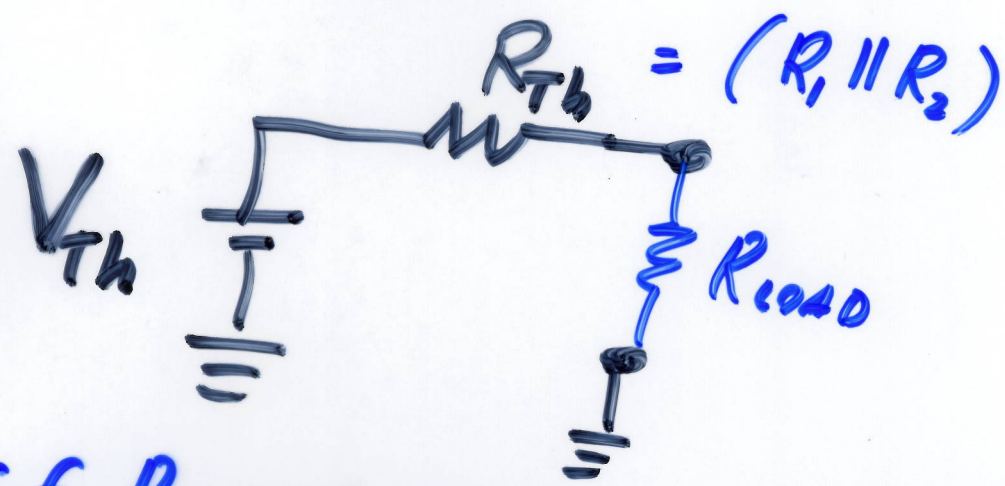
$$V_{out} = IR_2 = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$



Set $R_{load} \rightarrow \infty \Rightarrow V_{Th} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$
 Set $R_{load} = 0 \Rightarrow$ get short circuit current
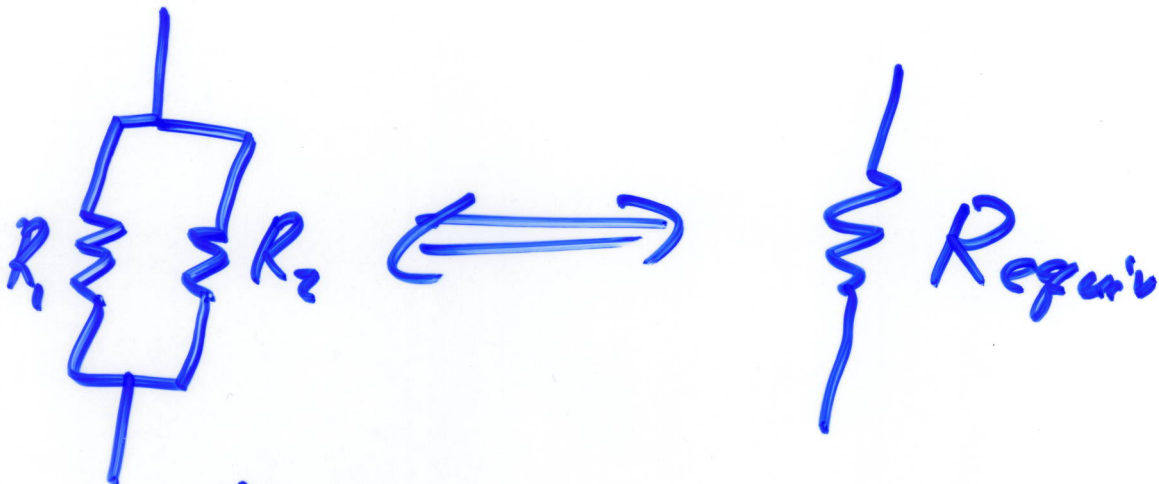
$$(R_1 \parallel R_2) = \frac{R_1 R_2}{R_1 + R_2} = R_{\text{equiv}}$$



$$\frac{1}{R_{\text{equiv}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$

e.g. $20\Omega \parallel 20\Omega = 10\Omega$

