



What are the four currents an instant after the switch is closed? (Positive values if the currents are flowing in the directions indicated; negative if flowing the opposite direction.)

What are the four currents a long time after the switch has been closed?

What are the four currents an instant after the switch is opened again, after having been closed for a long time?