
Design a common emitter amplifier of nominal gain $g = -10$ to work at $f = 100$ kHz. Let the supply voltages $V_{CC} = +12$ V, $V_{EE} = -12$ V. Center the output voltage as best you can. Use capacitive coupling and set the quiescent current at 1.0 mA.