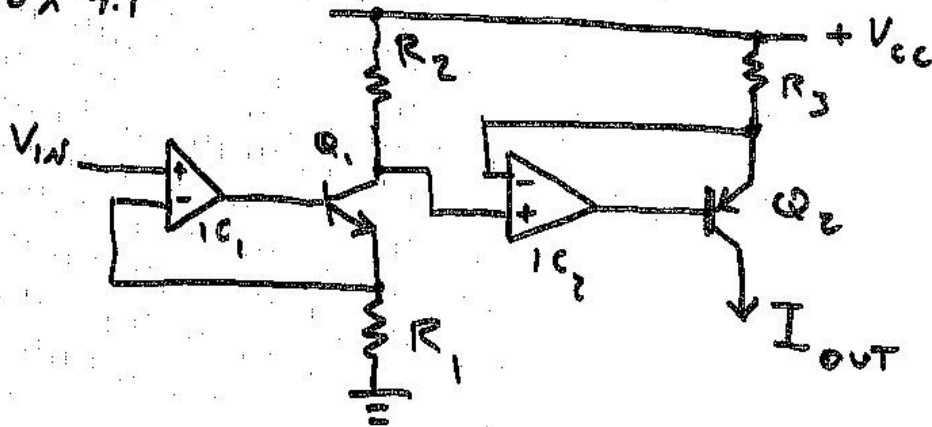


EX 4.1



NOTE: BOTH OP-AMPS HAVE NEG. FEEDBACK

$$I_{OUT} = \frac{V_{CC} - V_{E, Q2}}{R_3}$$

NOW,  $V_{E, Q2} = V_{IC2}^+ = V_{C, Q1}$  (NEG. FEEDBACK)

$$V_{C, Q1} = V_{CC} - I_{C, Q1} \cdot R_2$$


$$\text{BUT, } I_{C, Q1} \approx I_{E, Q1} = \frac{V_{IN}}{R_1}$$

$$\Rightarrow V_{C, Q1} = V_{CC} - V_{IN} \frac{R_2}{R_1}$$

$$\text{SO, } I = \frac{V_{CC} - (V_{CC} - V_{IN} \frac{R_2}{R_1})}{R_3} = + \frac{V_{IN} R_2}{R_1 R_3}$$

Ex. 4.2

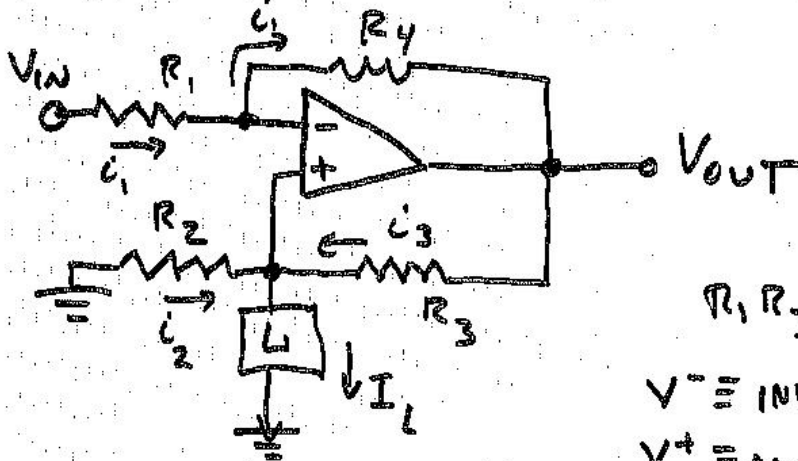THE STRATEGY IS TO EXAMINE CURRENT FLOW. IDEALLY, OP-AMPS DRAW NO INPUT CURRENT.



$$R_1 R_3 = R_2 R_4$$

$V^-$   $\equiv$  INVERTING VOLT.

$V^+$   $\equiv$  NON-INVERTING V.

$$i_1 = \frac{V_{IN} - V^-}{R_1} = \frac{V^- - V_{OUT}}{R_4} \quad (1)$$

$$I_L = i_2 + i_3$$

$$= \frac{0 - V^+}{R_2} + \frac{V_{OUT} - V^+}{R_3} \quad (2)$$

SINCE  $V^- = V^+$ , (1) BECOMES:

$$\frac{V_{IN} - V^+}{R_1} = \frac{V^+ - V_{OUT}}{R_4} \quad (3)$$

EX 4.2 CONT.

$$E_0 (3) \Rightarrow V_{OUT} - V^+ = -\frac{R_4}{R_1} (V_{IN} - V^+)$$

FROM (2)

$$-\frac{V^+}{R_2} - \frac{R_4}{R_1 R_3} (V_{IN} - V^+) = I_L$$


BUT  $R_1 R_3 = R_2 R_4$ , SO

$$I_L = -\frac{V^+}{R_2} - \frac{1}{R_2} (V_{IN} - V^+)$$

$$\therefore \boxed{I_L = -\frac{V_{IN}}{R_2}}$$


EX. 4.3

(a)

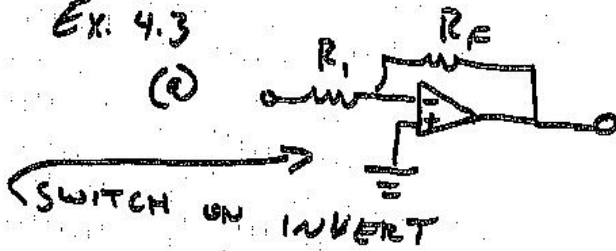

$R_F = R_{IN} = 10 \text{ k}\Omega$   
 OBVIOUSLY,  $G = -1$

SWITCH ON FOLLOWER:

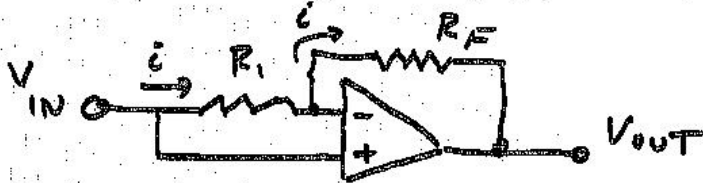

$$V^+ = V^- = V_{IN}$$

$$i = \frac{V_{IN} - V^-}{R_1} = 0$$

BUT


$$i = \frac{V^- - V_{OUT}}{R_F} = 0$$

$$\Rightarrow \underline{V_{OUT} = V^- = V_{IN}}$$

$\therefore \boxed{G = +1}$  AS ADVERTISED.

Ex. 4.3

(b)

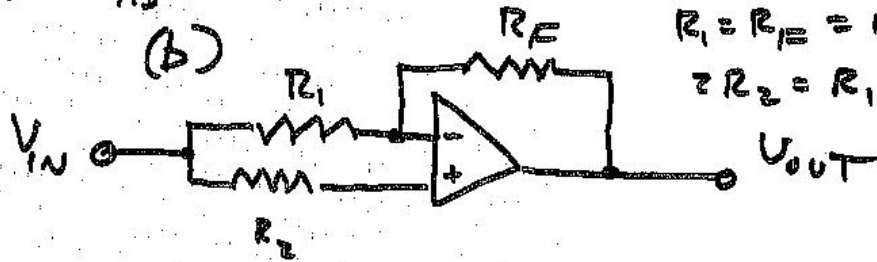

$R_1 = R_F = 10 \text{ k}\Omega$

$R_2 = R_1$

$V^+ = V_{IN}$  (+ INPUT DRAWS NO CURRENT)

NEG. FEEDBACK  $\Rightarrow V^+ = V^-$

BY REASONING IN 4.3 (a) THEN


$G = +1$

NOTE: NO CURRENTS FLOWING IN CIRCUIT !



$V^- = V^+ = 0$  ( $R_2$  IRRELEVANT)

CIRCUIT LOOKS LIKE:

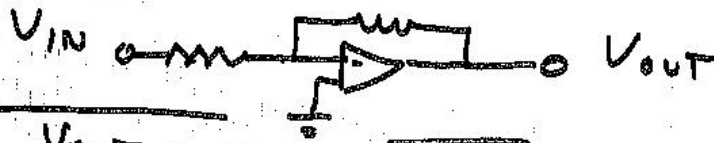

$$G = \frac{V_{OUT}}{V_{IN}} = -R_F/R_1 = -1$$